RADIO SETS SCR-608-A AND SCR-628-A

War Department Technical Manual TM 11-620

Radio Sets SCR-608-A and SCR-628-A

WAR DEPARTMENT WASHINGTON 25, D. C., 1 January, 1944.

TM 11-620, Radio Sets SCR-608- Λ and SCR-628- Λ , is published for the information and guidance of all concerned.

[A. G. 300.7 (6 August, 1943).] By order of the Secretary of War:

> G. C. MARSHALL, Chief of Staff.

Official: J. A. ULIO,

Major General, The Adjulant General, Distribution:

C and H6(4); Bn 18(4); IC18(2), 11(10), (For explanation of symbols see FM 21-6.)

TABLE OF CONTENTS

ECTION I.	Description. Pag	ţe.
		1
2	Performance Characteristics	1
3		1
4		7
- 5	Frequency Modulation	9
6	Mounting FT-237-(*)	
7.	Radio Receiver BC-683-A	
8.	Radio Transmitter BC-684-A	
9.	Remote Control Unit RM-29-D Dynamotors DM-34-(*), DM-35-(*), DM-36-(*), DM-37-(*)	
10.	Dynamotors DM-34-(*), DM-35-(*), DM-36-(*), DM-37-(*)	
11.		
12.	Mountings FT-284-(*) and FT-285-(*) and Frame FM-43	
13.	Mast Bases	
	Mart Buse Bracket MP-52	
15.	Mast Sections	
16.	Cords and Cordage	1
II.	Installation and Operation.	
17	Initial Procedure	9
	Installation	9
	Preparation for Usc	10
	Operation	32
21	Presetting Push Buttoes	16
	System Operation	1
111.	Functioning of Parts.	
28	Functioning of Radio Receiver BC-683-A Functioning of Radio Transmitter BC-684-A	i3
24	Functioning of Radio Transmitter BC-684-A	7
25	Functioning of Remote Control Unit RM-29-D	53
26	Functioning of Dynamotors DM-34-(*), DM-35-(*), DM-36-(*), DM-37-(*)	53
27	Functioning of Control Circuits	53
IV.	Maintenance.	
20	General Maintenance Information	71
- 20	Routing Check of Mounting	
36	Routing Check of Radio Receiver BC-683-A	73
37	Routine Check of Radio Transmitter BC-684-A	77
32	Routine Check of System Emergency Check of Receiver Output Volume and Circuit Alignment.	84
33	Emergency Check of Receiver Output Volume and Circuit Alignment	84
35	Emergency Alignment of Radio Transmitter BC-684-A	y:
36	Emergency Sources of Test Tones	X
37	Procision Alignment of Radio Receiver BC-683-A	90
36	Precision Alignment of Radio Transmitter BC-684-A	ď.
39	Location of Trouble in Radio Receiver BC-683-A	
40	Location of Trouble in Radio Transmitter BC-684-A	24
41	. Maintenance of Dynamotors	50
	Supplementary Data.	
43	Replacement of Parts	3:
4	Modifications During Manufacture	35
4	Color Codes on Components	43
4.	Table of Replaceable Pares	51

LIST OF ILLUSTRATIONS

	grouped according to components	
Fig.	Title P.	20
-	General:	V.
1	Radio Set SCR-608-A: Front View of Cabinet CH-74-A with Associated Components V	
2		u
3	Radio Set SCR-608-A: Over-all and Unit Dimensions	0
23		61
69	Radio Set SCR-608-A; System Schematic Diagram	20
		_
	Radio Receiver BC-683-A:	
6	Front View	2
7		3
8		4
9		5
11	Push-button Assembly, Right-stide Vicw	6
24		6
25		3
26		4
27a	Functional Diagram of Discrizzinator Vector Diagrams Showing Phase Relations in the Discriminator	6
27b, c, d	Vector Diagrams Showing Phase Relations in the Discriminator	
28		
29		
30		4
31		
43	Functional Diagram of the Heater Circuits .	
44	Among the Property Continue Plants	
45	Apparatus Location Diagram, Front view of Panel Apparatus Location Diagram, Left-side View	
46		
51 -	Applicates Location of Alignment and Tuning Controls Voltage Diagram 9	
57	Voltage Diagram	
58	Resistance Diagram	6
70	Resistance Diagram 11 Schematic Diagram Showing Modifications During Manufacture 19 Schematic Diagram 19 Schematic	1
71 72	Schematic Diagram Showing Modifications During Maonfacture 19 Schematic Diagram Without Front Panel 19	3 .
72	Wiring Diagram Without Front Panel 19	
	W. H. M.	
	Radio Transmitter BC-684-A;	
12	Front View With Crystal Compartment Open	
13	Assembly and Exploded View of Crystals	
14		
16	Interior View with Top Cover and Dynamotor Removed	
17		
18	Interior View with Business C. B	
33 -	Block Disgram	
34	Block Diagram 2 Functional Diagram of Oscillator and First R-f Amplifier 5 Functional Diagram of Mechanics and Process 5 Functional Diagram of Mechanics and Process 5 Structure 1 Str	3
35		3
36	Method of Modulation	
37	Method of Modulation Functional Diagram of Tripler, Doubler, Power Amplifier, and Antenna Coupling Circuits 6 Functional Diagram of Applications of Applica	
38		
10	Apparatus Location Diagram, Top View and Detail Infough Section A-A	

LIST OF HILLISTRATIONS - Continue

LIST OF ILLUSIKATIONS - Commune										
Title								P	age	
Apparatus Location Disease: Front View									80	
Apparatus Location Disgram, Bottom View		0	0			0			82	
Veltage Diagram					0				125	
Resistance Diagram									127	
Schematic Diagram Showing Modifications During Manufacture								- 1	197	
Schematic Diagram		-							199	
Wiring Diagram		-							201	
Artificial Antenna Used for Testing			*						205	
Oblique Front View									10	
Details									10	
Schematic Diagram		*	*						199	
Witing Diagram							į,		133	
B C III-is RM 30 D.										
Front View									23	
Interior View					-				23	
Schemitic and wiring anagram									203	
D DM 24 (#) DM 25 (#) DM 27 (#) DM 27 (#)										
Dynamotor DM-34-(*) or Dynamotor DM-36-(*)									24	
Dynamotor DM-34-(*) or Dynamotor DM-36-(*): Sub-base View .			-			-			24	
Dynamotor DM-35-(*) or Dynamotor DM-37-(*)									26	
Dynamotor DM-35-(*) or Dynamotor DM-37-(*): Sub-base View								2	4 66	
Schematic and Wiring Diagrams								0	66	
Departure DM-34-(*) or Departure DM-36-(*): Exploded View									67	
Demander DM-35-(*) or Denamotor DM-37-(*): Exploded View					-		-	*	68	
-,	1									
Adapter FT-384-(*):										
									101	
Rack View		-				-			101	
Application to Radio Receiver BC-683-A	Ċ					1			102	
Schematic and Wiring Diagram									103	
Capacitors and Resistors:										
									146	
Molded Mica Caracitors: Three-dot Color Code	•	-	-	- 1					150	
Molded Mica Capacitors: RMA Six-dot Color Code	1		1	1	0	0	0	1	151	
Molded Mica Capacitors: AWS Six-dot Color Code	1				0			1	152	
Molded Paper Capacitors: AWS Six-dot Color Code									153	
Fixed Resistors: RMA and AWS Color Codes					÷				154	
Artificial Antenna:										
For Testing Radio Transmitter BC-684-A									205	
100000000000000000000000000000000000000	Apparent Lordies Diagram, Frent View Apparent Lordies Diagram, Brown View Lordies of Adigment and Tunag Controls Lordies of Adigment and Tunag Controls Control Lordies of Adigment and Tunag Controls Control Lordies of Adigment and Tunag Controls Control Lordies of Engine Stewards Diagram Sciences Diagram Sciences Diagram Sciences Control Lordies Frent View Death Control Lordies Control Lordies Front View Death Control Lordies	Apparent Increio Diagram, Proce Ver Apparent Increio Diagram, Proce Ver Apparent Increio Diagram, Processor Ver Apparent Increio Diagram, Processor Ver Apparent Increio Diagram (Anna Processor Apparent Diagram Showing Medification Daring Manufacture Diagram Noveling Diagram (Anna Processor Anna Processor Processor Ordinary Manufacture Wining Diagram (Anna Processor Processor Processor Diagram (Anna Processor Proc	Apparents Location Diagram, From View Location of Augment and Tuning Controls Resistance Diagram Annabel Apparents Location Loca	Apparent Incurion Diagram, Frent Ver Apparent Diagram Restructor Diagram Restructor Diagram Archical Astronato Duagram Archical Astronato Duagram Archical Astronato Duagram Restructor Diagram Restructor Diag	Apparent Iocotion Diagrae, Prote Vew Apparent Iocotion Diagrae, Prote Vew Apparent Iocotion Diagrae, Protes Vew Apparent Iocotion Diagrae, Protes Vew Apparent Iocotion Diagrae, Protes Vew Residence Diagrae Residence Diagrae Residence Diagrae Residence Diagrae Residence Diagrae Residence Diagrae Residence Tolograe Re	Apparent Location Diagram, Freen Wew Apparents Location Diagram, Boston View Apparents Location Diagram Activation of Augment and Tuning Controls Resistance Diagram Activation of the Control o	Apparent Increion Diagram, Proor View Apparent Increion Diagram, Proor View Apparents Increion Diagram, Proor View Apparents Increion Diagram, Proor View Apparents Increion Diagram Control Diagram Resources Diagram Showing Modification Daring Manufaceure Wiring Diagram Archeld Antennat Douglam Trackeld, Antennat Douglam Archeld Antennat Diagram Wiring Diagram Diagram Wiring Diagram Diagram Wiring Diagram Diagram Wiring Diagram Diag	Apparents Incotion Diggrage, From View Apparents Incotion Diggrage, From View Apparents Incotion Diggrage, From View Apparents Incotion Diggrage, Promos View Actions of Adaptions and Training Controls Resistance Diggram Resistance Diggram Annothing American Diggram Annothing American Diggram Annothing American Used for Testing Monatting FT-371-7*); Oblique From View Deaths Northing American Diggram William Diggram Digg	Apparent Incurion Diagram, Frent Ver Apparent Diagram Control. Restoacte Diagram Showing Modification Daving Manufacture Wiring Diagram Manufact F1-237-(**): Charlest Apparent Diagram Manufact F1-237-(**): Children Frent Ver School Diagram Manufact F1-237-(**): Children Frent Ver School Diagram Wiring Diagram Diagram Wiring Diagram Diagram	Apparents Incotion Diggrac, From View Apparents Incotion Diggrac, From View 8 3 Apparents Incotion Diggrac, From View 8 3 Apparents Incotion Diggrac, From View 8 3 8 2 And

LIST OF TABLES AND CHARTS

Table	Title				P
I	List of Components and Other Items Required Channel and Crystal Frequencies Battery Cutrents Scienting of Dynamonors				
II	Channel and Crystal Frequencies				
Ш	Battery Currents				
IV	Salarman of December				
W	Selection of Dynamotors Motor Switch Readings (RECEIVER TUNE-OPERATE switch at OPERATE				
W	Meter Switch Readings (RECEIVER TUNE-OPERATE switch at RECEIVE	E) .	n in.		
VII	Canadian Champanistic	KIL	JNE)		1
VIII	Capacitor Characteristics Table of Replacable Page				1
IV	List of Manufactures				1
***	Table of Replaceable Parts List of Magnefacturers				1
Chart					
1	Equipment Required for Servicing of Radio Receiver BC-683-A				
TE	Servicing Procedure for Radio Receivers BC-683-A Nor Mounted in a Vehicle				33
TITE	Services Beauty for Radio Receivers BC-083-A Not Mounted in a Vehicle				1;

DESTRUCTION NOTICE

WHY To prevent the enemy from using or salvaging this equipment for his benefit.

WHEN When ordered by your commander, or when you are in immediate danger of capture.

HOW 1. Smash— Use sledges, axes, hand-axes, pick axes, hammers, crowbars, beavy tools, etc.

Cut— Use axes, hand-axes, machete, etc.

 Burn— Use gasoline, kerosene, oil, flame-throwers, incendiary grenades, etc.

Explosives—Use firearms, grenades, TNT, etc.
 Disposal— Bury in slit trenches, foxholes, other holes. Throw in streams.

Scatter.

Use anything immediately available for destruction of this equipment.

WHAT 1. Smash— Crystals, meter, plugs, tuning controls, tubes, capacitors, resistors, sockets, insulators, microphones, headsets, and relays.

Cut— Cords, wiring, and cables.

 Bend and/or Break— Arrenna sections panels mounting and nameplate.

 Burn— Circuit label, technical manual and all papers, cords, witing, cable, dynamotors, capacitors, resistors, and nameplate.

Bury and/or .
 Scatter— Any or all of the above pieces after breaking.

DESTROY EVERYTHING

SAFETY NOTICE

THIS EQUIPMENT USES DANGEROUSLY HIGH VOLTAGES. IT CAN KICK LIKE A MULE AND IS A DARN SIGHT MORE DANGEROUS. DON'T CHANGE VACUUM TUBES OR WORK IN THE EQUIPMENT WITH THE DYNAMOTOR RUNNING, EXCEPT AS SPECIFICALLY DIRECTED IN THIS MANUAL. BE CAREFUL, DON'T TAKE CHANCES.

SPECIAL NOTICE

Certain schematic and wiring diagrams in this manual include modifications during manufacture which are discussed in Paragraph 43. Not all these changes are included in the functional diagrams, Figs. 25 through 38. Any discrepancies between these two groups of figures are explained under appropriate heading in Paragraph 43. In case of such discrepancies, follow the circuit label on the equipment.

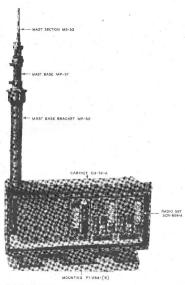


Fig. 1. Radio Set SCR-608-A: Front View of Cabinet CH-74-A with Associated Components

SECTION I. DESCRIPTION

 Purpose. Radio Sets SCR-608.A and SCR-628.A provide frequency-modulated radio relephone communication for anni-aircraft and anti-rank warning and control ness, for base stations a battalion command posts for fire central and fire direction ness, and for intra-bartalion communication. The radio sets may be installed and operated in combat while its such accommand.

and operated in combat webicles such as command cars, half-tracks, or any other authorized webicle. The sets are designed to operate whinin a temperature range of minus 40 degrees to plus 130 degrees Fahrenheit around the set. Don't operate this equipment for long periods of time if

rise too high. Watch this. 2. Performance Characteristics.

· C--t--

а.	ap	tem.			
	(1) (2)	Frequency Channel s	range27.0	to	38.9 megacyc 100 kilocyc

in enclosed spaces where the temperature may

(3) Number of channels available 120 (4) Channel numbers 270 to 389 inclusive (5) Number of preset channels 10

Note: Radio Sers SCR-608-A and SCR-628-A are equipped with dynamotors for operation from a 12-volt battery. If authorized, they may be operated from a 24-volt battery by substitution of the proper dynamotor. This is explained fully in Paragraph 10: Be sure you don't operate you set from a battery of the wrong voltage. You'll hom out tobes, dynamotor, and capacitors.

b. Radio Receiver BC-683-A.

71		1 microvolt
2)	Intermediate frequency	2.65 megscycles
3)	Band width	80 kilocycles
4)	Power output, speaker	2 watts
	Power output, headset	0,2 wars
	Call signal	Lamp
	Noise suppression	"Souelch"
6	Barrery design 12-volt supply	4 ampere

(9) Battery drain, 24-volt supply 2 amperes (see Note under Paragraph 2s.) NOTE: Throughout this manual an asterisk within

NOTE: Throughout this manual an asterisk within parentheses (*) indicates the applicable issue letter of interchangeable components of the equipment.

c. Radio Transmitter BC-684-A.

	Nominal power output	20 watts
(2)	Nominal frequency deviation	± 40 kilocycles
(3)	Crystal frequency range	375.000 to 40.277 kilocycles
	Frequency multiplication	. 72
(5)	Buttery drain, 12-volt suppl	y 20 amperes
(6)	Battery drain, 24-volt supp	y 12 amperes

(see Note under Paragraph 2s.)

3. General Features.

a. Arrangement and Weight of Major Conpowents. The general construction and arrangement of Radio Seas SCR-608-A and SCR-628-A are shown in Figs. 1 and 2. Over-all component and assembly dimensions are shown in Fig. 3. The radio sets consist of these combinations of major units:

(1) Radio Set SCR-608-A.

11) 10000 000 000 000 000	
Radio Receivers BC-683-A with	
12 -1 12 DM 24 (#) 70 II	

Mounting FT-237-(*) with Cord CO-278-A for connection to power supply 44 lbs.

Total weight (2) Radio Set SCR-628-A.

CO-278-A for connection to

1	Radio Receiver BC-683-A with
	12-volt Dynamotor DM-34-(*) 35 lbs
1	Radio Transmitter BC-684-A with
	12-volt Dynamotor DM-35-(*)67 lbs
1	Mounting FT-237-(*) with Cord

power supply _______44 lbs.

Total weight _____146 lbs.

b. Components of Radio Sets SCR-608-A and SCR-628-A. For a list of components, refer

c. Vacuum Tube Complement. Radio Receiver BC-683-A and Radio Transmitter BC-684-A include, and are issued with, a complete

181 lbs.

to Table I.

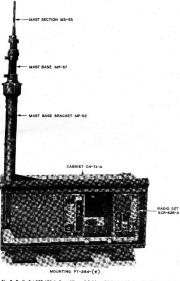


Fig. 2. Radio Set SCR-628-A: Front View of Cabinet CH-74-A with Associated Components

Table I. List of Components and Other Items Required

Quantity	Article
	Adapter Kit MC-471; includes:
	I Adapter plate; 15 in. x 35 in. x 13/8 in.
	1 Reinforced plate; 16 in. x 1½ in. x 1½ in.
	Necessary hardware
1	Antenna A-83-(*) (Phantom)
2	Battery Bracket BA-27 [for Remote Control Unit RM-29-(*)]; 1 in Use, 1 Running Spare
1	Box BX-40 [for 30 crystal Holders FT-241-(*)]; includes 30 Holders FT-241-(*)
	Bracket (extension for Mounting FT-285)
	Bracket (Cabinet CH-74-A)
	Cabinet CH-74-A
1	Case CS-76-(*) [for Remote Control Unit RM-29-(*)]
1	Chest CH-96 for Microphone T-17, Headset HS-30-(*),
	Box BX-40, spare tubes, technical manuals, etc.]
2	Clamp MC-423 (for Mast Section MS-51); 1 in Use, 1 Running Spare
2	Clamp MC-424 (for Mast Section MS-52); 1 in Use, 1 Running Spare
2	Cord CD-307-A [65-in. long, for Headset HS-30-(*)]; 1 in Use, 1 Running Spare
	Connector and Bondnut; Appleton Electric Co. No. 61001 and BL-50 respectively
	Connector and Bondaut; Appleton Electric Co. No. 61007 and BL-50 respectively
2	Cord CD-604 [for Headset HS-50-(*)]; 1 in Use, 1 Running Spare
1	Cord CD-689 (for Mast Base MP-48-A)

Cable WC-562 Cord CD-318-A (for Microphone T-45)

M 11-620

Cordage CO-212 Cordage CO-218 [for connecting slip ring to

Interphone Control Box BC-606-(*) in turret.]

Cover BG-96 (for radio set)

Cover BG-108 (for Mast Base MP-48-A)

Dynamotor DM-34-(*) [for Radio Receiver BC-683-(*)]; 12 volts; includes the following Running Space in page attached to dynamotor:

4-anush (L.v.) INCLUDES SPRINGS

4-BRUSH (H.V.) INCLUDES SPRINGS

Dynamotor DM-35-(*) [for Radio Transmitter BC-684-(*)]; 12 volts; includes the following Running Spare in BAG attached to dynamotor:

--PRIISH (L.V.) INCLUDES SPRING

4-BRUSH (H.V.) INCLUDES SPRING Frame FM-43 [for Cabinet CH-74-A or Mounting FT-237-(*)]

Hardware Kit: Miscellaneous items

Headser HS-30-(*): 1 in Use. 1 Running Spare

(When Headset HS-30-(*) is not available, Headset HS-18 or HS-23 may be issued.) Insulator IN-101

Insulance IN-104
Insulance IN-121 (11/-in-lone fee insulating appenda wire through metal partition.)

Insulator IN-121 (1½ in. long, for insulating antenna wire through metal partition.)

Interphone Control Box BC-606-(*); includes attached hardware as follows: screws, washers, clamps, clips, and books:

Table I. List of Components and Other Items Required-Continued

Sweams	Artide
1	Mast Base MP-48-A
	Mast Base Bracket MP-52 (Cabinet CH-74-A)
	Mast Base Bracker MP-5/1
	Mast Section MS-51
2	Mast Section MS-52; 1 in Use, 1 Running Spare
2	Mast Section MS-53; 1 in Use, 1 Running Spare
	Microphone T-17 (hand-type)
	Microphone T-15 (lip-type)
	(When Microphone T-17 or T-45 is not available, Microphone T-30 may be issued,
3	Microphone Cover M-367; 2 in Usc, 1 Running Spare
1	Mounting FT-237-(*); includes:
	1 Cord CO-278 (for power)
	1 set dust covers for receptacles
	All necessary mounting holes, nurs, and lock washers.
*	Mounting FT-284 (for Cabinet CH-74-A)
	Mounting FT-285 (for Cabinet CH-74-A); includes: mounting bolts, nuts, acrews, straps, and bracket.
	Mounting FT-326
2	Radio Receiver BC-683-(*); includes:
	10 Fuse FU-24; 1 in Use, 9 Konning Spare
	3 Lamp LM-63; 1 in Use, 2 Running Spare
	2 Tube JAN-6H6 (VT-90); 1 in Use, 1 Ronning Spare
	2 Tube JAN-6J5 (VT-94); 1 in Usc, 1 Running Space
	2 Tube JAN-6V6GT/G (VT-107-A); 1 in Usc. 1 Rumping Spare
	4 Tube JAN-6AC7/1852 (VT-112): 3 in Use, 1 Running Spare
	3 Tube JAN-12SG7 (VT-209); 2 in Use, 1 Running Space
	3 Tube JAN-6SL7GT (VT-229); 2 in Use, 1 Running Spage

Radio Transmitter BC-684-(*); includes: 120 Crystal Holder FT-241-(*) with Crystal (10 in Sockers, 80 in Drawer Compartmère, 30 in Box BX-100.

10 Fixe FU-64; 1 in Usc, 9 Running Spare 3 Lamp LM-38: 1 in Usc, 2 Running Spare

3 Lamp LM-38: 1 in Use, 2 Running Spare 11 Tube JAN-1619 (VT-164); 7 in Use, 4 Running Spare 2 Tube JAN-1624 (VT-165); 1 in Use, 1 Running Spare

Remote Control Unic RM-29-(*)

Roll BG-56-A (for antenna mast sections)

Technical Manual TM 11-620 for Radio Sets SCR-608-(*) and SCR 628-(*)

Wire W-128

The asserisk within parentheses (*) indicates that items so indicated are interrhogeable with shore marked with a different unifix lenter. An asterisk in the column headed Quantity indicates that the item is issued in quantities authorized, depending upon the type of installation to be made.

6SL7-GT

see of vacuum tubes in place. The tube complement of each component follows:

Circuit Designation	Function	Signal Corps Designation	Commercial Designation
VI	R-f amplifier	VT-112	6AC7
- V2	Modulator	VT-112	6AC7
V3	R-f oscillator	VT-94	615
V4	I f amplifier	VT-209	12SG7
V5	I-f amplifier	VT-209	12SG7
V6	Limiter	VT-112	6AC7
V7	Detector (dis- criminator)	VT-90	6H6
V8	Second a-f amplifier	VT-107-A	6V6-GT
V9	AVC and	VT-229	6SL7-GT

VT-229 amplifier and i-f oscillaror

(2) Radio Transmitter BC-684-A.

First a.f.

Circuit Designation	Function	Signal Corps Designation	Cammercia Designation
V101	First r-f amplifier	VT-164	1619
V102	Rectifier	VT-164	1619
V103	Doubler	VT-164	1619
V104	Power amplifier	VT-165	1624
V1.05	First a-f amplifier	VT-164	1619
V106	Second a-f	VT-164	1619
V107	Oscillator	VT-164	1619
V108	Tripler	VT-164	1619

d. Crystal Holders and Frequency Range. The receiver and transmitter operate between 27.0 and 38.9 megacycles; this range is divided into 120 channels of 100 kilocycles each. (See Table II) Channels 270 to 279, inclusive, have the same frequencies as channels 70 to 79, indusive, of the Armored Force [Radio Sets SCR-508-(*), SCR-528-(*), and SCR-538-(*)1. These channels may therefore be used for liaison

DUEDOSES.

A drawer in the transmitter provides storage for 80 Crestal Holders FT-241-A, one for each of 80 channel frequencies out of the 120 channels available. Each crystal holder contains a low-frequency quartz crystal (see Table II). and is marked with the channel number and output frequency.

e. General Spare Equipment.

(1) Receiver. Ten 15-ampere Fuses FU-24 (one in use, one in the spare holder, and eight in the attached bag) and three neon CALL SIGNAL lamps (one in use and two in the attached base) are furnished with each receiver.

(2) Transmitter, Ten 1/2-ampere Littelfuse Type 4AG fuses (one installed, one in the spare holder, and eight in the attached bag) and three pilot lamps (one installed and two in the at-

tached bag) are furnished with each transmitter. (3) Mounting. The mounting includes and is issued with one Cord CO-278-A and ten 75ampere Western Electric 66B fuses (one in use,

one in the spare holder, and eight in the attached bag). Also included are one set of receptacle dust covers and all necessary mounting bolts. nuts, and lock washers, together with two copies of Preliminary Instructions for Radio Sets SCR-608-A and SCR-628-A f. Code Designation of Component Parts.

Remember the method of numbering the component parts used in the various units of these radio sers. This will help you determine whether the part belongs in the receiver, transmitter, etc. Parts in the schematic and wiring diagrams, and usually on the equipment units also, are designated by a number preceded by one or more letters For example, C25, C115, L701, etc. Numbers for these units are shown in the column headed "Reference Number" in the Table of Replaceable Parts, Paragraph 45. Reference numbers from:

1 to 99 are used for parts in-Radio Receiver BC-683-A.

101 to 199 are used for parts in Radio Transmitter BC-684-A

401 to 499 are used for parts in Mounting FT-237-(*). 501 to 599 are used for parts in

Dynamoro: DM-45-(*) (transmitter, 12 volts). 601 to 699 are used for parts in Dynamotor DM-37-(*) (transmitter, 24 volts).

701 to 799 are used for parts in Dynamotor DM-34-(*) (receiver, 12 volts).

801 to 899 are used for parts in Dynamotor DM-36-(*) (receiver, 24 volts).

Crystal Frequency Output Frequency Crystal Frequency Output Frequency Crystal Frequency Output Frequency Out

	270	375.000	27.0	Channel	(bilocycles)	(megacycle	7)
	271	376.388	27.1	330	458.333	33.0	7
	272	377.777	27.1	331	459.722	33.1	
	273	379.166	27.2	332	461.111	33.2	
	274		27.3	333	462.500	33.3	
	275	380.555 381.944	27.4	334	463.888	33.4	
	276		27.5	335	465.277	33.5	
	277	383.333	27.6	336	466.666	33.6	
	278	384.722	27.7	337	468.055	33.7	
		386.111	27.8	338	469,444	33.8	
	279 280	387.500	27.9	339	470.833	33.9	
		388,888	28.0	340	472.222	34.0	
	281	390.277	28.1	341	473.611	34.1	
	282	391.666	28.2	342	475.000	34.2	
	283	393.055	28.3	343	476.388	34.3	
	284	394.444	28.4	344	477,777	34.4	
	285	395.833	28.5	345	479,166	34.5	
	286	397.222	28.6	346	480.555	34.6	
	287	398.611	28.7	347	481,944	34.7	
	288	400.000	28.8	348	483.333	34.8	
	289	401.388	28.9	349	484.722	34.9	
	290	A02.777	29.0	350	486,111	35.0	
	291	404.166	29.1	351	487,500	35.1	
	292	405.555	29.2	352	488,888	35.2	
	293	406.944	29.3	353	490,277	35.3	
	294	408.333	29.4	354	491.666	35.4	
	295	409.722	29.5	355	493.055	35.5	
	296	411.111	29.6	356	494,444	35.6	
	297	412.500	29.7	357	495.833	35.7	
	298	.413.888	29.8	358	497.222	35.8	
	299	415.277	29.9	359	498,611	35.9	
	300	416.666	30.0	360	500,000	36.0	
	301	418.055	30.1	361	501.388		
	302	419.444	30.2	362	502,777	36.1	
	303	420.833	30.3	363	504,166	36.2	
	304	422.222	30.4	364	505.555	36.3	
	305	423.611	30.5	365	506.944	36.4	
	306	425.000	30.6	366	508.333	36.5	
	307	426.388	30.7	367	509,722	36.6 36.7	
	308	427,777	30.8	368	511.111		
	309	429.166	30.9	369	512,500	36.8 36.9	
	310	430.555	31.0	370	513.888	37.0	
	311	431.944	31.1	371	515.277		
	312	433.333	31.2	372	516,666	37.1 37.2	
	313	434.722	31.3	373	518,055		
	314	436.111	31.4	374	519.444	37.3 37.4	
	315	437.500	31.5	375	520.833		
	316	438.888	31.6	376	522.222	37.5	
	317	440.277	31.7	377	523,611	37.6	
	318	441.666	31.8	378	525.000	37.7	
	319	443.055	31.9	379	526,388	37.8	
	320	444.444	32.0	380	527,777	37.9	
	321	445.833	32.1	381	529.166	38.0	
	322	147.222	32.2	382	530.555	38.1	
	323	448.611	32.3	383	531.944	38.2	
	324	450.000	32.4	384	533.333	38.3	
	325	451.388	32.5	385	534.722	38.4	
	326	452,777	32.6	386	536.111	38.5	
	327	454.166	32.7	387		38.6	
	328	455.555	32.8	388	537.500 538.888	38.7	
	329	456,944	32.9	389		38.8	
				 202	540.277	38.9	
•							7

PAR. 3

Channel

4. Associated Items.

a. Antenna System.

(1) Mars Base MP-86 or MP-75 is used and not be counted in such a very that the artissa will usernally be in a serviced position to the service of position or source color continuous color canning up through the consex. A meant attention is provided as the upon of the mars base. Another terminal is provided on the upon the mars base. Another terminal is provided on the control of the consex of the control control of the control control of the control control control of the control contro

(2) Three mast sections (MS-51, MS-52, MS-53) must be used, except that only two mast sections (MS-52, MS-53) are to be used with Mast Base Bracket MP-52. (Mast Base Bracket MP-52 is used in half-track installations and is mounted on the top of Cabinet CH-74-A at the left front corner.) Mast joints should be tightened securely by use of gas pliers or other suitable tools, and should be taped to prevent loss of mast sections. Put on two servings of friction tape as rightly as possible. The first serving should be applied counterclockwise, starting on the lower half of the joint and taping upwards from the left to the right. If available, Clamps MC-423 and MC-424 should be used instead of tape.

(3) Wire W-128 should be used brevene the mass base and the saw show not he length of the ris is less than 40 inches. Do not use more W128 than is necessary. This wire can be connected so either the rop or the borront terminal MP4-180, run pay be fed up through the center of MP4-8 after emoval of the center coastal and some conceivable. In the latter case the maximum permissible length of W-128 is 52 inches. The conceivable length of W-128 inches will be reduced understand the same of the length of the wind in the conceivable length of the length of the wind in the length of the wind in the length of the wind in the length of len

hole to protect the wire. Wire should be run and supported in such a way that it is protected from damage and will not be subject to chafing due to vibration.


(4) Coaxial cable, Cordage CO-282, should be used between the mast base and the set when the length of run is over 40 inches. The length of CO-282 must always be 7 feet (plus or minus 1 foot). If 7 feet is more than is needed, tape up the excess in a coil. The sheath of CO-282 must be grounded at both ends. When MP-37 is used, a short ground lead at the mast base is required to ground the sheath. When MP-48 is used, the coaxial cable fitting that joins CO-282 to the center coaxial cable connector of MP-48 provides for sheath grounding at the mast base. When passing CO-282 through the side of the vehicle. chests, etc., always insert an insulating bushing, such as IN-101 or IN-111, in the hole. Cable should be run and supported in such a way that it is protected from damage and will not be subject to chafing due to vibration.

(5) In installations using Mast Base Bracket MP-52 mounted on top of Cabinet CH-74-A, the lead from the mast base to the binding post on Mounting FT-237-(*) will be W-128 run inside of MP-52. Coaxial cable must not be used and will be removed from MP-48, if already installed.

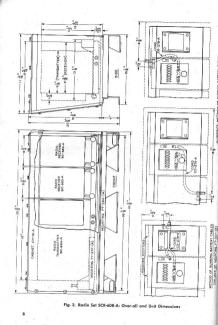(6) The antenna may be tied down when the vehicle is in motion in order to clear overhead power lines and obstructions. When the weblide is surfacency, the autenna may be tied down for reasons of conceilment. Remember, however, that range and signal threngs are related when the autenna is not down. For maximal threat the autenna to down to the control of the control of the control of the control of Rope RPs, an insulanor such as IN-86 or IN-87, and a short piece of flat mencal. Drill holes in each end of the metal piece, slip it over the threaded part of a mass section ferrule, and assemble the joint. The down to a convenient point on the vehicle with the insulator placed.

close to the antenna mast.

Note: The radiating system, which includes the antenna and ground circuit, must be of such



dimension that the circuis of the transmitter and the rectors can deal receiver on the enables and the rectors can be enabled to the enables and frequencies. Make the ground connection for the attention spring mitings the contact be seen the mounting and the frame of the vehicle where there is no different connection to the frame, or where the connection is smultiple, connect in the frame through short lengths of bridded opper strap 1/2-inch wide. Make certain that there is good electrical contact at both ends of the strap and allow sufficient slack to permit free movement of the unit in the shock mounting. If your ground lead is too short, vibration will soon break it.

b. Microphones and Headasts. One Headact B-Sto-(*). HS18, or HS23 and one Microphone T-17, T-30, or T-35 are required for each person using the equipment. Microphone T-30 is the curbon throat type, and Microphone T-33 is the magnetic hand type. Separare jacks are provided for use with either the carbon or the magnetic type of microphone.

. Butter Power Supply. You rail on strip gaze from either a 12-0: Advolb harburg power soure (dipending upon the transmitter and receive dynamours (minished); see Paragraph 10). The harvery used is the one already installed in your vehicle. You must have reglected harver opinish and charging rails to maketan estretally held tragge in the harry saude and opening the stage in the sharty saude and opening all units of the rails of th

35.1	Table	III. Battery Co	ırre	ents
		Bellery Dre	tin :	(Amperer)
lio Sel		(11-15 solts)		24-Vols Battery (22-30 vals/)
-608-A		28		16
1-628-A		24		14

24

SCR

a. Radio Sers SCR-608-A and SCR-628-A op-

5. Frequency Modulation.


erate on the principle of frequency modulation.

This system of communication, which is comparatively new, has one important advantage over the older amplitude modulation systems. Within the limit of its usuful range, trouble from static is greatly reduced. Of course, static is nor completely eliminated, her within the mornial 5- to 15-mile range it is much its woodstoom. It was not been stated in the state of the

b. Communication is effected by modulation of the carrier frequency. That is to say, the carrier frequency for its or say, the carrier frequency is made to vary with the londwest and pitch of the soice signal. Load speech cause: greater sudation of the carrier frequency, oil preech causes levy ariation. High-pitched consult cause the carrier frequency to vary more rapidly than do low-pitched sounds. The amplitude and power of the transmitted wave cremain substantially constant during modulation.

These characteristics are quite different from those of amplitude modulation such as used by Radio Sers SCR-245-(*) and SCR-299-(*) in which the amplitude and modulating frequency of the transmitted wave vary with the speech loudness and pitch, while the carrier frequency remains constant. Static noise is more closely related to amplitude modulation than it is to frequency modulation; therefore interference with signals is reduced through the use of frequencymodulation receiver circuits which suppress amplitude variations. This "discrimination" against received static noise gives you improved communication within your set's range. But at the end of your range and beyond it, frequency modulation cannot control static. Therefore, when static gets bad, you're either at the end of your range, or your receiver isn't getting much of a signal from the station you are trying to hear.

The methods employed for modulation and demodulation are explained in Paragraphs 23 and 24 of this technical manual.

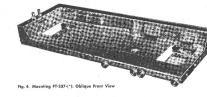

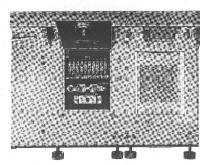


Fig. 5. Mounting FT-237-(*): Details

6. Mounting FT-237-(*).

- a. General. This mounting (Fig. 4), will hold
- Radio Ser SCR-608-A. One Radio Transmitter BC-684-A and two Radio Receivers BC-683-A.
- (2) Radio Ser SCR-628-A. One Radio Transmitter BC-684-A and one Radio Receiver BC-683-A. The transmitter must be installed in its allotted place at the left end of the mounting, but the

receiver may be installed in either of the two right-hand positions. Each unit is secured to the mounting by thumbscrew clamps and may be quickly removed without tools. Dust covers are provided for protection of the

unused receptacles. Screw the dust covers to the rear of the mounting when removed from the receptacles. (See Fig. 4.) A reversible nameplate bearing the words

BATTERY VOLTAGE 12 Von one side, and BATTERY VOLTAGE 24 Von the other side, is screwed to the front of the mounting near the right-hand end. (This place will normally show BATTERY VOLTAGE 12 V for Radio Sets SCR-608-A and SCR-608-A. Don't reverse the nameplate unless 24-volt operation is authorized.

b. Fastening of Mounting. Secure the mounting to the vehicle frame or other support by holts passed through two heavy hedplates on the mounting. There are four holt holes in each bed-plate.
Each bedelate supports the mounting through

two sets of rubber shock absorbers. In addition, two rubber snubbers on each bedplate prevent excessive movement of the equipment on the mounting. Electrical bonding straps are connected across each rubber shock absorber to provide a good ground connection to the bedplates.

6. Terminals. There are two terminals at the left end of the mounting. Connect the antenna system to the terminal designated TR for radio transmission and reception (Radio Sets SCR-608-A and SCR-628-A) or to the terminal designated REE for reception only. A ground terminal

is provided by a screw on the mounting. Later mountings have a ground binding post located near the antenna terminals for grounding the sheath of coaxial cable (Cordage CO-282).

A door in the base place of the mounting perminal series (TS401) (See Fig. 5.) One of the super battery faces is held in a clip on the under side of the door. The positive battery connection is mude at the right-hand end of five F401. The negative battery connection is made at a street on the under side of the mounting base place, which is marked x in Fig. 5. These methods the running the battery called, though the right end, front, or rear of Mounting FT-237-(4°), are illustrated in Fig.

d. Interconnections Between Units. All connections between the transmitter and receiver units and the mounting are made through multicontact plugs and receptacles which are automatically engaged when the units are inserted into their proper positions on the mounting. The wiring between receptacles is enclosed in a trough along the teat and left end of the mounting.

7. Radio Receiver BC-683-A.

a. Description of Functions. Radio Receiver BC-683-A is of the superheterodyne type and is intended for reception of frequency-modulated signals within the range of 27.0 to 38.9 megacycles. The receiver can deliver an output of approximately 2 watts to its self-contained loudspeaker or about 200 milliwatts to its headner circuits.

A front view of the receiver is shown in Fig. 6 and an oblique rear view is shown in Fig. 7.

The receiver is turned to ON or to OFF by the

The front panel contains ten push buttons by means of which any one of ten penadjusted channels may be selected immediately, much the same as any home "touch-tuning" radio. When a push button is fully depressed, it craches and is held in until another push button is partially depressed, at which time the first push button teleases and the selector mechanism is disconged. When the selector is disconaged (all push button).



Fig. 6. Radio Receiver BC-683-A: Front View

tons released), the receiver may be tuned by pushing the PUSH TO TUNE push button while rotating the TUNING control.

solding to FINING CORTON.

Two jacks, madeled PHONES, are provided for Two jacks, madeled PHONES, are provided for headest operation. The output of the receiver may be countered to the headest citizith by throw-ing the output TO PHONES SWIGH, to ON. Which the OUTPUT TO PHONES SWIGH to ON. When the OUTPUT TO PHONES SWIGH is at OFF, the headest circuit is disconnected from the tasio connected of the receiver. The Joudepselex, powers, will said be countered to the receiver output. To use the load-search of the seasons are swifted to the receiver output. To use the load-search output. The period of the receiver output. To use the load-search output. The period pe

A noise suppression or "squelch" circuit is switched on or off by the squelch switch. When the SQUELCH switch is at ON, the sensitivity of the receiver is adjusted by the SENSTIVITY control. When the squelch switch is at OFF, the receiver sensitivity is restored to maximum an cannot be adjusted.

The CALL SIGNAL lamp indicates that a sign is being received provided the SQUELCH switch is at on and the SENSITIVITY control has been acquisited to prevent operation of the squelch circu by received noise.

The TUNE-OPERATE switch starts a preset in termediate-frequency oscillator when at TUN to assist in the adjustment of the channel selection mechanism or to aid in tuning to weak signals. The intermediate-frequency oscillator is also used when aligning or servicing the receiver.

Active and spare fuses are contained in the two fuse receptacles designated FUSE and SPARE Antenna and ground binding and spare

Antenna and ground binding posts, designated A and G, are provided for resting purposes and special services. These connections are not used when the receiver is installed for operation.

To remove the receiver dust cover rum the fastener on the rear of the cover (see Fig. 7) one-fourth turn to the left and slide the cover of the rear of the receiver. Figure 8 is a view of the left-hand side of the receiver, and Fig. 9 shows the right-hand side of the receiver after shows the right-hand side of the receiver after shows the right-hand side of the receiver after shows the reverter push button assembly, viewed.

from the right side and the front respectively.

A Power Supply, Radio Reciver BC685-A is issued with Dynamono Dheft (*) for operation from a Double when the product of the power of the authorized, the receiver may be operated from the authorized the receiver may be operated from the authorized the power of the powe

8. Radio Transmitter BC-684-A.

a. Description of Functions. The transmitter operates in the frequency band from 27.0 or 38.9, megacycles and delivers a monital power output of 20 wasts to its antenna system. The carrier is frequency-modulated. A maximum frequency deviation of plus or minus 80 kilocycles (total frequency swing, 160 kilocycles) can be obfrequency swing, 160 kilocycles) can be ob-


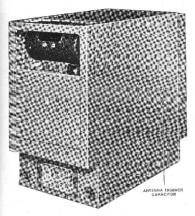


Fig. 7. Radio Receiver BC-683-A: Oblique Rear View

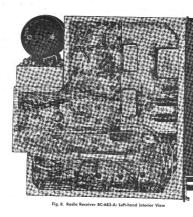

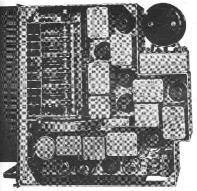


Fig. 9. Radio Receiver BC-683-A: Right-hand Interior View

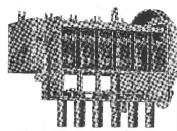


Fig. 10. Radio Receiver BC-683-A: Push-button Assembly, Right-side View

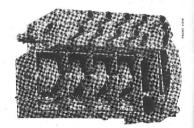


Fig. 11. Radia Receiver BC-683-A: Push-button Assembly, Front View



Fig. 12. Radio Transmitter BC-684-A: Front View with Crystal Compartment Open



Fig. 13. Radio Transmitter BC-684-A: Assembly and Expladed View of Crystals

tained; ordinarily, however, the frequency deviation is much less than this. Under most operating conditions the deviation, even on soice peaks, is less than plus or minus 40 kilocycles (total swing, 80 kilocycles).

A front oblique view of the transmitter is shown in Fig. 1 (large unit at the left). Figure 12 is a closer front view and Fig. 13 shows assembly and exploded views of typical crystals. A view of the tright-hand end of the transmitter showing the various controls and access openings is given in Fig. 14.

The front panel contains ten push buttons by means of which any of ren preadjusted transmitting channels may be immediately selected. This operates exactly like the push-button type of broadcast radio for the home. Like the receivers, you merely push one of several buttons on the front of the set to select the channel you want. Antenna and ground binding posts, designated A and G, are provided for test purposes, and they are not normally used when the transmitter is installed for operation. The RECEIVER TUNE-OPERATE switch makes it possible to use the transmitter as a source of known signal frequency for adjustment and testing of associated radio receivers. The transmitter filaments and relay circuits are energized by the ON-OFF switch and

transmission is started by operating the contreswitch on the operator's microphone. The pile lamp lights when the TRANSMITTER switch is a ON. Plug microphones of the carbon type, such as Microphone T-17 and Microphone T-30, into the CARB MIC Jack. Connect Microphone T-31, which is of the magnetic type, at the MANCHES

which is or the magnetic type, at the MAGNETI MIC jack.

Active and spare fuses are contained in th

Two fuse receptuales designated FUSE and SPARE
The panel meter may be connected in variou
citcuits by means of the TUNEANT CUR, which to
the panel and the six-position MTTEL SWITCH
(Fig. 14) to observe transmitter output and cit
cuit operating conditions. The meter is not call
beated in milliamperes or other standard unit of
measure as it is used only as an indicator of rela-

tive current flow.

The SIDETONE CONTROL Shown in Fig. 14 ad justs the volume of transmitted speech heard it the operator's headset. The ten screwdriver

operated controls are for antenna tuning adjustments.

Remove the top or bottom cover plates for access to the interior of the transmitter. Figure 15 is a view of the interior with the top cover plate removed, Figures 16 and 17 show the transmitter pushbutton assembly viewed from the left and from the right side respectively. A view of the interior with the bottom cover plate removed is shown in Fig. 18.

b. Power Supply. Radio Transmitter BC-684-A is furnished with a dynamotor, Dynamotor DM-35-(*), suitable for operation from a 12volr vehicle battery. If authorized, the transmitter may be operated from a 24-volt vehicle battery by merely substituting Dynamotor DM-37-(*) in place of Dynamotor DM-35-(*). This is the only change necessary, since a multicontact jack on the base of each dynamotor is wired to make the necessary circuit changes. The design of Dynamotors DM-35-(*) and DM-37-(*) is based on an average duty cycle of 5 minutes on and 15 minutes off at high temperatures. Don't operate the transmitter dynamotors continuously over long periods. You might burn out your dynamotor.

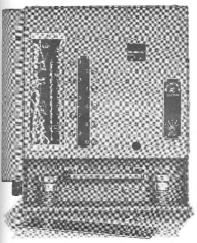


Fig. 14. Radio Transmitter BC-684-A: Right-hand End View with Cover Plate Removed

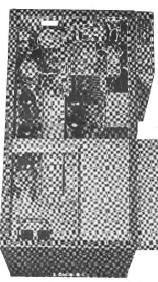


Fig. 15. Radio Transmitter BC-684-A: Interior View with Top Cover and Dynamotor Removed



- Landara (Alexandra)

Fig. 16. Radio Transmitter BC-684-A: Push-button Assembly, Left-side View

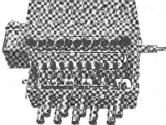


Fig. 17. Radio Transmitter BC-684-A: Push-button Assembly, Right-side View

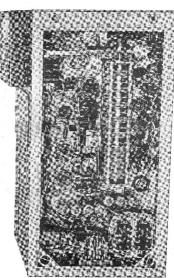


Fig. 18. Radio Transmitter BC-684-A: Interior View with Bottom Cover Removed



Fig. 19. Remate Control Unit RM-29-D: Front View

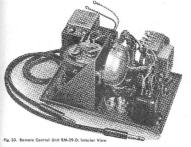




Fig. 21a. Dynamotor DM-34-(*) or Dynamotor DM-36-(*)



Fig. 21b. Dynamotor DM-34-(*) or Dynamotor DM-36-(*): Sub-base View

9. Remote Control Unit RM-29-D.

Note: The information regarding Remote Conroll Unit RAL-20-5 in this and subsequent paragraphs is given to assist radio operators in setting ap Radio Sers SCA-608-A and SKA-628-A for succes control operation. Do not regard this information as complete, but refer to Technical Minual TM 11-305, overring the remote control ain, for detailed information and instructions. Description of Functions, Remote Control.

Unit RM-29-D provides for remote control of the radio equipment and operates in conjunction with Telephone EB-8-(**) over a two-wire telephone line. A front view of the remote control unit is shown in Fig. 19, and an internal view with the loositing removed it shown in Fig. 20.

Two place-eminated corbs are provided to concorde emone coronal unit rothe alloid ranomitre and radio receiver. The two-wire relophone line from the removely located field Telphone IE-6, (**) terminates at brinding poss 1st and 1st on the remove corrol unit. Micrograft T-17 and a headset, when plugged into the reroce correl unit, are usure for transmission and reception of signals via the radio set, for moniing signals between the reliphone and the radio set, and for direct communication with Telephone IE-8-(**).

The three modes of operation are selected by the switch marked RADIO-THROUGH-THE EPHONE on the front of the remote control unit. Operation is as follows:

(1) Switch at RADIO. The radio set is controlled entirely by the operator stationed at the tenore control unit, with the switch at RADIO. The operator can transmit and receive signals via the radio set.

(2) Switch at THROUGH. The radios set is still under control of the operator at the emone control unit with the switch at THROUGH. However, this operator can no longer transmit via the radio set, but can only monitor all signal the radio set, but can only monitor all signal passing over the line, both from the radio receiver to any Telephone EE-8-(*) connected to the elephone line from the remote control unit, and from any elephone to the radio transmitter. (3) Switch at TELEPHONE. The remote control unit functions as a telephone very similar to Telephone EE-8-(*) with the switch at TELF-PHONE, and the operator can communicate with any telephone connected to the telephone line, but is disconnected from the radio equipment.

b. Power Supply. One Bartery BA-27 (4½ volrs) is mounted inside the remote control unit for operation of Microphone T-17. The current drain from this battery is from 50 to 95 milliamperes, depending on the position of the microphone.

Dynamotors DM-34-(*), DM-35-(*),
 DM-36-(*), DM-37-(*).

a. Dynamotor IDM-Hr²) and DM-Hr² (Each of these dynamotors provide short 2).

We had no breed symmetrees provide short 20 volts for operation of the receiver. The dynamotors are of similar appearance, and to volves are shown in Fig. 21a and Fig. 21b. The dynamotors are totally enclosed. Their amazores are dynamically balanced and are supported by two single-rack hall bearings. Both dynamotors are indust wound. The primary and secondary which we have been also also been also been also been also been also also been als

b. Dynamotors DM-35-(*) and DM-37-(*). Each of these dynamotors provides approximately 625 volts for operation of the transmitter. The dynamotors are of similar appearance; and two views are shown in Fig. 22a and Fig. 22b. Except for screened breathing vents in the end covers, the dynamotors are totally enclosed. The screened holes have been omitted in later dynamotors to reduce the entrance of dust or sand. This does not affect the power tating of the dynamotors. Their armatures are dynamically balanced and are supported by two single-race ball bearings. Both dynamotors are compound wound. The primary and secondary are wound in the same armature slots, but the two windings are brought out to separate commutators mounted on opposite ends of the armature shaft.

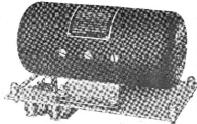


Fig. 22a. Dynamotor DM-35-(*) or Dynamotor DM-37-(*)

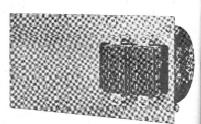


Fig. 22b. Dynamotor DM-35-(*) or Dynamotor DM-37-(*): Sub-base View

11. Cabinet CH-74-A. Cabinet CH-74-A is a protective housing for the radio equipment in installations where the equipment would otherwise be exposed to the elements (see Fig. 1). Cabiner CH-74-A is supported within the vehicle by Mounting FT-284-(*), Mounting FT-285-(*), or Frame FM-43, depending upon which vehicle is being used. Mounting FT-237-(*) is bolted in place in the cubinet. The top of the cabinet extends somewhat over the front of the radio equipment. A canvas cover assembly is provided for the front of the cabinet to completely enclose the racio equipment, if desired. The canvas cover may be folled back over the too of the cabiner, or it may be supported by a bracket which relescopes into the top of the cabiner. Except in an emergency, do not operate the eminment during hot weather with the canvas cover completely closed. Even in an emergency, do not operate either the transmitter or the receiver long enough for the equipment to over-

12. Mountings FT-286.(*) and FT-285.(*)
and FT-285.(*) and FT-285.(*)
and Frame FM-4. Mountings FT-284.(*) and
FT-285.(*) and Frame FM-15 are used to support Cabiner CH-74-A in vehicles where the
clother is used. The choice among these mounting depends upon the particular vehicle in which
the radio equipment is to be intulled. (See Paragraph 3-b.). Figure 1 aboves an installation using
Mounting FT-284.(*).

13. Mast Bases.

a. Mast Base MP-37. This mast base provides an insulated and flexible mounting for the anterna; it is rigidly mounted on the vehicle but includes a large helical spring for flexibility. Mast Section MS-53, the largest, screws into this base.

6. Mast Base MP-48. Another way to have a flexible antenna support is to use Mast Base MP-86. Use this base with a cuaxial transmission line such as Cordage CO-282. Two binding posts pennit use of a single wire lead (Wire W-128).
14. Mast Base Bracker MP-52. Mast Bose Brack-

14. Mast Base Bracker MP-52. Mast Base Bracker MP-52 serves to support an antenna and mast base about two feet above Cabinet CH-74-A. Clamp the mast base to the bracket cover plate and bring the antenna lead down through insulating guides into the cabinet for connection to the radio ecuipment. The bracket is fustmed to the cabinet by 12 obles. (See Fig. 1.)

15. Mast Sections. Mast Sections MS-51, MS-52, and MS-53 are used with these radio sets, except that only two mast sections (MS-52, MS-53) are to be used with Mast Base Bracket MP-52. (Mast Base Bracket MP-52 is used in half-track installations and is mounted on the top of Cabinet CH-74-A ar the left front corner.) The mast sections are made of high-tensile-strength flexible steel, Mast Section MS-51 is the top (and smallest) section. The others follow in numerical order. The lower end of each mast section is fitted with a servated (notched) shank and screw for engaging the threaded upper end of the next must section. Ends which are joined in assembling have enamel marks of the same color. The body of each section is enameled black and bears the type number at the lower end. The lower end of each mast section has an entering guide to aid assembly. Store the mast sections in Roll BG-56-A when not in use.

16. Cords and Cordage.

a. Cord CO-278-A. Cord CO-278-A is used to connect Mounting FT-237-(*) to the terminal box (battery) of the vehicle. It consists of 8 feet of Cordage CO-212 to which connection terminals have been soldered. The inner conductor is connected to the positive side of the battery and the outer conductor is grounded.

b. Cord CD-307-A. Cord CD-307-A in two lengths, 48 inches and 65 inches, extends the radius within which the crew of the vehicle may receive signals in their headsets. Plug PL-55 at one end of Cord CD-307-A plugs into the radio receiver. The headset plug is connected into Jack JK-26 at the other end of Cord CD-307-A.

c. Cord CD-318. Cord CD-318 is a 7-foot cord assembly for connection between the short cord supplied with Microphone T-30 and the radio equipment or a remote control box. The assembly includes Switch SW-141-E for control of the microphone current, provided with a neck strap for its support. The neck strap quickly detaches from the switch.

d. Cord CD-786. The auxiliary Cord CD-786 provides for making thirreen connections to a receiver or transmitter when not installed in the mounting. One such use is testing a receiver on a bench. The cord consists of

(1) A male plug for insertion in the socker

J401, J402, or J403 of Mounting FT-237-(*).
(2) A receptacle for connection to the plug PG1 of the receiver, or PG101 of the transmitter.

(3) Six feet of cordage containing conductors to connect corresponding numbers in these two plugs,

Terminals 1 and 2 of the plug are connected to corresponding numbers in the receptacle by 10gauge stranded wires. This constitutes the power connection and is suitable for carrying several amperes. A 22-gauge twisted, shielded pair of stranded wire is used for terminals 4 and 5. The other terminals used are numbers 7, 8, 9, 10, 19, 20, 21, 22, and 25.

e. Cordage CO-212. Cordage CO-212 is composed of two concentric conductors and is used in making Cord CO-278-A. Cordage CO-212 is supplied in bulk lengths and is used to replace damaged Cords CO-278-A or where a longer cord is needed. The cordage is installed so that the inner conductor is positive and the outer conductor is at ground potential.

f. Cordage CO-282. Cordage CO-282 is a flexible two-conductor corxial cordage intended for transmission of high-frequency currents. It is used in all misultantons of Radio Sets SCR. 608 A and SCR-628A where the distance beween the hinding poor on Monuting FT2-37. (*) and the mast base is more than 40 currents for the mast base is more than 40 currents. (*) Test effects of minust 100-31, ET of the state of the thin is needed, tape up the excess in a coll. Be sure no ground the shearth at the state of the s

SECTION II. INSTALLATION AND OPERATION

17. Initial Procedure.

L'impacting. Check the containers before queing them. Be careful when supaching or lamilieg the equipment. Avoid durange. Carelially inspect each unit for damage incurred in spinners and for loose parts. Remova all date owns and impere the interiors. For justifying them or brank out any dust or dirt. If an air grin justifying the sare that the air is for from water, in, and grit, avoid allyfulling of almanying air, appears are using. Manually these questions of the public broads and other controls on each of the public broads and other controls on each

b. Preparation for Installation.

- (1) Determine whether the vehicle battery is 12 or 24 volts and set the reversible voltage disignation plate on the front of the mounting, so that it properly describes the battery in use. (See Fig. 4.)
- (2) Open the hinged door on the mounting and check for the presence of a 75-ampere fuse in the circuit and in the spare fuse clip on the door. (See Fig. 5.)
- (3) Remove the unnecessary dust covers from the receptacles on the mounting and mount them in the positions provided at the back of the mounting.
- (4) Using Table IV, select the proper dynamotor for installation in each of the units.

Table IV. Selo	ction of Dynam	otors	
Unit in Which Dynamotor is Required	Dynamicson for Use With a Vehicle Battery of 77 Volts 24 Volts		
Receiver	DM-34-(*)	DM-36-(*)	
Transmirter	DM-35-(*)	DM-37-(*)	

(3) Remove the dust cover from the receiver, insert the proper dynamotor in place, and make certain that the dynamotor receptacles properly engage the plugs on the receiver. Tighten the four hold-down screws of the dynamotor and replace the receiver dust cover.

- (6) Remove the top cover plate from the transmitter. Take out the crystal storage drawer by pulling the drawer all the way out and lifting up the front end. Insert the proper dynamotor and make certain that the dynamotor receptacles properly engage the plugs on the transmitter. Tighten the four hold-down screen, using a long, thin strewdriver. Replace all parts that were removed.
- (7) Open the cover of the transmitter crystal storage drawer and remove the crystal compartment cover plate. Check the number of crystal holders in both places. Do not remove any crystals bound in the crystal compartment, since they will be used for subsequent installariton tests.

18. Installation.

a. Preparation of Vebicle. Detailed information on installation of the radio sets in various types of vehicles are to be found in the installation instructions for the particular type of vebicle concerned.

b. Installation of Equipment.

(1) Clerk the volved battery and the Steat per designation plant on the measuring. She have the contract areas around the monating both roles on the monating and one the monating and the curresponding and the volved on the whole on the adopter plant to insteat a good on the whole on the adopter plant to insteat a good properly from all contractions must be made at their points or the stalls set still not practice properly from all contractions must be made at their points or the stalls set still not practice properly form and contraction must be made at their points or the stalls of a still not practice properly must be provided by the stall to the monatting in stall taken them finally in place.

(2) Install Cord CO-278-A, which connects the mounting to the vehicle terminal box, in the mounting in a manner to prevent its damage by personnel (especially by their feet) and by movement of the mounting on its shock absorbers. Three sets of holes in the mounting sorbers.



- STICK TO WHAT'S RECOMMENDED

make possible the entrance of Cord CO-278-A from any one of three directions, as shown in Fig. 3. Use the holes which will result in the cleanest and shortest installation. The center conductor connects to the positive or ungrounded side of the terminal box. The outer conductor connects to the negative or grounded side of the terminal box. One end of the cord has smaller terminal lugs than the other end. Connect the smaller lugs to the mounting with the lug on the center conductor connecting to fuse F401 and the lug on the outer conductor connecting to the ground screw on the mounting (marked x in Fig. 5). Do not connect the hattery (terminal box) end of Cord CO-278-A without checking for accidental ground on the mounting, Check the polarity. (3) Antenna and ground connections differ

- somewhat for each type of vehicle, but make the installation in accordance with the general information contained in Paragraph 4s. The TR binding post on Mounting FT-237-(*) is used for the antenna connection when both transmission and reception are desired. Use the REC binding post for reception only.
- (4) Check the dynamotor installed in the transmitter to make sure it is of the proper type

for the vehicle buttery voltage. If not, replace the dynamotor with one of the proper voltage rating. Replace the cover plate. Place the transmirror on the mounting base with the push buttons toward the front of the mounting. Slide the transmitter to the left until the transmitter plug firmly engages the receptacle on the end of the mounting. The guides and tapered pins on the mounting properly align the transmitter as it is pushed into place. The two thumbscrews at the right-hand end of the transmitter may then he pressed down to engage the threaded holes in the mounting and firmly turned to the right to lock the transmitter in place.

- (5) Make certain that the dynamotor installed in each receiver is correct for the vehicle battery employed. If two receivers are to be used (Radio Set SCR-608-A), they may be placed in either of the two positions on the mounting (see Fig. 1). When only one receiver is used (Radio Set SCR-628-A), place it in the right-hand pusition to give yourself enough room to get at the adjustments on the right end of the transmitter (see Fig. 2). Slide the receiver toward the rear of the mounting until its plug engages with the receptacle. The tapered pins properly align the receiver to engage the receptacle. Engage the cupped edges of the thumbscrews on the mounting with the hold-down brackets. Then tighten the thumbscrews.
 - (6) To install Remote Control Unit RM-29-D follow the instructions provided with this unit

19. Preparation for Use.

a. Receiper.

- (1) Performance Check. Here's how to check receiver performance:
- (a) Turn the REC switch to ON and make certain that the receiver dynamotor starts. After about 15 seconds the vacuum tubes will be heated
- sufficiently for operation of the receiver. (b) Set the SPEAKER switch to ON, the

SQUELCH switch to OFF, and the OUTPUT TO PHONES switch to ON. Plug a Headset HS-30(°), HS-18, or HS-23 into one of the PHONE jacks

(r) Turn the VOLUME control all the way to the right. If it's on the air, you should hear poise, or a signal, from the loudspeaker and in the headset. The volume of sound may be varied by adjusting the VOLUME control. The CALL SIG-NAL lamp should light.

(d) Turn the SQUELCH switch to ON and observe the CALL SIGNAL lamp while turning the SENSITYTY control. It should be possible to extinguish the CALL SIGNAL lamp by turning the SENSITIVITY control to the left; the CALL SIGNAL lamp may not always light when no signal is being received. The noise, or signal, from the loudsneaker should cease whenever the CALL SIGNAL

lamp goes out.

(e) Turn the SQUELCH switch to OFF and listen to the noise while pressing the PUSH TO TUNE push button and operating the TUNING control. Noise or signals should be heard at any dial setting. An unmodulated signal (a station on the air but not talking) will sometimes cause a reduction of noise at one dial setting. The noise should increase as the dial is turned either side of such a station

(2) Receiver Antenna Tuning. In making the following adjustments, place the receiver in the vehicle and connect the antenna. Don't let the antenna touch anything and locate your vehide in the open, but only to the extent permitted by camouflage requirements.

(a) Install the receiver in the right-hand position on the mounting and set the ON-OFF switch to ON. The left-band position must be

(b) Set the SQUELCH switch to OFF and

the TUNE-OPERATE switch to OPERATE. (c) Set the SPEAKER switch to ON. (If you wish you may use a headset instead of the loudspeaker, in which case set the SPEAKER switch to OFF and the OUTPUT TO PHONES switch

to ox.) (d) Release the push buttons (see Paragraph 7)

(e) Manually tune the receiver to a froquency near the high-frequency end where there

is noise (not a signal). To manually tune the receiver hold in the PUSH TO TUNE button and

rotate the TUNING control. (f) Adjust the VOLUME control so that

poise is iner audible (g) Adjust the antenna trimmer (acces-

sible through porr hole on left side of receiver) for maximum noise in your headser or loudspeaker. Use a small insulated screwdriver or an insulated hexagonal socket wrench.

(b) Set the ON-OFF switch to OFF.

h. Transmitter. Here's how to check transmitter performance:

(1) Remove the antenna lead from the antenna post on the mounting and connect Anrenna A-83 between the TR binding post and the ground screw on the mounting.

(2) Connect either Microphone T-17 or T-33 to the transmitter.

(3) Throw the RECEIVER TUNE-OPERATE switch to OPERATE, and the TUNE-ANT CUR

(4) Turn the TRANSMITTER switch to ON and see that the pilot lamp lights.

(5) After about three seconds, depress a channel selector push button, and press the microphone switch. The transmitter dynamotor should start and the panel meter should show a deflection or movement. Release the microphone

(6) Reneat step (5) on all remaining chan-

(7) Throw the TUNE-ANT CUR switch to TUNE and note the meter reading for each position of the METER SWITCH. The readings should agree approximately with those given in Table V. (See Paragraph 31e(11) for a detailed discussion.)

(8) Start an associated receiver, plug a Headset HS-30-(*), HS-18, or HS-23 into the receiver PHONES iack, and throw the OUTPUT TO PHONES switch to OFF. Operate the microphone push burron and speak into the microphone. The

Table V. Meter Switch Readings*

1	2		4	4	
Doubler Grid	First R-f Grid	Rectifier Grid	Tripler Grid	Power Amplifer Grid	Total Plate
30	30	20	20	10	
20	25	25	25	15	65
	Grid 30	Grid Grid 30	Grid Grid Grid 30 30 20	Grid Grid Grid Grid 30 30 20 20	Grid Grid <th< td=""></th<>

speaker's voice should be heard in the headset. The headset volume may be adjusted to the de-

rise headset votume may be adjusted to the desired level by turning the SIDETONE control on the end of the transmitter. '

(9) Press in a channel selector push button

on the transmitter, and throw the transmitter RECEIVER TUNE-OPERATE switch to RECEIVER TUNE. The transmitter dynamotor should start when this latter switch is operated.

Caution: Don't zun the dynamotor for long periods. It may overheat.

(10) Manually tune the associated receiver to the transmitter channel frequency. Throw the

SPEAKER Switch to ON.

- (11) Operate the microphone switch and speak into the microphone. The speaker's voice should be heard in the receiver loudspeaker at a receiver dial setting within about one half a transmitter frequency. Recure that summittee frequency for the transmitter frequency for the frequency fore
 - c. Frequency Check on Receiver Dial.

(2) Throw the receiver TUNE-OPERATE

- (1) Throw the transmitter and the receiver ON-OFF switches to ON.
- switch to TUNE.

 (3) Throw the SPEAKER switch to ON and
- turn the VOLUME control to the right.

 (4) Throw the squelch switch to on and
- set the SENSITIVITY control to minimum.

 (5) Latch (depress) corresponding trans-
- mitter and receiver push buttons.

 (6) Set the transmitter RECEIVER TUNE

- OPERATE switch to RECEIVER TUNE. A beat note should be heard and the receiver dial setting should correspond to the transmitter frequency within one half a dial division.
- (7) If a beat note is not obtained hold in the PUSH TO TUNE button and rotate the dial slightly to obtain a beat note.
- slightly to obtain a beat note.

 (8) Repeat steps (5) through (7) for the remaining push buttons, noting all channels upon which note is not obtained.
- (9) Reset all receiver and/or transmitter push buttons for channels upon which a beat note is not obtained (see Paragraph 21).
- (10) If practical, check settings by establishing communication with another vehicle.
- d. System Test. Whenever practicable, check operation of the installation by establishing communication with another radio set.
- 20. Operation. This paragraph describes procedures for placing the receiver and transmitter in operation, assuming that the push button selectors are adjusted to select the ten desired channels. If it is necessary to change the channels selected by the push buttons of the receiver or transmitter, follow the procedures in Paragraph 21 before operating the equipment.
- a. Operation of the Receiver. You may operate the receiver with the SQUELCH switch at either ON or OFF. The squelch circuit controlled by the SQUELCH switch functions to disable the receiver output when no signal is being received; undestrable background noise is thus eliminated during "no-transmission" interpression?
 - (1) SQUELCH Switch at OFF. For loud-

peaker reception, throw the SPEAKER switch to 0% unit the VOLIME control to the extreme right, and throw the TUNE-OPERATE switch to 09-18/AM. For headser reception, plug the headser stora PHONES jack, throw the SPEAKER switch 00-097, turn the VOLUME control to the extreme left, set the TUNE-OPERATE switch to OPERATE, and the OUTPUT TO PHONES SWITCH TO PHONES TWITCH TO PHONES SWITCH TO ON.

To sure the receiver, throw the RXC solids to See, It takes about 15 seconds for the vacuum units carbods to bear. If the receiver controls are sife for loadspeaker operation, noise (or possibly) will be heard when the tubes have beard Regulares the volume with the VOLUME beard Regulares the volume with the VOLUME outsile. If the receiver controls are set for head-size and sufficient time has aligned to the receiver controls are set for head-size the volume of volume of the volume of volume of the volume of volume of the volume of the

Dependent publishment corresponding to the damed upon which reception is desired. The MINIST adjustment is supplementary to the scan publishment, whe selector having previously been set to the desired channels. However, the selector having previously been set to the desired channels. However, the manufacture of the selector having previously prepared by the selector having the strukeness of the selector having the TUNNED CORTOR of the Selector of the selecto

(2) SQUELCH Switch at ON. When the RRELEIS which at ON, the gain of the receiver me be varied by adjusting the assurativery conunit. (With the squares swith a row, the receiver operate at full gain and the assurativery consured in a function of the state of the

ceiving weak signals throw the SQUELCH switch to OFF and leave it there. Don't take a chance. If it isn't adjusted on the nose you may miss incoming calls.

For proper adjustment with the SQUELCIE which at ON, set the sensormery control as far to the cipit as possible for satisfactory operation. When receiving a weak signal, as deened by state into the thin tomorphism of the sensormery control carefully to the left until the CALL SORAL Bight jutt goes on as soon as the innoming signal goes off the air. The SENSTRYPT CONTROL STATE AS THE SENSOR STATE AS THE CONTROL STATE AS THE SENSOR STATE AS THE STATE AS THE

b. Operation of the Transmitter. Here's how to put the transmitter in operation:

(1) Set the TUNE-ANT CUR switch to ANT CUR. (Large differences between the meter readings as observed during operation of the transmitter on various channels and the readings noted when the transmitter was tuned up indicate trouble.)

(2) Start the transmitter by throwing the TRANSMITTER switch to ON. Allow about five seconds for the tube filaments to heat.

(3) Plug Microphone T-17 or T-30 into the CABB MIC jack, or Microphone T-33 into the MAGNETIC MIC jack.
Caution: Always make sure a CHANNEL SE-


LECTOR push button is depressed before pressing the microphone switch. Remember this. (4) Put the transmitter "on the air" by first latching the CHANNEL SELECTOR push button corresponding to the desired channel, and then

pressing the microphone switch.

(5) Turn the TRANSMITTER switch to OFF which finished sending if the stand-by period is likely to exceed three or four minutes. This will prolong tube life.

c. Operation of the Remote Control Unit. For information regarding operation of Remote Control Unit RM-29-D, refer to Technical Manual TM 11-308 furnished with this unit.

THESE PLACES ARE BAD FOR RADIO I

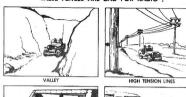







34

d. Operating Precautions.

(1) Transmission Conditions. The range at which your radio see will work depends on termin, interference, and radio noise. Under most conditions you should expect 5 to 7 miles except in valley, and under or close to underpasses, orehead seel bridges, and other obstructions which book not seen and other obstructions.

Dips, depressions, valleys, and low places are port for radio transmission and reception. The serounding higher terrain tends to absorb radio meray.

dicrgy.

Good places for sending and receiving are tills, elevations, and slight rises in ground. Flat ttrain is also good. But avoid high-tension lines, ovehead wires, and locations near electrical muchinery which create interference and may lot out even the best of reception. In general, your radio works best in the clear. You can concell your webide under trees or

camouflage, however. Trees and shrubbery won't our your range. But don't let your aerial rest on



FROM A VALLEY !

branches or shrubbery when sending or receiving. They will leak off your radio power. Here's another good operating tip to remem-

her: When you come to the fringe of your opteraning range—say 10 miles out—static and ignation noise may begin to bot out ory our reception. If you can 80 ir, try shutting off your vehicle's moot. You'll hear father. But your bactery must be well-charged as your radio draws heavily on it. Keep this in mind if you need a mile or two more range.

(2) Overheating. If the entire equipment is mounted in a tightly-enclosed space without enough ventilation, there is damper of overheating after extended periods of operation. Try to operate the equipment for as short intervals as practicable under such conditions.

(3) Receiver. Take care when using the squelch circuit and adjusting the SENSITUTY control. Improper use of these features will result in seriously reducing the range of the set. If there is any doubt whatever about use of the SQUELCH, turn it to OFF and reduce the receiver output



TM 11-62

volume sufficiently to prevent fatigue on long stand-by periods but not enough to prevent hearing a signal. Watch this. For weak signals and important incoming calls turn the SOUELCH to OFF and leave it at OFF. Don't take a chance.

- (4) Transmitter, Always press a CHANNEL SELECTOR push button before starting the dynamotor by operating the microphone control switch or by throwing the RECEIVER TUNE-OPERATE Switch to RECEIVER TUNE.
- Operation of the transmitter filaments for long periods without application of plate voltage tends to evaporate the active material from their surface and reduce their useful life. Therefore, the TRANSMITTER switch should be at OFF if the transmitter is not to be used for an extended period.
- (5) How to Use Your Microphone. These radio sets have been designed to work under noisy conditions such as in a tank or other noisy vehicle. To get best results, hold the microphone in a nearly vertical position with your lips just touching the surface. You don't have to shout: but it is necessary to make your voice go into the microphone at a higher level than the surrounding noise. Complete each word before starting the next and pur a slight emphasis on all sibilants. such as c, s, and z, and terminal letters, such as t and g. Speak slowly. Although the equipment has been designed to reduce as much as possible the effects of the mechanical noise, these instructions will help you obtain satisfactory communication with a remote station, especially under poor receiving conditions. Remember, don't mumble away from your mike. Sound off, directly into it.
- 21. Presetting Push Buttons. Presetting the push buttons simply means tuning the channels ahead of time to the required frequencies and locking the settings, so from there on tuning may be accomplished by merely depressing the necessary push buttons. This process is exactly that used in a home "push button" radio. It's fast and simple to operate.
 - a. Presetting the Transmitter. The presetting

procedure is divided into two parts: First-se ting the push buttons. Second-tuning the ar tenna circuit.

- (1) Setting the Push Buttons. The push bu tons may be set with the transmitter in the vehicl or removed. However, if the transmitter is p moved a suitable source of d-c power and Mounting FT-237-(*) or other means of cor necting the source of power to the transmitte are required.
 - (a) Set the ON-OFF switch to ON. Note Allow the transmitter to warm for five minute before setting the push buttons. Perform step
 - (b) through (k) while waiting. (b) Remove receivers. (If the receiver are to be preset also you can save time by leavin the right-hand receiver in position and setting it ON-OFF switch to ON.)
 - (c) Remove the crystal holders from th crystal compartment and put them in the crysta storage drawer.
 - (d) Select the required crystal holder for the new frequencies and insert them in th jacks of the crystal holder compartment in th prescribed order. (If no order is prescribed, in sert them by numerical order of channel numbe from top to bottom of the compartment). I desired, write the corresponding channel nurr bers on the white spaces provided opposite th push buttons.
 - (e) Replace the crystal holder compar
 - ment cover. (f) Release the push buttons by parriall
 - depressing one of them. (g) Turn the tuning capacitor contro (located below the handle on the right end of the transmitter; see Fig. 52), as far as it will g
 - toward the front of the transmitter. (h) Turn the locking screw (you ca reach this with a screwdriver through a small hole located above and to the left of the handle see Fig. 52), to the left until it binds slightly
 - then turn it to the right one-half turn. (i) Turn the tuning caracitor control al the way to the rear (minimum capacity).
 - (i) See the TUNE-ANT CUR switch to

- (k) Set the METER SWITCH to position 3.
 (l) Latch the push button for the frequency to be set. You will find it easier to set the highest frequency (highest channel number)
- (m) Then, if five minutes have clapsed since the ON-OFF switch was set to ON, start the dynamotor by setting the RECEIVER TUNE-OPER-ATE switch to RECEIVER TUNE.
- Caution: Do not operate the dynamotor any longer than necessary. Always stop the dynamotor when any pause is made in the procedure. Don't fet it overheat.
- (n) Slowly rum the runing capacitor control to the right until the panel meter indicates a peak value. Then continue to rotate the control for about one-eighth turn. If two or more peaks are obtained set the control for the highest one.
- (o) Set the METER SWITCH to position 1 and carefully readjust the tuning capacitor control for the peak.
- Caution: When the METER SWITCH is in position 1, the tuning capacitor adjustment is very critical and the control requires little or no change from the setting that was obtained for the highest peak in step (n).
- (p) Stop the transmitter by setting the RIXENUR TUNE-OPERATE switch to OPERATE.
- (q) Release the latched push button by slightly depressing an adjacent push button. Whice doing this step keep your finger on the
- betten being released to prevent it from snapping out with such force as to disturb the setting. (r) Repeat steps (k) through (c) for the remaining push buttons, preferably going such time force, a higher to the new lower for
- the remaining push burtons, preferably going each time from a higher to the next lower frequency channel.

 (s) After the last push burton is set, care-
- fully release it. (Use two fingers.)

 (t) Turn the runing capacitor control to
- the maximum front position and tighten the locking screw.

 (u) Check each push button setting by
- (u) Check each push button setting by tarning the METER SWITCH to position I, depressing the push button, setting the RECEIVER TUNE. OPERATE SWITCH TO RECEIVER TUNE, and moying

- the runing capacitor control slightly. If the setting is correct the meter reading should decrease when the runing capacitor control is moved slightly to carb side of that position to which it has been set by the push button. Repeat steps (f) through (f) for all settings that are not correct.
 - (2) Twining the Antenna Grazii. When runing the antenna criciti the Antenna A-83 to prevene tzaliarion. If Antenna A-83 is not available the transmitter must be in place in the vehicle, the mast antenna must not touch anything, and the vehicle should preferably be located well away from trees, trudes, and other large objects, but only to the extent permitted by camouflage requirements.
 - Caution: Never tune or operate the transmitter without the regular or a suitable artificial antenna (such as Antenna A-83) connected to the antenna post. Large currents developed in the antenna meter circuit with the antenna disconnected would burn out the thermorounle.
 - (a) Set the TUNE-ANT CUR switch to ANT CUR.

(c) Latch the push button for the fre-

(d) Start the dynamotor with the push-

- (b) Set the METER SWITCH to position 6. If the meter switch is not set to position 6 sufficient coupling may exist at some frequencies to cause the meter indicator to go off scale.
 - quency nearest 27 megacycles. (This is the best freepiency upon which to tune the amount for maximum output on the greatest number of frequencies. However, if it is definitely known that maximum output is desired on some particular freepiency the coupling can be adjusted on that freepiency, but the coupling should be adjusted for one frequency only.)
- to-talk switch on the microphone (RECEIVER TUNE-OPERATE switch at OPERATE).

 to

 (e) Adjust the antenna trimmer capacitor
 - (see Fig. 14) that corresponds to the latched push button for maximum indication on the panel meter.
 - (f) Adjust the antenna coupling control (see Fig. 14) for maximum indication on the panel meter.

- (g) Readjust the antenna trimmer capacitor that corresponds to the latched push button for maximum on the panel meter.
- (h) Latch remaining posh buttons one at a time and adjust the corresponding antenna trimmer capacitor for maximum on the panel meter. (Do not readjust the coupling control.) Caution: Do not run the dynamotor any more than necessary.
- (i) Make the frequency check outlined in Paragraph 19c.
- in Paragraph 19c.

 (j) Remove Antenna A-83 (if used) and connect the mast antenna.
- (k) If practical, check settings by establishing communication with another vehicle. (If desired, this check need not be made until after the receiver push buttons have been preset.)
- b. Presetting the Receiver. The presetting procedure may be divided into two parts: First setting the push buttons. Second—tuning the antenna circuit.
- (1) Setting the Pack Battons. The push houses may be see with the exertive in the white for removed. However, if the exertive its removed is available source of de-power and a Mountaing FF.257-4*) or other means of connecting the source of power is required. An unmodulated signal at the frequency or frequencies to which receiver is to be under must be available. The signal may be from either a remote transmitter or an associated transmitter. The changes necessary to adapt the procedure for use with a remote transmitter are devisions.
- (a) Set the transmitter and receiver otiore switches to sox. Note: Before setting the receiver pash buttons the transmitter should warm up for at least 5 minutes and the receiver at least 15 minutes. If you had left toe right-hand receiver in place, and it was warming while the reassmitter was being preset, it would not be necessary to wait long. However, you may perform steps (b) to (i) while warting.
- (b) Release the receiver push buttons by partially pressing any one of them.
- (c) Press the PUSH-TO-TUNE button and while holding it in, turn the TUNING control

- toward the high frequency end of the tuning dial until the word LOUK appears under the hairline. (d) Insert a screwdriver in the hole
- above the push buttons and turn the locking screw to the left until it binds slightly; then turn
- it right one-half turn:

 (c) Set the receiver controls as follows:

 (1) SPEAKER switch to ON. (You may
- use a headset instead of the loudspeaker if you wish.)
- (2) VOLUME control about two thirds to the right.
 - (3) SENSITIVITY control to minimum (to the left position).
 - (4) SQUELCH switch to ON.
 - (5) TUNE-OPERATE switch to TUNE.

 (f) If a second receiver is to be preset, place it in position and make the following ser-
- tings. (These settings are necessary to eliminate all probability of interference by this receiver.)

 (1) ON-OFF switch to ON. (Allow the
- receiver to wann up.)
 - (2) SPEAKER SWITCH to DEF.
 (3) SENSITIVITY control to minimum
- (4) TUNE-OPERATE switch to OPER-ATE.
- (5) Rotate the dial to its LOCK position.
 (6) SOUBLEH switch to ON.
- (7) OUTPUT TO PHONES switch to OFF.
 (g) Latch the transmitter push button for the frequency to be set. (The procedure is
- made easier if the lowest frequency is set first.)

 (h) Then if 15 minutes have elapsed since the ON-OFF switch on the receiver to be preset first was set to ON, turn the transmitter RECHYRE TURE-OFFRATE switch to RECHYRE
 - (i) Hold in the UNISTO-UNIS BUTION on the receiver to be present first and care the form of the receiver to be present first and care the TUNING control until the receiver is tuned to the retainminer frequency as determined by a best more and the setting of the dial which should correspond to the transmitter frequency. If the description of the dial does not correspond to the transmitter frequency it is probable that the receiver is tuned to a harmonic or that the transmitter is incorrectly preset.

TUNE.

(j) Hold in the PUSH-TO-TUNE button and latch the receiver push button corresponding to the transmitter frequency.

TM 11-620

(k) Slowly release the PUSH-TO-TUNE button while rotating the TUNING control just orough in either direction to maintain approxi-

mough in either direction to maintain approximately zero beat (very low pitched note). (I) Press the larched push button against

its sup two or three times. If the bear note is still very low-pirched depress an adjacent push button slightly and carefully ease the latched push button out. (Use two fineers.)

(m) If the setting is still correct turn the transmitter RECEIVER TUNE-OPERATE switch to OPERATE.

(n) Repeat steps (g) through (m) for the remaining push buttons, preferably each time going from a lower to a higher frequency.

Caution: Always stop the transmitter dynamotor during any pause in the procedure.

(o) After the last push button is ser,

(o) After the last push button is set, carefully release it (using two fingers) and rotate the dial to the LOCK position. (p) Lock the setting by tightening the locking screw. The screw should be firmly tightence but not enough to damage the push-button mechanism.

ence but not enough to damage the push-button mechanism.

(q) Make the frequency check outlined

in Paragraph 19c.

(r) Set the controls for operation as follows:

(1) TUNE-OPERATE switch to OPER-

ATE.
(2) Adjust the SENSITIVITY control so

the CALL SIGNAL lamp just goes out when no signal is being received. (See Paragraph 20a.) (s) If practical, check serrings by establishing communication with another vehicle.

(2) Taming the Antenna Circuit. You must unce the receiver ancenna circuit when the set is first installed in the vehicle. Ordinarily it will not require tuning again unless you make some change in the antenna. You can tune it before serting the push bustons if you wish. See Paragraph 194(2) for the prescribed method of tuning the ancenna circuit.

REMEMBER THESE NINE POINTS-

- Keep your antenna vertical. It sends and receives better that way. Be sure you use the right number of sections.
- Don't talk away from your mike. Speak directly into it. Sound off!
- If you want distance, head for the high spots. Watch out for steel bridges, valleys, dips, and low places. Your radio will work, but not so for.
- Conceal your vehicle but don't let your antenna rest against tree branches when sending or receiving. They will leak off your radio power.
- Watch out for the SQUELCH switch. For weak signals or important calls, turn it off and leave it off. Play it close to the vest.
- Don't let your radio sit out in the rain. Try to cover it. Rain may ruin radio equipment in a hurry.
- Dan't install your radio in a tightly inclosed space. Give it air.
- Don't run your dynamotors unnecessarily long. They get hot and, abused, may burn out.
- The operation of your set is basically simple. Practice it a few times and it will become second nature.

22. System Operation.

a. Radio Set SCR-608-A. Each radio set may mannin on any one of 10 preset channels and receive on any one of 20 preset channels. Twoway communication between two radio sets may be established by use of a single channel or by use of two channels.

The radio set may be used in either of two communications systems: (1) radio communications only, or (2) radio-plus-wire eleghance communication. In the first instance the radio equipment needs no auxiliary apparatus other than Microphone T-17, T-30, or T-33 and Heads 1850 (*), H81-36, or H82-3. In the second in sance Remote Centrol Unit RM-29-D is used to consect a remoterly located field Telephone EE-8 (*) to the radio equipment. Figure 23 stores a system block diagram.

ST STATION

(1) Radio Communication Only. When the two ends of the radio system (5 to 15 miles apart) have been placed in operating condition, it is necessary only to choose the channel frequency by pressing the proper channel selector button on the respective radio transmitter and radio receiver and press the microphone control switch when transmission is desired.

(2) Redis-Plas Wire Telephone Communication. In this case the visited pair from the removely located field Telephone EE-8-(*) is connected to the Li and Li binding posts of Remove Control Unit RM-2-D, and Plags PL-3 and PL-8s of the RECUPLE AND MICOPHONE CORD, respectively, are inserted into the receiver PhiONES and the transmitter CAB MC [265.]. The radio operator's Header 18-30-(*), HS-18, or HS-2-3 and Microphone T-17 or T-30-

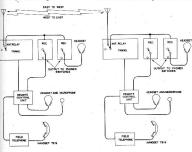


Fig. 23. Radio Set SCR-608-A: System Block Diagra

are plugged into the HEADSET and MICROPHONE jacks on Remote Control Unit RM-29-D. The radio operator may communicate with the field telephone operator by throwing the three-position key to TELEPHONE. The ringing generator and ringer are connected at all times and are operative regardless of the position of the threeposition key. When the key is at TELEPHONE, the radio equipment is disconnected from the relephone line and from the radio operator's headset and microphone. When the local operator wishes to communicate with the distant field operator, he may do so by theowing the threeposition key to RADIO and pressing the microphone push button while speaking. Operation of the key to the RADIO position disconnects the wire line from the radio equipment and from the local operator's brades and microphous When the three-position key is at "retorous the field steplone is connected to the radio receiver, and the local operator's microphone is rendered inoperator to the radio period of the rendered inoperator is microphone in rendered inoperator cannot be the rendered inoperator to the field stelephone operator cannot start the radio ransmitter when he desires so talk and it is necessary, therefore, for the local operator cannot can flower-sections and press and release his microphone push button as required by the row speakers.

b. Radio Set SCR-628-A. This radio set operares exactly like Radio Set SCR-608-A except that it is only possible to receive on 10 channels instead of 20, since there is only one receiver.

SECTION III. FUNCTIONING OF PARTS

Fig. 24. Radio Receiver BC-683-A: Block Diagram

23. Functioning of Radio Receiver BC-683-A.

a. General Circuits Used. A block diagram of Radio Receiver BC-683-A is shown in Fig. 24. The receiver employs the superheterodyne principle of operation. The high-frequency circuits include one scage of runed radio-frequency amplification (V1), a modulator (V2), and a radio-frequency oscillator (V3). The intermediate-frequency amplifier comprises two stages (V4 and V5), the second of which (V5) provides some limiting action on strong signals. The limiter stage (V6) not only functions as a limiter on moderate signals, but it also reduces amplitude modulation. The detector or discriminator (V7) is followed by two stages of audio-frequency amplification (V10' and V8). An intermediate-frequency oscillator (V10") permits thecking the receiver tuning. A single dual-purpose vacuum rube (V10) functions as the first audio stage (V10') and the intermediate-frequency oscillator (V10"). A second dual-purpose tube (V9) provides delayed automatic volume control (V9') and "squelch" (V9") which suppresses noise by disabling the receiver output when no signal is being received.


b. Schematic, Wiring, and Apparatus Location Diagrams. Complete schematic, wiring, and apparatus location diagrams are shown in Figs. 43, 44, 45, 46, 71, and 72. The system schematic. Fig. 69, shows (with some of the minor details omitted) the general arrangement of the control circuits; this drawing will be useful in studying the basic operation of these circuits.

c. R-f Amplifier, Modulator, and R-f Oscillator. Figure 25 is a functional diagram of the radio-frequency amplifier (V1), modulator (V2), and radio-frequency oscillator (V3) circuits.

The anrenna is coupled to the input of the radio-frequency amplifier stage by the antenna tuning unit, LCU1A. Current flowing through the primary winding LCU1A induces a voltage across the tuned secondary winding. The voltage thus developed is impressed between the grid and cathode of VI through by-pass capacitor C35. Decoupling resistor R37, along with this capacitor, prevents interstage coupling through the automatic-volume-control wiring. These by-pass capacitors are needed because the d-c grid return is made to the automatic-volume-control lead instead of to ground. The amplified radio-frequency voltage from V1 is impressed across the tuned primary winding of the interstage tuning unit, LCU2A, through by-pass capacitor C39. Trimmer capacitor C1.1 is used to compensate for variations in the antenna systems of various installations.

Current flowing through the tuned primary winding, L33, induces a voltage across the tuned secondary winding, L34, that is impressed between the grid and the cathode of the modulator tube V2, through by-pass capacitor C3. Capacitors C36 and C38 provide temperature compensation. The bias potential for V2 is determined by the cathode resistor, R3.

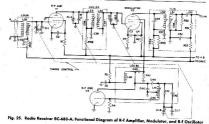The signal frequency, 27.0 to 38.9 megacycles, is converted to the intermediate fre-



quency, 2.65 megacycles, by hesetodyning being fed from the plate of V3 to the plus B lead.

ween the signal-frequency voltage and a few quency (2.56 megacytes higher) derived from the radio-frequency oscillator, V3, in the modulator (or mixes) usible. V1. The radio-frequency oscillator voltage is supplied to the suppresser grid of V2. Several modulation frequencies are available in the output of V2; but the first intermediate-frequency filter, FL1.A, setests the lower sideband and rejects the undesired frequencies. The radio-frequency oscillator employs a

The ratio-frequency oxillator employs a thuntefel Harriey circuit. The oxillator em bodies three negative coefficient capaciones (24, C44, and C46 in order to compensate for remperature changes and to enable the oxillator to maintain a high degree of frequency stability. Capacitors C41 and C42 are pudding expacitors. En and expactor C46 is a blocking expacitor. En experience (34 is a blocking expacitor). En experience (34 is a blocking explicit) freely discontinued to experience (34 is a blocking explicit). Freely consider the experience (34 is a blocking explicit) freely discontinued to the consideration of th

Radio-frequency voltage for the suppressor grid of V2 is derived from the place circuit of V3 through a coupling capacitor, C45. Resistor R5 and capacitor C5 prevent radio frequency beL42 is the oscillator plate choke inductor.

Gapacitors C1.2, C1.4, C1.6, and C1.8 are gapacitors C1.2, C1.4, C1.6, and C1.8 are four tuned circuits. Alignment of the circuits is assured by trimmer capacitors C1.1, C1.3, C1.5, and C1.7 and adjustable iron dust stugs in inductors L32, L33, L34, and L41.

d. 1-J. Amplifer and Limiter. The essential circuius of the intermediate-frequency magilier and limiter stages are shown in Fig. 26. Bandpass filters FLA, 26. and FLA suppress undestired frequencies conside an 80 kilocycle transdestired frequencies considerated and 80 kilocycle and 10 kilocycle transcript frequency considerated and 10 kilocycle cycles, the whole is considerated and 10 kilocycle aligned by the adjustment of the first side of the within earth call. Revisors R32, R62, and R72 in the three filters aid in securing the desired band-pass frequency characteristics.

Intermediate-frequency filter units FL1A, FL2A, FL3A, and FL4 are all provided with temperature compensation in the form of ceramic capacitors with negative temperature coefficients. See Paragraph 43b/10).

The arrangement used in later production is

shown in Fig. 26. Capacitors C53, C56, C63, C66, C73, C76, and C87 are all negative coefficient ceramic capacitors with a nominal capacitance of 60 micromicrofarads. In each case, the capacitor compensates for the positive temperature coferient of the coil across which it is connected.

The details of the filters used in earlier production are shown in Fig. 70. In this case, the resonating capacitance for the colls was secured by the use of two parallel capacitors: a 50-micromicrofarand moded mica unit and a 10-micromicrofarad ceramic unit. This laster unit was so constructed that is negative coefficient compensated for the positive coefficients of both its associated only and the mica canacitor.

The first intermediare-frequency amplifies (V4) is subject to delayed-automatic-volume-control action, its grid bias being supplied through decoupling resistors R51 and R53. The remaining potentials applied to the vacuum tube are such as to allow the tube to operate as a conventional amplifier.

The second intermediate-frequency amplifier (V5) differs from the first in the method of grid bias supply and in the relationships between the streen and plate operating potentials. The signal voltage developed across the secondary (L61) in FL2A is applied to the control grid of V5 through coupling capacitor C61. Grid bias is supplied through the decoupling resistor, R63. and the grid leak resistor, R61, from the negative high-voltage lead. The plate decoupling resistor, R74, is returned to the voltage divides at the common function of R21, R28, and R29 the plate voltage, under no-signal conditions, is approximately 60 volts. As a result of this low plate-supply voltage, the output of this stage is limited to a relatively low amplitude, even with a large input from the first intermediate-frequency stage. (Positive peaks are limited by plate saturation conditions; negative peaks are limited, or "clipped," by plate cutoff.)

The screen of V5 is connected to the plane return of the first intermediate-frequency stage (V4) through dropping resistor R8. Under the no-signal condition, the screen potential is approximately 90 volts. This results in a fairly high-


voltage gain on weak signals in spite of the low plate voltage. On strong signals, however, the increased screen current causes a relatively large voltage drop in resistor R8 (70,000 ohms); this reduces the screen potential, thereby reducing the gain. Consequently, the screen circuit serves

as a form of automatic gain control. On strong signals, rectified grid current flowing through R61 and R63 holds a negative charge on capacitor C61. The values of R61. R63, C61, and C63 are such that their time constant is high with respect to the intermediate frequency. As the input signal swings positive in each half cycle, grid current flowing through R61 charges C61. The charge is retained during the negative half cycle because of the high time constant. The negative bias from the rectified grid current flowing through R61 and R63 limits the positive swing on the grid of V5, thus limiting the peak excitation. The negative half-cycle swings are limited by the cutoff of the tube, which has been fixed by the plate voltage selected. The receiver is frequently required to operate with an extremely wide range of signal strengths impressed on the antenna, A peak limiter which is effective on moderate signal strengths tends to overload and fall off in output for very strong signals. To avoid this possibility the peak limiting action mentioned above is provided in the second intermediate-frequency stage to reduce the range over which the limiter stage (V6) is required to function.

The limiter stage (V6) uses two separate types of limiting action: (1) overload (peak) limiting, as just described, and (2) feedback limiting. The fixed grid bias obtained from the voltage drop across R24 is sufficiently large to give a degree of plate detection prior to overload, which is important in feedback limiting.

The overload method establishes a ceiline

which the output cannot exceed. On received voltages big enough to reach this ceiling this method keeps the output uniform and thus cuts off disturbances which would tend to increase the output irregularly. It does not, however, have any limiting effect on signals which do not reach this ceiling.

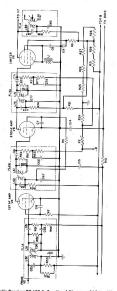

rig. 26. Kadio Receiver BC-083-A: Functional Diagram of I-f Amplifier and Limiter

The feedback method is based on the idea of balancing out a disturbance in the audio-fre quency range by means of an equal and opposite impulse. This is very effective on disturbances of an audio-frequency nature which are not large enough to be taken care of by the overload limiter. It is less effective but still helpful in the range between signals strong enough to start partial peak limiting and those of sufficient amplitude to cause complete peak limiting. The neestive feedback method operates by means of the coil L1 and the small parallel capacitor C8, presenting a low radio-frequency impedance and a high audio-frequency impedance. Coil L1 is connected in series with the cathode of V6 and lowfrequency amplitude variations in the plate circuit flow through this coil. The effect of this current flow is to develop a voltage across the coil between ground and the cathode. This voltage is therefore effectively applied across the grid-cathode circuit of the tube. The voltage developed across the coil and applied to the cathode opposes the effect of the audio-frequency variations in the grid circuit. When the grid voltage increases at an audio-frequency rate due to an increase in the undesired "ripple," the cathode bias will oppose the increase. When it decreases due to a decrease in the ripple, the bias will oppose the decrease. This action tends to smooth out the ripple. Amplitude variations at the carrier frequency will be by-passed by the capacitor C8 and will produce negligible feedback. At frequencies below the audible range the cathode choke L1 represents negligible impedance and does not affect the bias of the tube. For these slower changes the delayed automatic volume control is effective provided the signal is sufficiently large to overcome the delay bias. On the other hand, delayed automatic volume control does not respond to audio-frequency changes in amplitude, due to automatic-volume-control filter circuits.

In this discussion the noise producing disturbance has been considered as a single frequency having a more or less seeady value. In practice, however, the disturbance will probably consist of a number of varying frequencies of varying amplitudes. As long as the disturbing frequencies interact with the carrier to produce frequencies which are in the audio range (and the amplitude is not large enough to reach the ceiling of the peak limiting action), feedback caused by the coil will occur and smoothing of the ripple will be produced.

e. Discriminator. The purpose of the discriminator is to transform the received intermediate-frequency currents (which are frequencymodulated) into amplitude variations at audio frequencies. A functional diagram is shown in Fig. 27a.

The discriminator uses the phase shift between the primary and secondary windings of the intermediate-frequency transformer at the input of V7. Look at the diagram, Fig. 27a; the signal voltage across the primary I.82 is shown as E... The tapped secondary winding L81 is shown as two windings in series. The induced voltage across these two windings is shown as E. Voltage F. is developed across the capacitors C85 and C86 in series. Since C85 and C86 are very closely matched, their junction is at the same voltage as the midpoint of the secondary tuned circuit of FL4. The voltage across C85 is impressed on one diode (terminals 5 and 8 of V7). The return path is through capacitors C20.3 (which is paralleled by C82), ground, C83, C87 (which is paralleled by C88), and back to the junction of C85 and C86. The other half of the secondary voltage (developed across C86) is impressed on the other diode (terminals 3 and 4 of V7). The return is through C81. C20.3, ground, C83, C87, and back to the junction of C85 and C86.

In addition to these secondary voltages, the primary voltage is also impressed on these two dodes. The junction of C83 and C86 also connects directly to the plane of V6 (the limiter). The primary voltage is developed from this point or ground. Thus, E₁ is impressed across a criouit consisting of C85, there the diode (treminuls 5 and 8 of V7), then C103, to ground. The path through the other side of V7 is through C86, through terminals 3 and 4 of V7, through C81.

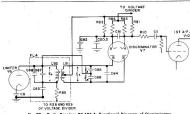


Fig. 27a. Radio Receiver BC-683-A: Functional Diagram of Discriminator


and Co.3, to ground. These are all ac paths. Since a diode is a tube that is unidirectional, that is, current flows in only one direction, these impressed alternating currents are rectified and this direct current flows through resistors R81 and R83 to the tap at the middle point of L81. This is merely a dc-return.

From this description, it is seen that each diode has impressed on it the primary voltage developed across C87 in series with one half the secondary voltage developed across C85 and C86.

secondary voltage developed across C85 and C86. The action of the discriminator depends upon the phase relations between these voltages. At resonant frequency (see Fig. 27b), E. and E., are each almost exactly 90 degrees out of phase with the primary voltage Ep. Consequently, Wro the total voltage across R83, and Ym the total voltage across R81, are equal in magnitude; since the rectified voltages appearing across the two resistors are opposite in sign, the resultant d-c voltage is zero. When the impressed signal is either above or below the resonant frequency. however (see Figs. 27c and 27d), the 90-degree phase relationship no longer holds, and the d-c voltages across R83 and R81 no longer balance out. The net result is that the discriminator output voltage follows the variations in frequency

of the incoming signal; the original frequency modulation is translated into amplitude modulation of the discriminator output voltage. This voltage is then impressed upon the grid of the first audio-frequency amplifier tube.

A somewhat more detailed explanation of the discriminator phase relations follows: Consider first the conditions when the output of the intermediate-frequency amplifier and limiter is at the resonant frequency to which both the primary and secondary circuits of FL4 are tuned. This is the case when the signal from the distant transmitter is at the mean or resting carrier frequency (i.e., no modulation is taking place). Voltage E. (see Fig. 27b) exists across primary winding L82; the primary current, In lags E, by very nearly 90 degrees; the resulting flux, 4, which links the secondary winding is exactly in phase with the current, so it also lags 90 degrees be hind the voltage, E,. Now this flux induces, ir secondary winding L81, an electromotive force which drives a current, L., through the secondary circuit. (Note that this electromotive force or inducing voltage is not Ex, the secondary voltage which would be measured by a voltmeter con nected across the secondary winding.) The in duced electromorive force lags the inducing flux by 90 degrees, it therefore lags the primary voidgage, Ba, by 100 degrees, as shown in Fig. 27th. As mentioned before, the secondary circuit is resourced exactly to the frequency of the signal, consequently, the impedance which is presented in the secondary of the signal consequently, the impedance with a presented sistence and the resulting current, IL, is a phase with the electromotive force, as indicated in Fig. 22th. Now consider value gas IL, III, and IL, Since, the consequence of the size of the size of the size of the tense of the size of the higher than resonance; the essential phase relations within the discriminator circuit are shown in Fig. 7ct. The relations of Fig. 14, 5, and the induced electromotive force in the secondary are as they were in the case of resonance. Now, are as they were in the case of resonance in the electromotive force is no longer provily resisters, it has an inductive component and consequently the secondary current lags the electromotive force. Consequently, and Fig. are related to Fig. as indicated in the figure and the voltages across SSS and RSS (Wg. and Yg. respectively) are no longer equal in magnitude; they do not caucal out.

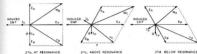

Figs. 27b, 27c, 27d. Radio Receiver BC-683-A: Vector Diagrams Showing Phase Relations in the Discriminator for Variations in Received Frequency

are 180 degrees out of phase with each other (remember that each is measured with respect to the mid-point of the two capacitors, or, what is the equivalent, the center tap of the secondary coil). It follows, then, that one of the two voleages must lead I_a by 90 degrees and the other must lag by 90 degrees, as indicated in Fig. 27h.

As explained previously, the total voltage impressed upon the left-shand diode of VT is made up of E_c (across CS7) in series with E_c (cross CS3); the total voltage impressed upon the right-shand diode is made up of E_c in series with E_c (across CS6). There total voltages are shown in Fig. 27b as $W_{\rm S}$ and $Y_{\rm S}$, respectively. It will be noticed that under the condition assumed (namely, the tuned circuits resonant at the frequency of the impressed signal), the absolute magnitudes, or lengths, of $W_{\rm S}$ and $Y_{\rm S}$ is the same.

Now assume that the signal frequency is

When the signal frequency is below resonance the phase relations are as shown in Fig. 27d. The series impedance of the secondary circuit is capacitive and accordingly the secondary current, L. leads the included electromotive force with the result shown. Notice that whereas in the preceding case (frequency above resonance) We, was greater than Y_n, in this case, Y_n, is greater.

than W_e.

The functions of the various units are described as follows: The tunned circuic comprising 122, CS₂, and CSS tunes the plate circuit of the limiter tube V6 to the intermediate frequency. The capacions CSS and CS in series complete the intermediate frequency circuit between plate and cathode. CSS provide temperature compennent of the complete complete compensation of the LS₂, is adjusted for exact resonance at the intermediate frequency for means of an into dust tunmediate frequency for means of an into dust tun-

ing slug. Plate voltage is applied to the limiter

the receiver.

tube, V6, through the decoupling resistor R85 from the junction of R28 and R29 on the voltage divider. L81 (the tapped secondary), which is coupled to L82, is resonated with capacitors C85, C86, and C84. (C84 is small and provides remperature compensation for the tuned circuit.) This secondary tuned circuit feeds through the double diode V7 to the load resistors R81 and R83 of the discriminator. Capacitor C81, connected across resistors R81 and R83, serves as an intermediate-frequency by-pass and also contributes somewhat to the shaping of the audiofrequency response characteristic. (R82 and R84 are discussed in connection with the automaticvolume-control and squelch circuits; they play no part in the discriminator action.)

One side of the discriminator load circuit is connected to ground through the ratio-frequency by-pass capacitor C82 and the audio-frequency by-pass capacitor C20.3 connected in parallel. The other side of the discriminator load circuit connects to the audio-frequency amplifier through series resistor R10 and coupling capacitor C11.

f. Voltage Divider. The voltage divider which is shown in the lower part of Fig. 29 serves three general functions:

 It constitutes a bleeder across the highvoltage direct current from the filter to discharge the capacitors when the power supply is not in use.

(2) It provides the reduced positive voltages required by the second intermediate-frequency amplifier, the limiter, the delayed-automatic-volume-control, and the squelch circuits.

(3) It provides negative grid bias for the radio-frequency and intermediate-frequency amplifiers as well as the limiter.

Current flowing from the positive hrush of the dynamotor must pass through audio- and radio-frequency choke coils and through R31, R29, R28, R27, R26, R25, R24, and P2 (provided the sQUILCLI SWICH is in the On position) to the negative brush of the dynamotor, It will be noted that R29 (13,000 ohms) and R31 (6,800 ohms) in series are shunted by R21 (30,000 ohms); in

is, electrically, the equivalent of a single resistor of 12,000 ohms. The combination of three resistors is used, rather than a single 12,000-ohm resistor, because of convenience in mounting and heat dissipation. The junction points between the resistors provide taps giving various voltages which are progressively less positive going from R31 to the junction point of R24 and R25, which point is grounded. (It is useful to bear in mind that neither terminal of the dynamotor is grounded.) The voltage becomes progressively more negative as we go from the ground point through R24 and P2. These two resistors are in the circuit which supplied bias to the grids of the first two amplifier tubes. R24 is fixed but P2 is adjustable. Since an increase in this resistance causes an increase in the voltage developed across it, an adjustment of P2 changes the negative bias applied to the first two amplifying tubes and thus changes the sensitivity of

g. A-f Amplifier. A functional diagram of the audio-frequency amplifier is shown in Fig. 28. The audio-frequency output of the discriminator is developed across the load (R81 and R83 in series) as described in Paragraph 23e. It is connected through the series resistor R10 and series capacitor C11 to the grid of vacuum tube V10'. The other side goes to ground through the radiofrequency by-pass capacitor C82, which has C20.3 shunted across it to reduce the audiofrequency impedance of this pure of the ground return. The circuit to the cathode of V10' is through C20.2. Capacitor C13 is shunted from the grid of V10' to ground and shapes the audiofrequency response curve. The resistor R10, in conjunction with C13, is a radio-frequency filter which among other things prevents intermediatefrequency currents from appearing on the grid of V10'. C11 is an audio-coupling capacitor. C26 is part of the intermediate-frequency oscillator circuit. Plate current flowing through cathode resistor R12 serves to bias the grid of V10' when the receiver is operated with the SQUELCH switch at OFF. Since R12 is not by-passed there will be a small amount of negative feedback in the first stage of this audio amplifier which causes some

reduction in the gain of V10'. (Negative feedback is incorporated in this circuit not primarily to reduce distortion but rather to reduce the gain of V10', the full amplification of which is not required for this application.) Grid return is completed through the grid leak R11 and the

squelch circuit resistor, R17, to one side of R12. The function of R17 is described in Paragraph

sufficient to extinguish the CALL SIGNAL lamp. At very high signal levels, which normally cause overloading, the lamp may be extinguished over part of the cycle due to that overload. This condition results in some distortion which is not usually objectionable.

The plate of V10' is connected through the coupling capacitor C21 to one side of the volume control PL, the wiper of this control being con-

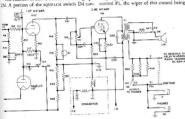


Fig. 28. Radio Receiver BC-683-A: Functional Diagram of A-f Amplifier

nexts the junction of R12 and R17 to ground when the SQUELCH switch is at OFF (removing any additional bias that might be developed scross R17 by the squelch circuit). The plate circuit of V10' connects through R18 and R19 to the B supply voltage, which is by-passed to ground by C16. The 2-megohm resistor R19 is shunted by the CALL SKINAL Jamp El, a neon lamp which has an impedance of about 200,000 ohms when normal lighting current is passing through it. When a signal is received the plate current flows and develops a voltage across R19 which increases up to the breakdown potential of the lamp. The lamp then breaks down, greatly reducing the impedance in series with the plate and lighting the lamp. At normal signal levels, the plate current variations of V10' are not

necred directly to the control grid of the second audio amplifier (beam power). Vs. The grid cricuit of V8 is completed from the other side of the volume courted JP1 to the nimus B lead. A high-capacity electrolytic capacitor, C23, pre-tunt audio frequency feedback across the cathole bias resistor R20, which contneres to the nimus B lead. Experience C19 is connecred across P1 to reduce further the higher audio frequencies, and to present the possibility of pickup of unwarned intermediate frequency current within might otherwise be amplified by V8.

The value of C21 as well as the value of C11 previously referred to were chosen to reduce the gain of the audio amplifier at frequencies below 400 cycles.

The screen grid supply for V8 is obtained

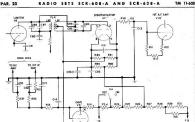


Fig. 29. Radio Receiver BC-683-A: Functional Diagram of Delayed-automatic-volume-control Circuit

through the series resistor R23 from the plate power-supply circuit. Capacitor C24 is the screen by-pass capacitor. The plate circuit of V8 is connected through the primary winding of the output transformer T1 to the power supply which is by-passed at this point by capacitor C25 to complete the return circuit to the minus B lead.

Capacitor C22, connected across the primary winding of the output transformer T1, serves to reduce the higher audio frequencies. It also serves to reduce transient voltages that may be developed in the plate circuit of V8 under overload conditions, which would tend to drive the grid voltage beyond cutoff. The bias for V8 is developed by plate current flowing through the cathode resistor R20. One of the secondary windings of the output transformer T1 may be connected through the speaker switch D3 to the loudspeaker, With switch D3 at OFF, resistor R30 is connected across this winding to prevent changes in headset level taking place when the loudspeaker is turned on and off, Resistor R30 also provides a constant load on the output of V8, further reducing effects of transient voltage. The remaining winding of the output trans-

52

former T1 connects through the parallel resistors R22 R32 and R33 to the OUTPUT TO PHONES switch D2. This switch connects in turn to the PHONES jacks It and I2. (A parallel connection is provided from these jacks to terminal 21 of the plug PG1.) The return circuit to this winding is completed through ground from I1 and J2. The series resistors R22, R32, and R33 in this circuit prevent the sidetone circuit (which is also connected to the PHONES jacks J1 and J2 through terminal 21 of PG1) from being shortcircuited by the disabling relay in the transmitter. The disabling relay in the associated transmitter functions during periods of transmission to short-circuit this latter winding of T1.

When background noise is high, particularly at the point of transmission, the operator should make sure to talk directly into his microphone in a loud tone of voice in order to override local noise. This will increase the volume of the receiver output considerably. Under actual service conditions the overloading due to loud talking does not reduce the degree of intelligibility very much, but the decreased volume caused by failure to talk loudly and directly into the microphone will often result in poor reception of your signals.

h. Delayok-automatic-volume-control Circ.
in: A functional diagram of the delayok-arcomatic-volume-control circuit is shown in Fig. 25As laredy menoisted it is very important that
the signals reaching the discriminance bed using
the signal starting the discriminance bed using
the signal provided in the second intromediate-frequency amplifier (''') and both
pack limiting and freedback limiting are povided in the limiter stage ('0'). In addition, the
amountar volume control is used on take care
of the variations below the analoctropensy.

of the variations below the analoctropensy of
the control of the control of the control
freeback limiter and no small for the overland

limiter. The detailed circuit arrangements will

be described following a discussion of the gen-

eral method by which the delayed-automaticvolume-control arrangement functions.

Since this is delayed automatic volume control, there must be a delay bias. This is provided by connecting the plate of the delayed-automaticvolume-control tube '99' so a point which is negside with respect to the cathode connection. This fixed bias prevents plate current from flowing in '99' when there is no output from the liniter V6. This fixed bias is the sum of the volt-

ages across PZ, R24, R25, and R26.
When ther is ourper from the limiter, the
immediator frequency voltage developed across
the immediator frequency voltage developed across
the impressed sarciss the plate and cathode of
VJ (as described in more detail larer). When
his infection in magnitude to overcome the
final bias on V9, plane current will flow in the
during part of each half cycle. This plate
ignores flows through a high resistor (R419)
shelt in the common grid reason of the radioflowprent; and first intermediate-frequency
and first intermediate-frequency
and first intermediate-frequency
and first intermediate-frequency
and first intermediate frequency
and first intermediate fre

it will be noted that the cathode circuit of V9' includes R81 and R83 which form the discrimnutes load resistor. Direct current flows from hose resistors due to discriminator action makes their junction negative with respect to the outer ends of the combination. Since the negative end of this developed voltage is toward the cathode of V9', this effect tends to reduce the delay bias materially as the signal strength increases.

In addition, intermediate-frequency current flowing through resistors R81 and R85 (from the plate of V6 through C95, C86, and must the plate of V6 through C95, C86, and control through C81, C82, and C81 (C82, and C83) causes an intermi-cincuit of L81, C82, and C8) causes an intermi-cincuit of L81, C82, and C8) causes an intermi-cincuit calculated of V97. This intermediate-frequency voltage is necrified when the peaks exceed the reduced delay bias. It will be noted that since distinctions divides equally through the discriminator load resistors, it does not affect the audio-frequency discriminator output.

The net result of these factors is that the automatic-volume-control tube, V9', is biased so that no plate current flows in it until the output of the limiter V6 exceeds a certain amplitude. When that occurs, this intermediate-frequency voltage (which is applied to both the discrimingtor and the automatic-volume-control tube) undergoes half-wave rectification in V9' and causes pulsating plate current in that tube. This plate current develops a d-c voltage in R14 which is effectively in series with the fixed bias applied to the radio-frequency and first intermediatefrequency amplifiers (V1 and V4). This rectified dic voltage component progressively increases the negative bias applied to V1 and V4. decreasing the amplification of these tubes, thus tending to maintain a constant output from the limiter

The circuit arrangements for providing the automatic-volume-coertor actions are described in more detail as follows (referring again to Fig. 9): The cathods of the automatic-volume-control diode V9' is connected through RR1 and RR2 in parallel with RS3 and RR4 or the inaction of £16 and RR7 on the voltage divider, then off the control of the control

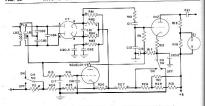


Fig. 30. Radio Receiver BC-683-A: Functional Diagram of Squelch Circuit

no signal is being received. This recrifier circuit is completed to ground through R14 (P2 when the SQUELGE which is a to N5), and R24. These resistors are also in the circuit which provides beas to the first radio-frequency and first incrementation for the receiver of the receiver of

The intermediate-frequency voltage developed across FL4 appears between the plate of V6 and ground. The plate of V6 is connected directly to the junction of C85 and C86. As far as relation to ground potential is concerned, this junction is equivalent to the midpoint of L81 which is connected directly to the cathode of V9'. Thus the cathode of V9' is connected effectively to the plate of V6. The return circuit from the plate of V9 is through C14. The intermediate-frequency voltage is thus impressed across the rectifier V9'. When the amplitude is sufficient, halfwave recrification occurs, which causes plate current to flow through R14. This causes the point (x) to become increasingly negative as the output of V6 increases. Since the potential of point (x) determines the bias applied to V1 and V4 (radio-frequency and first intermediate-frequency amplifiers), it is apparent that increasing the input to the receiver causes a decrease in the gain and thus tends to keep the output of V6 constant.

Currents reaching the discriminator cause d-c

voltagas acoss 181 and 183. Iy discriminate action. The jencino of there cave resistors is the negative and of each, 182 and 1812 are connected in such a way that, 831 and 1852 are effectively in gazilled with 1855 and 1863 are effectively in gazilled with 1855 and 1864 for this application, and the negative cod of the voltage developed across this combination is commercial to the earlier control of VP. This voltage is not large enough to overcome the fiscal base but reduces it materially concerned to the earlier control of the voltage of the VP. This voltage is not large enough to overcome the fiscal base but reduces it materially enough the voltage of the voltage in the voltage enough to overcome the fiscal base but reduces it materially interest artificial to the voltage of the voltage of the voltage in the voltage enough to overcome the fiscal base to the voltage in the voltage of the voltage in the voltage enough to the voltage of t

The grid bias lead for VI and VI is supplied through reison SIA with capacitors GI4 and GI5 connected to ground at its two eachs to prevent radio and audio-frequenty feedback to the grid of these tubes. VI and V4 also have in-80 years of the grid and the control of the grid of these tubes. VI and V4 also have in-80 years of the grid and the control of the second of the grid and the code has an individual radio-frequency by-pass capacitor connected from the grid end of its filter session to ground.

 Squelch Circuit. A functional diagram of the squelch circuit is shown in Fig. 30.

The squelch circuit is designed to disable the receiver output when the desired carrier is not received. In this manner, hiss and undesirable hadgeound noise (normally present under a nosignal condition) are eliminated in the "nomanushison' interests, in noder in accomplishin accomplishin

The operation of the squelch circuit is accomplished by having plate current flow in the squelch tube V9" when no carrier is being received. This plate current in V9" flowing through resistor (R17) produces a d-c voltage which is applied as negative bias to the first audio-frequency amplifier V10'. This bias is sufficient to prevent any signal transmission beyond that point. Thus there is no receiver output. When carrier voltage is received, the current flowing through resistors R81 and R83 from discriminator action sets up a d-c potential which is uselied to the grid of the squelch tube V9" to prevent the flow of plate current. Thus the bias caused by that plate current is removed from the grid of V10' and the audio amplifier operates normally. The following discussion shows in more detail how this is accomplished:

When there is no input to the discriminator, no signal voltage will be built up across either R81 or R83. With no signal voltage being rereized noise voltage is developed across R81 and R83. If the SOURLCH switch is at ON, the amount of noise voltage is adjustable by means of P2, and the audio-frequency amplifier V10' (Fig. 30) is then biased beyond cutoff by reason of the current (from the plate circuit of the squelch tube V9") flowing through R17. The CALL SIGNAL light is then extinguished since no outrent flows in the plate circuit of V10'. It will be observed that the control grid of the squelch tube is positive with respect to the cathode (grid current flow is limited by R15 and R16). The cathode is connected to the junction of R25 and

R26 while the grid is eventually returned to the junction of R26 and R27. This return path is through resistors R15 and R16, then through R81 and R82 in parallel with R83 and R84, to the voltage divider. Also the plate is returned through R17 and the switch D4 (at ON) to the junction of R27 and R28 which is positive with respect to both the cathode and the grid. Therefore, plate current flows in the squelch tube V9" and through resistor R17 to produce a voltage drop through R17. The negative end of this voltage drop is at the junction with R11 and thus applies negative bias through R11 to the grid of the first audio-frequency amplifier V10'. This voltage is sufficient to bias V10' below cutoff; hence, no plate current flows and the amplifier is "disabled." The by-pass capacitors C17 and C18 are connected to ground from either side of R16, to prevent intermediate-frequency or audiofrequency currents from flowing through R15 and R16 and actuating the squelch tube, since operation of this circuit is controlled mainly by the d-c component of the rectified input signal. Caracitor C12 serves to filter the plate circuit of V9" in a similar way. Capacitor C20.2 provides an audio-frequency return path to ground from the cathode circuit of the first audio-frequency stage.

When a signal is being received, a voltage of intermediate frequency is developed across the capped secondary L81 of filter unit FL4. This is applied to the two diodes of the discriminator V7. In one case a resulting electron flow occurs from the cathode (4) to the plate (3), through L81 (upper winding), R81, and back to the carbode. The other circuit is from the cathode (8) to the plate (5), through L81 (lower winding), R83, and back to the cathode. The voltages built up across R83 and R81 are such that the negative reminal of each is at the junction of the two resistors. For bias purposes, these two voltages are effectively connected in parallel by connecting two high resistors, R84 and R82, from the positive reminals of R81 and R83. The other ends of both R82 and R84 are then connecred to the junction of R26 and R27 on the voltage divider.

The negative end of this potential effectively

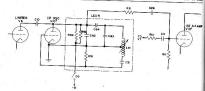


Fig. 31. Radio Receiver BC-683-A: Functional Diagram of I-f Oscillator

developed across RSi and RSi in parallel is applied shrough resiscon RSi) and RSi in the prior of the speech table V9°. It will be roosed white his potential is in opposition to the grid hiss (the voltage drop across RSi and RZT) which is a root of the root of the root of the is at Os. When no input cases (and RZT) which is at Os. When no input cases, the voltage developed across resiston RSI and RSi is sufficition to extend the root of the root of the case of the root of the root of the root of speech is eliminated. Thus the effect of the speech is eliminated.

The sensitivity control is described as part of the voltage divider. It regulates the radiofrequency gain of the receiver to make it as high as possible withour providing enough average noise voltage to "trip" the squelch tube.

j. I-f Oscillator. A functional diagram of the intermediate-frequency oscillator is shown in Fig. 31.

The intermediate frequency oscillator employs a Hartley circuit which is quite similar to the radio-frequency oscillator of the receiver. Coil 191 is adjustable to permit tuning to 2.65 megacyles. Capacitor C93 provides the bulk of the tuning capacitance. Capacitor C92 provides temperature compensation and C94 is a blocking the control of the contro

capacitor. Capacitor C91 provides feedback and resistor R91 provides grid bias. The intermediate-frequency oscillator operates

as an autodyne electrone. Some intermeditar for questy energy from limeter V6 is impressed upon the plare of the cosilinor through a small coupling capacities. C10. This energy modulars the cosilinor, and the audio-frequency heat most produced is passed on the first audio-frequency amplifier through R6 and C26. C26 is a coupling capacities. R6 persons a short circuit of the sudio amplifier. The coupling capacities of the sudio amplifier. The coupling capacities from appearing on the plate of the limiter. The oscillator is controlled by the TUNE-OPERATE switch, D5, which supplies plate voltage on Vigoforcing the load supplies plate voltage on Vigoforcing the load seatons R92 and R93.

k. Vacuum Tube Heater Circuits. A functional diagram of the vacuum tube heater circuits in the receiver is shown in Fig. 32.

These circuits are permanently grounded to the receiver chassis at three points, i.e., terminal 2 of VI, terminal 7 of VI, and terminal 2 of VI, terminal 1 of plug PC2 is grounded also. When the dynamous is installed in the receiver, the strap connections shown (which are included in the base of the dynamous) modify the circuit in the base of the dynamous? Insolity the circuit as required for operation at the battery voltage indicated on the dynamous? Thus, if 24-volt battery indicated on the dynamous? Thus, if 24-volt battery indicated on the dynamous? Thus, if 24-volt battery is the dynamous? Thus, if 24-volt battery is the control of the dynamous? Thus, if 24-volt battery is the control of the dynamous of the dynamous Thus, if 24-volt battery is the dynamous Thu

tury operation with Dynamonor DM-56 (*) 18 seasond, 1901 of the dynamonor connected serminal 3 on plug FG2 to terminal 2; and the 2-bt with lareny is impressed across three parallel coins (of series latenters) to ground (*) 69, 77 (v), and 37), (*) 69 and 470, a accomplish a similar function on the high-voltage end. L701 together with C25 constitutes an audio filter to remove the audio-frequency ripple which exists at the output of the dynamotor.

For Dynamotor DM-36-(*), the corresponding components in the 800 series perform similar functions.

24. Functioning of Radio Transmitter BC-684-A.

a. Block Diagram. A block diagram of the transmitter is shown in Fig. 33.

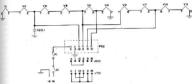


Fig. 32. Radio Receiver BC-683-A: Functional Diagram of the Heater Circuits

hattets to ground: (V2 and V1), (V6 and V8), (V10 and V3), (V7 and V9), (V4), and (V5). As mentioned in Paragraph 76, a 12-voit synammour must be used with a 12-voit battery and a 2-voit dynamoror with a 24-voit battery. The connections within a dynamotor are so arranged that the circuit is surromatically changed to adapt is to the battery voltage.

1. Dynamotor Filter Grouits. Filter Grouits to provided in both the low- and the high-solage sides of the dynamotors to overcome in-inference caused by the commutator as well as to provide the required degree of filtering. In the case of Dynamotor DM-3+6°, capacitors CO3 and C704 together with L702 constitute a swolage filter to prevent commencate interference from the low-voltage end. C704, C702, O8, and C706 together with L703 and L706 USs, and C706 together with L703 and L706 USs, and C706 together with L703 and L706 USs, and C706 together with L703 and L706 USs.

The gang-tuning control, operated by the push button selector, selects any one of ten presidenced crystals and connects it to the oscillator (V107). The oscillator output frequency (i, i) is amplified by the first radio-frequency amplifier (V101) and, along with the audio-frequency signals, is impressed upon a saturated iron-core modulation coil (uson cott).

to the control of the modulation coll is it in harmonics of the crystal frequency. After seeds forming by 100, the reason for which will be given laser, the twelfth harmonic of the crystal frequency (42. 5), the reason for which will be frequency (42. 5) upiles (1701a). The tripler couput (56. 6) excits a frequency doubler (1701a). The doubler couput (76. 6) excits a frequency doubler the proper of the control of the crystal frequency doubler couput (76. 6) drives the power amplifier (1704) in the carrier frequency (16-72 fs.). The proper one of the presumed and the couput (76. 5) and the carrier frequency doubler couput (76. 5).

L

di

in

rad



Fig. 33. Radio Transmitter BC-684-A: Block Diagram

tenna coupling circuits is selected by the gasgtuning control and connected to the antenna. Speech signals from a microphone associated with the transmitter are amplified by a two-stage audio-frequency amplifier (V105 and V106).

A small amount of audio output from V106 is caused to past frowly the headsic critici. This is called "sidetone." It enables the commander to hear all that goes out from his raidor transmitter and prevents confusion where two people have microphone for the same crammitting set. Also, when the operator's cert are covered by a headsic he does not have the command sentation of hearing himself talk unless sidetone is provided.

b. Schematic, Wiring, and Apparatus Location Diagrams. Complete schematic, wiring, and apparatus location diagrams are given in Figs. 47-50, 74, and 75.

c. Crystal Oscillator and First R-f Amplifier.
 A functional diagram of the crystal oscillator

(V107) and the first radio-frequency amplifier (V101) is shown in Fig. 34.

The frequency of the oscillator (V107) is controlled by any one of ten crystals in Holders FT-241-A placed in the crystal compartment. The crystal frequencies are in the range of 375

The crystal frequencies are in the range of 37 s of 50 kilosydes, as fixed accurately in Paugraph 34, Table II. In the functional diagram the important components of the oscillator are the crystal, Y101 to Y110, capacitor C131 from the curron just of V107 to ground, and the numed circuit C105-L102 in series with capacitar C101. The crystal is connected between the control grid and the junction of the tamed circuit the crystal control of the control grid and the junction of the tamed circuit the proper screens; provide the provide th

The oscillator operates as a modified "gridground" oscillator in which the crystal is above ground because of the impedance of capacitor C104. The phase of the current through this

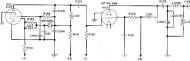


Fig. 34. Radio Transmitter BC-684-A: Functional Diagram of Oscillator and First R-f Oscillator

58

capacitor is such that some additional feedback is obtained, over that occurring in the usual gridgound circuit. This causes more rapid crystal suring and increases the output.

The parallel-connected inductor and capacitor in the plate circuit of the oscillator, L102 and C183, are proportioned to increase the excitation on the grid of V101 at the higher frequencies over that which would be obtained otherwise. Cipuisor C150 prevents the oscillator plate decoding the observation of the grid of V101.

Grid bias for the first radio-frequency amplifer V101 flows, through resistor R139. The treen of V101 is kept at radio-frequency ground potential by by-pass capacitor C101. The d-c supply for the screen is obtained from the 400audio signal (output of the second audio-frequency amplifier, V106).

The ratio-frequency input derived from the first ratio-frequency amplifier causes a current of about 0.3 ampere to flow through parallel-resonant circuit L100A, L104, C100, and C117. Its contract that the lower current than this. When the instantaneous ratio frequency current exceeds the stantanion value there is no appreciable increase of flux density and the inductance of the cold drops to a low value. Consequently very little voltage at lower lates of the contract of the

Between the saturation value and zero current, the coil has a high inductance, and a change

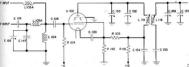


Fig. 35. Radio Transmitter BC-684-A: Functional Diagram of Modulator and Rectifier

role supply through resistor R103. The plate droit is fed through radio-frequency choke coil £191, and the load circuit (£103A, £104, and £106), is isolated by blocking capacitor £103.


d. Modulator and Rectifier. A functional diagram of the modulator and rectifier stages a tives in Fig. 35.

Two important functions are performed by adorce L104, which is a small nonlinear coil specially designed for use in this transmitter. He coil, openher with its associated unning induce and capacitors (L103A, C106, C147).

I functions as a modulating element which use the carrier frequency output of the first make frequency amplifier to be phase-modulated in conformity with amplitude variations of the

in current causes a relatively large change of flux density. Under this condition (that is, when the current passes through the magnetization range of the coil) there is a large change in the magnetic field; a high counter-voltage is induced across the coil. The current through L104, therefore, produces tharp voltage peaks each half cycle as the zadio frequency current wave passes through zero. The voltage peaks actemize in politany each half cycle and are evenly speed in politany each half cycle and are evenly speed on contain many harmonics of the original (crystal) frecuency.

Figure 36 shows how phase modulation may be produced by passing combined carrier and signal currents through L104. Figure 36a represents the current through L104 (crystal fre-

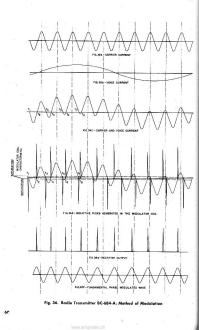

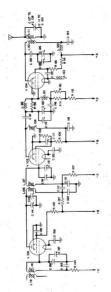


Fig. 37. Radio Transmitter BC-684-A: Functional Diagram of Tripler, Doubler, Power Amplifier, and Antenna Coupling Circuits

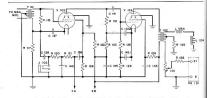


Fig. 38. Radio Transmitter BC-684-A: Functional Diagram of A-f Amplifier

quency in the absence of any modulating signal. An audio-frequency (sine wave) signal is shown in Fig. 36b. As shown in Fig. 55, the two currents pass through 1.104 to ground. The combined current is shown in Fig. 36c. Figure 36d shows the inductive voltage peaks generated in 1.104 (near zero instantaneous coil current) by the combined current.

The peaked voltage across J Juli 6 sectified by a based recifier, July 2a shown in Fig. 5. The fixed bias on the gaid of V102 is sufficient or eliminate all pocinions of the wave shown in Fig. 56c except the upper peaks. The rectified output of V102 is illustrated in Fig. 56c. The wave shown in Fig. 36c is representative of the fundamental component of the wave in Fig. 56c. The wave shown in Fig. 36c is representative of the fundamental component of the wave in Fig. 56c. The difference between the evenly spaced intervals on the "time said" and the points of "zero cut- enter" represents the amount by which modulate on has shifted the wave.

The wave in Fig. 36e contains a large number of harmonic frequencies, each of which is similarly phase modulated. A tuned filter (C152, C153, L119, L118, C156, and C157) suppresses all but the twelfth harmonic of the crystal frequency. This is passed on to the triplet stage of the transmitter.

e. Tripler, Doubler, Power Amplifier, and Antenna Coupling Circuits. A functional dia-

gram of the tripler (V108), doubler (V103), power amplifier (V104), and antenna coupling circuits is shown in Fig. 37.

The input to the tripler tube, the voltage across tuning capacitors C156 and C157, is at twelve times the crystal frequency, or one sixth of the output carrier frequency. Coupled antiresonant circuits (C113, C114, L106 and C115, C116, L107) in the plate circuit of V108 and the grid circuit of V103 select the thirty-sixth has monic of the crystal frequency and impress it upon the doubler stage, V103. The doubler output is tuned to the output carrier frequency by anti-resonant circuit L108, C119, C120, While capacitor C121 is included in the tuned circuit, it is of low reactance and is used only as a deblocking capacitor. The power amplifier, V10l, is coupled to the antenna by coupled circuit C125, C126, L110 and L111, C127-C136, L121-R158 is included in the grid lead of V104 to sup press high-frequency parasitic oscillations

f. A-f Amplifier and Microphone Circuits. The essential circuits of the audio-frequency amplifier and the microphone circuits are shown in Fig. 38.

In Fig. 38.

The first audio-frequency amplifier tube,
V105, may be excited by a microphone. This may
be a carbon-type microphone (cither Microphox
T-17 or T-30) connected to J102, or a magnetic

appe microphone (Microphone T-33) connected in 100. In circles case, pressing the which on the morphone energines the dynamotor celay winding (5102) and close its connects to start the transmitter dynamotor. The voltage from a magnificactive microphone is impressed across the pairury of input transformer T101. The second-specific production of the product of the p

Size the output of a cubos tepe microphone, mean step provided no care for this difference. A magnetic etype microphone, means tep provided no care for this difference. A magnetic etype microphone may be Pugged into juk JUI or a carebon-type microphone may be plugged mo juk JUI. The detailed unformity of excitation of V105 (in spine of differences in microphone curpor) is obtained by the voltage doubter action of cryatores C137 and C138 and microphone curpor (C137 and the advantage across C137, which is the excitation for the current in Octorior of the microphone current is obtained through a replic filter to (III). C101, C102, III (III), from the volticle but control (III) (III), C103, C103,

The output of V105 is coupled to the grid of V106 by capacitor C141 and resistors R151 and R125. R124 is a noise filter resistor for the plate of V105. Capacitor C145 serves as a ground renum for the plate circuits of V105 and V106.

Output transformer T102 has two series-conered secondary windings. One winding supples siderone to terminal 21 on plug PG101 through resistor R128. The sidetone volume is adjusted by varying the setting of potentionerer. P101. The second winding supplies modulating signals to the modulation coil, L104, through tailor trequency choice coil L1054.

g Metering Circuits. A single meter, M101 (Fig. 74), may be switched to any one of several dividuals in the transmitter by operation of switch D125. The panel switch D121 is used to connect the meter to D125 or to the thermocouple Tcl01 for indicating antenna current. The following six circuits may be checked by use of D125.

Switch Position

1 Doubler grid
2 First 1-f amplifier grid
3 Rectifier grid
4 Tripler grid
5 Power amplifier grid
6 Total plate and screen

25. Functioning of Remote Control Unit BM-39-D. A combined schematic and writing diagram for the remote control unit is given in Fig. 76. The association of this unit with Rullo See SCR-608-A is also shown in the detailed syrtem schematic diagram, Fig. 69, and is explained in Paragraph 27. For more detailed information on the functioning of the various components in Remote Control Unit RM-29-D, refer to Techical Manual TM 11-308 which covers this unit.


 Functioning of Dynamotors DM-34-(*), DM-35-(*), DM-36-(*), and DM-37-(*).
 Four types of dynamotor are used with Radio Sets SCR-608-A and SCR-628-A. They are:

Dynamotor DM-34-(*): Receiver (12 volts) Dynamotor DM-35-(*): Transmitter (12 volts) Dynamotor DM-36-(*): Transmitter (24 volts) Dynamotor DM-37-(*): Transmitter (24 volts)


Each dynamocor combines the functions of a low-olarge (120-oka of 24-okt) d. In conce with a high-voltage (200 volts for the recover; 600 works for the reasonism) of generator in a cone field winding, and one pair of hearing are one field winding, and one pair of hearing are regaried. The armanure is wound with two separate windings, each of which is connected our occurrent and swinging diagrams of the four dynamones are shown in Fig. 32, and 42. The parts numbers are given in Fig. 34. The pairs numbers are given in Fig. 34. The pairs numbers are given in Fig. 34. and 42. The parts numbers are given in Figs. 41. and 42. The parts numbers are given in Figs. 41. and 42. The parts numbers are given in Figs. 41. and 42. The parts numbers are given in Figs. 41. and 42. The parts numbers are given in Figs. 41. and 42. The parts numbers are given in Figs. 41. and 42. The parts numbers are given in Figs. 41. and 42. The parts numbers are given in Figs. 41. and 42. The parts numbers are given in Figs. 41. and 42. The parts numbers are given in Figs. 41. and 42. The parts numbers are given in Figs. 42. and 43. The parts numbers are given in Figs. 42. and 43. The parts numbers are given in Figs. 43. and 44. The parts numbers are given in Figs. 44. and 45. The parts numbers are given in Figs. 44. and 45. The parts numbers are given in Figs. 44. and 45. The parts numbers are given in Figs. 44. and 45. The parts numbers are given in Figs. 44. and 45. The parts numbers are given in Figs. 44. and 45. The parts numbers are given in Figs. 44. and 45. The parts numbers are given in Figs. 44. and 45. The parts numbers are given in Figs. 44. and 45. The parts numbers are given in Figs. 44. and 45. The parts numbers are given in Figs. 44. and 45. The parts numbers are given in Figs. 44. and 45. The parts numbers are given in Figs. 44. and 45. The parts numbers are given in Figs. 44. and 45. The parts numbers are given in Figs. 44. and 45. The parts numbers are given in Figs. 44. and 45. and 45. and 45. and 45. and 45. and 45. and 45

27. Functioning of Control Circuits.

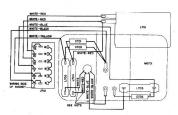a. Radio Set SCR-608-A. Figure 69 is a system schematic drawing of Radio Set SCR-608-A showing control circuit wiring in the receivers, transmitter, and mounting. It also shows Remote Control Unit RM-29-D and field Telephone



DYNAMOTOR ON-34-(+), WIRING DIAGRAM

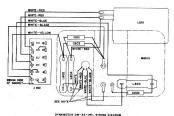

THESE WIRES SHOULD SE KEPT AS PAR AS POSSIBLE FROM ALL OTHER WIRES.

Fig. 39. Dynamotors: Schematic and Wiring Diagrams



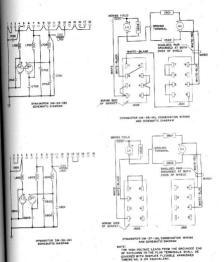


Fig. 39. Dynamotors: Schematic and Wiring Diagrams

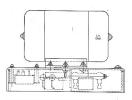

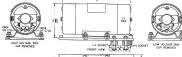

DAMPHOLOS DIN-24-HE WID DAMPHOLOS DIX-26-HE





DYNAMCTOR DM-35-(K)AND DYNAMCTOR DM-37-(K)

Fig. 40. Dynamotors: Apparatus Location Diagrams

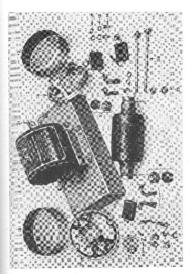


Fig. 41. Dynamotor DM-34-(*) or Dynamotor DM-36-(*): Exploded View

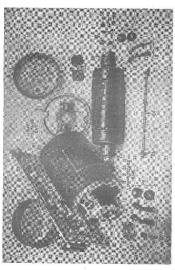


Fig. 42. Dynamotor DM-35-(*) or Dynamotor DM-37-(*): Exploded View

EE.8-(*), so that the wiring of a complete system is included. Refer to Fig. 69 for the discussion which follows.

Connections to the vehicle barrery are shown at the lower right of the mounting. The negative side is grounded and the positive lead goes to terminal 1 of mounting receptacles 1901, 1902, and 1903. On the occurrence (PG3), terminal 1 connects to the one-occurrence (PG3), terminal 1 connects to the one-occurrence, terminal 1 connects to the one-off-work D124.

When a receiver ON-OFF switch D1 is closed. the receiver vacuum tube cathodes are heated and the receiver dynamotor starts. The output of either or both receivers is available at receiver headset jacks J1 and J2, when the OUTPUT TO PHONES switches D2 are at ON. Interconnection herween headset tacks of the two receivers is over the lead connecting to terminal 21 of PG1. This lead also connects through the mounting to terminal 21 of the transmitter plug PG101, which goes to a winding on transformer T102 of the transmitter to provide sidetone in the receiver beadsets when transmitting. Receiver output volume is adjusted by VOLUME control P1, and sidetone level is adjusted by potentiometer P101 in the transmitter. The receiver loudspeakers are numed on or off by switches D3. The antenna monection to the receivers is from the TR binding post on the mounting through terminal A1 of 1403 and PG101, through a break contact of the transmitter antenna relay \$101, through terminal A2 of PG101 and I403, through terminals At of 1401 or 1402 and PG1, to the grid of vacuum tube V1. Transmitter relay S101 is ensteined when trunsmitting, so that the receivers we disconnected from the antenna.

When the transmitter ON-OFF switch DLTA is closed, the pilot hamp lights and the vacuum whe failments are heared. When a carbon-type Merophore T-17 (or T-30) is plaged into juk JiO2 and the BREWER TUNK-OFFRATE PRINCIPAL TO STATE, the TRANSMIT TO SPECIAL TO SPECIAL

energized. \$101 is the antenna relay which transfers the antenna connection from the receiver to the transmitter, applies plate voltage to the nower amplifier tube V104, and grounds the bias lead of the oscillator V107. S103 is the receiver disabling relay which, when operated, shortcilcuits the output of both receivers (leads from \$103 contacts through terminals 7 and 22 of PG101 and J405, through terminal 7 of J402, J401, and PG1; to transformers T1 in receivers). Speech signals from the microphone through 1102 are amplified in the audio amplifier tubes V105 and V106 and are impressed on the radiofrequency tubes via transformer T102. The lower secondary winding on T102 provides sidetone to the receiver headsets as previously described.

If a magnetic-type Microphone T-33 is used, it is plugged into juck 101 instead of J102. Closing the microphone switch grounds the dynamonor relay, \$102 winding over leads marked A and as and speech signals are impressed on the sudio input transformer T101 via leads marked c and n. Otherwise, operation of the transmitter is the same as that described for the carbon-type microphone.

To fumish carrier-frequency voltage for sering push button selectors in the transmitter and the receiver without purting the transmitter and the receiver without purting the transmitter. In the fore-going discussion of operation of the transmitter, In the fore-going discussion of operation of the transmitter, In the fore-going discussion is seen to accurate TUNIA (affect the co-cory switch is ourned to ox), the transmitter dynamous relay SIGD is energized and the dynamous transmit who of the selection of the discussion of the discussion of the selection of the discussion of the selection of the

Radio Set SCR-608-A may be used with Remote Control Unit RM-29-D and field Telephone EE-8-(*). These are also shown in Fig. 69, and a brief description of their function is given here.

Plug PL-55 of the remote control unit is plugged into a headset jack of the receiver and Plug PL-68 is plugged into the carbon-type microphone jack of the transmitter. A headset is

plugged into Jack IK-34-A of the remote control unit and a carbon-type microphone is plugged into Jack JK-33-A. Leads to the field telephone are connected at terminals L1 and L2. With Switch SW-185 of the remote control unit at RADIO, Jacks JK-33-A and JK-34-A are connected directly through to Plugs PL-68 and PL-55, respectively. When the transmitter and the receiver are turned on, operation is as previously described, except that speech signals pass through the remote control unit. The secondary of transformer C280 is not connected, so that no voice communication with field Telephone IE-8-(*) is possible. The field telephone station may ring the Ringer MC-131 in the remote control unit, however.

To communicate with a remote startion, Switch SW-185 of the remote control unit is thrown to TELEPHONE, which disconnects Jacks JK-33-A and connects them to transformer CER0, also connecting Battery BA-27 in series to provide talking battery supply for the microphone at the remote

control unit. When a remote station is to be called, the handle on the crank of Generator GN-38 is lifted and rotated to the right.

NN-9 is infeed and rotated to the right.

To allow the remove custom to transmit Swint's SW-185 in the remove current unit is seen in removal. The removal to the removal t

b. Radio Set SCR-628-A. The functions of Radio Set SCR-628-A are exactly the same as Radio Set SCR-608-A except that nolly one receiver is furnished. With this difference the foregoing discussion of the functioning of Radio Set SCR-608-A applies to Radio Set SCR-628-A.

MAINTENANCE SECTION IV

Social Notice to Maintenance Personnel: Be fore making replacement of any parts in this equipment, read Section V and particularly Pargraph 43 for changes in circuit components.

28. General Maintenance Information.

a. Precautions. Use care in servicing this quipment. Servicing should be done only by competent personnel who are supplied with adequate tools and test equipment. An inexrecienced operator, in attempting to locate and repair a minor trouble which a competent servkeman could care for in a few moments, might misslign or damage the equipment to such an extent as to require its being sent to a repair derot.

When working with the transmitter, either in use or in testing, make sure that one of the push buttons is always depressed when the dynanotoe is running. Also, turn the transmitter off whenever possible. In the following instructions it is necessary in

some cases to give values of voltage and current for certain conditions. Because of variations in tibes and other apparatus items, consider such values to be only approximations in most cases. As long as the result obtained does not differ greatly from the typical figure, it is probable that the unit in question is not in trouble. Several drawings will be useful in connection

with maintenance work on this equipment, parricularly the location of trouble. The following are included in addition to those mentioned in reevious paragraphs:

- Fig. 51. Radio Receiver BC-683-A: Location of Alignment and Tuning Controls. This shows where the various knobs and screws are located for use in aligning the tuned circuits and in making other necessary adjustments.
- Fig. 52. Radio Transmitter BC-684-A: Location of Alignment and Tuning Controls. This shows where the various adjustments are located for use in aligning

- the tuned circuits and in making other necessary adjustments.
- Fig. 57. Radio Receiver BC-683-A: Voltage Diagram. This shows the voltages to be expected under normal conditions from various points to the chassis.
- Fig. 58. Radio Receiver BC-683-A: Resistance Diagram. This shows the resistance values to be expected from various points on the receiver to the chassis. All resistance measurements are made with the dynamotor removed from the receiver.
- Fig. 59. Radio Transmitter BC-684-A: Voltage Diagram. This shows the voltages to be expected under normal conditions from various points to the chassis.
- Fig. 60. Radio Transmitter BC-684-A: Resistance Diagram. This shows the resistance values to be expected from various points on the receiver to the chassis. All resistance measurements are made with the dynamotor in place in the transmitter.
- Fig. 61. Mounting FT-237-(*): Schematic Dia-
- Fig. 62. Mounting FT-237-(*): Wiring Dia-

b. General Information. The cleaning, inspecting, and testing procedures contained in this section are intended to prevent development of faults in field service. Operation failures are usually caused by dirt, loose connections, bad vacuum tubes, defective wiring or component parts, misalignment, or incorrect tuning.

Unless otherwise specified, make the following soutine checks of the major components after every 300 hours of service. (Check the vehicle battery, charging generator, and voltage regulator prior to making tests of equipment installed in the vehicle.)

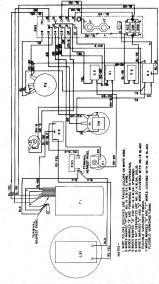


Fig. 43. Radio Receiver BC-683-A: Wiring Diagram of Front Panel

8. Routine Check of Mounting. Check the mouning and prepare it for sesting of the radio se is follows:

4. Be sure that the main fuse is intact and the the screws are tight.

A See that the spare fuse is in place.

the largest the transmitter and the receiver respecies. Repair or replace any that are damspec.

Leavest the insulators and the lead-in, and

the connection at the left-hand end of the nousing.

M. Routine Check of Radio Receiver BC-683-A.

M. RoutineCheck of Radio Receiver BC-683a. Cleaning and Inspecting.

(1) Remove the receiver from the mount-

(2) Clean the outside of the cover and the fine panel.
(3) Remove the cover and see that the cit-

nit label is secure.

(4) Clean and inspect plug PG1. Make sure

that there is a slight play in the plug mounting.

(5) Carefully shake or blow our dust and an from the interior of the receiver. Avoid troping a rag in contact with receiver parts as

his may damage them.


Now. If an air hose is used be sure that any sare condensed in it is blown out before applying the air stream to the equipment. Use only it intended for cleaning purposes and do not low hard enough to misplace or damage any popuratus.

(6) Inspect the set for:

(a) Loose or broken connections.

(b) Damaged parts.

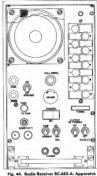(c) Evidence of excessive heating, such as luned resistors or melted wax. Such troubles can often be located by the sense of smell. Use not nose as well as your eyes.



Location Diagram, Front View of Panel

(7) Check both fuses and replace if necessary.

(8) Dust off the push-button assembly with compressed air or a bellows.

(9) Lubricate the push-button assembly as directed in Paragraph 30f. Castion: Do not get oil on the locking wedge or

friction washers.

(10) Make sure all screws and nuts are tight. Check each socket mounting screw and

each grounding screw with a screwdriver.

Contion: Do not use abnormal force when tightening screws. Take it easy.


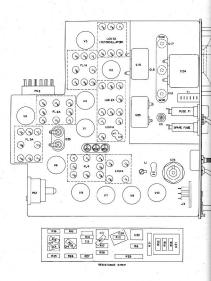


Fig. 45. Radio Receiver RC-683-A: Apparatus location Discours Left side View

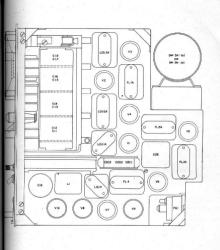

- (11) Inspect the sockets for dirty or damaged prong grips.
- b. Dynamotor Routine. Remove the dynamotor end bells and dust off the commutator and brushes. The receiver dynamotor may be serviced in accordance with Paragraph 41 of this section. Make sure that the dynamotor voltage rating is correct for the vehicle battery.

c. Vacuum Tube Cheek.

- Check the radio-frequency amplifier tube, V1, for rightness in its socket.
- (2) Remove the tube and clean the prongs.
 (3) Repair or replace the socket if the contact pins on the tube are not gripped properly
- by the socker receptacles.

 (4) Make sure that the tube is of the type specified, VT-112.
- (5) Test the tube, if possible, in the tube checker unit of Test Set 1-56-(*) in accordance with instructions furnished with the tube checker.
- Do not neglect the short-circuit test.

 (6) If the tube is satisfactory put it back in the socket from which it was removed.
- (Otherwise install a new tube.)

 (7) Repeat steps (1) through (6) for the remaining tubes.

Caution: Return each tube to the socket from which it was taken. It is important that even tubes of the same type shall not be interchanged.

d. Voltage Check.

- (1) Place all switches on the receiver panel in the downward position. Remove cover.
- (2) Connect the receiver to power, preferably with a test cord (such as Cord CD-786, one end of which plugs into a receptacle on the mounting and the other into the receiver under test). Otherwise insert the receiver into a mounting.
- (3) Connect a 1000-ohms-per-volt voltmeter of a vacuum-tube voltmeter (250- or 300volt scale) across capacitor C25, minus (—) to the blue lead and plus (+) to the red-white lead.

(4) Turn the REC switch to ON. Observe the wiring side of the chassis for smoke or sparks. If any are observed, rurn the REC switch to ory at once and check the set completely to remode the trouble. Then proceed with the following

Caution: High voltages are exposed.

- (5) Make sure that, after the tubes are warmed up, the potential across C25 is approximately 200 volts when the supply battery is in good condition.
- (6) Check the voltages at each terminal of V6 (limiter) as shown in Fig. 57. The value obtained should be reasonably close to thos specified for V6. Approximate agreement with the values given in Fig. 57 indicates that normal voltages are being supplied to a representative rube.

e. Operation Check.

- (1) Place all switches on the receiver panel in the downward position. Replace cover. (2) Insert the receiver into a mounting in
- which a transmitter is mounted.

 (3) Depress the first channel selector but-
- tons on the transmitter and the receiver.
- (4) Start the transmitter and the receiver.
 (5) Throw the RECEIVER TUNE-OPERATE switch on the transmitter to RECEIVER TUNE and the TUNE-OPERATE switch on the receiver to
- 1UNE.

 (6) Throw the SPRAKER switch to ON. If the receiver is in the proper adjustment, and set for the same frequencies as the transmitter, the full reading should agree with the channel in use, and a beat note should be heard in the load-speaker.
- (7) If no beat note is heard, check the transmitter and receiver controls to be sure that the are in the positions specified and set for the sam frequency. If not, tune the receiver as described in Paragraph 21b. If the settings are correct and no beat note is heard, check the receiver in accordance with Paragraph 3.

- (8) Throw the squelch switch to on and observe that the CALL SIGNAL lamp remains lighted. If necessary, adjust the SENSTIVITY control as described in Paragraph 20s(2).
- (9) Repeat steps (3) through (7) for each channel set up on the receiver. Turn the RECEIVER TUNE-OPERATE switch on the transmitter back to OPERATE whenever the output is not needed.
- (10) Check the operation of the manual tuning mechanism.
- (11) Throw the receiver tune-operate swith to operate.
- (12) Throw the RECEIVER TUNE-OPERATE switch of the transmitter to RECEIVER TUNE. Operate the microphone push button and speak into de microphone. Check the foudspeaker output for normal volume and quality.
- Note: The receiver output will be short-circuited by the disabling relay \$103 in the transmitter if the RECEIVER TUNE-OPERATE switch is at OPERATE.
- (13) Check the sidetone volume in the headset (OUTPUT TO PHONES switch in the OFF posison) while calking into the microphone. If sideone is not heard there may be trouble in tither the receiver or the transmitter. Check them in accordance with Paragraph 39 or 40.
- (14) Throw the RICLIVER TURN-OPERATE which on the transmitter to OPERATE, operate the microphone push button, and speak into the microphone. The sidetone volume should be satisfactory in the headset when the OUTPUT TO PHONES switch is set to ON.
- (15) Release the microphone push button and check the volume of noise in the headset. Turn the SPEAKER switch to OFF and note that the noise volume in the headset remains the same.
- f. Lubrication of Push-button Mechanism. Inspect the push-button mechanism occasionally. The push-button plungers should be lubricated with a very small amount of Univis 40 oil, or its equivatent. The rack and gests should be lubricated with Univis 115 oil, or its equivalent. Use

only a slight amount of oil, since too much oil may cause the plungers to stick under low-team perature conditions. If it is found necessary to clean the push-butnon mechanism, kerosene is the peeterred cleaning fluid. Under field conditions, where the recommended labricans may not be available, cleaning should be done with great care and lubricant omstead if the equipment is to be used under low-temperature conditions. Do not get oil on the lucking undige or the lifetime understant.

31. Routine Check of Radio Transmitter BC-684-A.

a. Cleaning and Inspecting.

- (1) Remove the transmitter from the mounting.
 - (2) Clean the case and the panel.

(3) Clean and inspect plug PG101. Make certain that there is a slight play in the plug mounting.

(4) Turn the transmitter upside down and remove the bottom cover plate.


Important: After any repair, adjustment, or teplacement of parts is made inside Radio Transnitret B/G-684-A, always take a reading with an ohmmeter between coil L119 and ground. If the reading is zero resistance you will burn out resistor R119 as soon as you apply power. Be careful.

- (5) Inspect the bottom of the transmitter for:
 - (a) Loose nuts, bolts, or screws.(b) Loose or broken connections.
 - (c) Damaged or worn parts.
 - (d) Dirt. (e) Excessive heating. Use your nose as
- well as your eyes.

 (6) Carefully inspect relays \$102 and \$103.

 If either relay requires servicing, refer to Para-
- graph 31f.

 (7) Inspect the spring and roller guides
 which keep the gang capacitor gear rack in place.

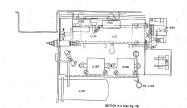

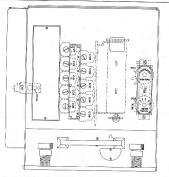


Fig. 47. Radio Transmitter BC-684-A: Apparatus Location Diagram, End View and Detail Through Section A-A

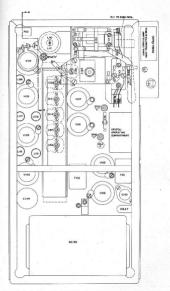


Fig. 48. Radio Transmitter BC-684-A: Apparatus Location Diagram, Top View

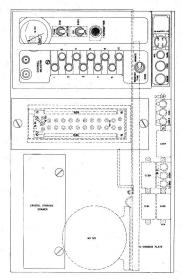


Fig. 49. Radio Transmitter BC-684-A: Apparatus Location Diagram, Front View

- (8) Clean the bottom of the transmitter.
- (9) Replace the bottom cover plate and on the transmitter right side up.
- (10) Remove the top cover plate and the mul storage drawer. See that the circuit label s secure. (When the drawer has been pulled at to its most extended position it can be remyed by raising the back portion and then rowing the front upwards to clear the catch under teback of the drawer.)
 - (11) Inspect the top of the transmitter for:
 - (a) Loose nurs, holts, or screws. (b) Loose or broken connections.
 - (c) Damaged or worn parts. (d) Dire.
 - (e) Excessive hearing.
- (12) Carefully inspect relay \$101. If this relay requires servicing, refer to Paragraph 31f.
- (13) Clean the push-button assembly with compressed air or a bellows. Use of an air hose
- requires caucion as noted in Paragraph 30a(5). (14) Lubricate the push-button assembly as directed in Paragraph 31g.
- Cestion: Do not get oil on the locking wedge or friction washers
- (15) Check each socket mounting screw with a screwilriver Contion: Do not use abnormal force when tight-
- ening the screws. (16) Check the security of the grounding points.
- (17) Inspect the tube clamps.
- b. Dynamotor Routine. The transmitter dynamotor may be serviced in accordance with Parasraph 41. Make sure that the dynamotor voltage tating is correct for the vehicle battery.

c. Vacuum Tube Check.

(1) Loosen the tube clamp and check the power amplifier tube, V104, for tightness in its socker.

- (2) Remove the tube and clean its prongs.
- (3) Repair or replace the socket if the contact pins on the tube are not gripped properly by
- the socker receptacles. (4) Make sure that the tube is of the specified type, VT-165.
- (5) Check the tube with a tube tester. Do not neglect the short-circuit test.
- (6) If the tube is satisfactory, put it back in the socket from which it was taken and re-
- righten the tube clamp. (Otherwise install a new tube.) (7) Repeat steps (1) through (6) for the
- remaining tubes. The tubes in the remaining sockets are marked VT-164. Replace each tube in the socket from which it was removed.

d. Crystal Check.

- (1) Open the crystal storage drawer and the crystal operating compartment and check the number of crystal holders issued.
- (2) See that the required crystal holders are properly placed in the crystal operating compartment
- (3) Check each operating crystal for firmness in its socker.
- (4) Replace the crystal storage drawer and the crystal operating compartment cover plate.
 - e. Operation Check. (1) Remount the transmitter and associated
- receiver on the mounting in the vehicle. (2) If radio eraosmission is not authorized.
- remove the antenna lead from the TR binding post on the mounting and connect Antenna A-83 (phantom) to the A and G terminals on the transmitter with short leads.

Note: If Antenna A-83 is not available, an antenna constructed according to Fig. 77 may be used. If, in an emergency, neither of these is available, a 40-watt, 115-volt Mazda lamp may be used. Notice, however, that neither the lamp nor the antenna according to Fig. 77 closely

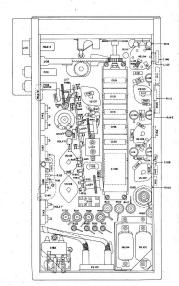


Fig. 50. Radio Transmitter BC-684-A: Apparatus Location Diagram, Bottom View

simulates the actual antenna; it is therefore doubly important to readjust the antenna trimner, as covered in paragraph (11) following, the connecting to the real antenna.

- (3) Plug in a microphone and a headset.
- (4) Turn the transmitter and the receiver on and sore that the transmitter pilot lamp lights.
- (5) Throw the transmitter receiver tunetograms switch to operate and the receiver supply to phones switch to off.
- (6) Press the microphone button, observe that the dynamotor starts, and talk into the microtione.
- (7) Note that sidetone is heard in the headset and that its volume may be varied by adjusting the transmitter SUDETONE Control.
 (8) Tune the transmitter and the receiver
- on the same channel and throw the OUTPUT TO PHONES switch on the receiver to ON.
- (9) Speak into the microphone and observe that the speaker's voice is heard in the headset.
- (10) Turn the SPRAKER switch to ON and ke that the speaker's voice is not heard. Throw the MILLIVER TUNE-OPERATE switch on the transsiter to RECEIVER TUNE and note the speech suppur is then obtained from the loudspeaker. Return to OPERATE at the transmitter.
- (11) For each push button, check the meter readings in accordance with Paragraph 19b, Table V. for each of the METER SWITCH positons (TUNE-ANT CUR switch on TUNE) and for he ANT CUR position of the TUNE-ANT CUR switch. It may be necessary to adjust the antenna trimmers (C127 to C136) because of possible differences between the real antenna and the phantom antenna. There will be considerable variation in meter readings among different transmitters due to power supply, vacuum tube, and circuit variations. Experience with a number of transmitters is the best way to learn which readings are satisfactory and which are not. When the transmitter is set to RECEIVER TUNE the meter current for METER SWITCH position 5

will rise to about twice that shown in Table V and the current for METER SWITCH position 6 will drop to about half that shown in Table V. Paragraph 40e gives further information on these differences.

(12) If this check is made in cold weather, notice that the thermostat which controls the beaters in the crystal compartment operates at approximately 70 degrees Fahrenheit.

f. Relay Maintenance.

(1) General. Burnish the relay contacts with a burnishing tool or other thin flat piece of smooth metal. Never use abrasive papers or cloths. If the contacts become pitred, a fine file may be used to remove the rougher spots, after which the contacts should be burnished. Take precautions against metallic filings falling or beine blown into the apparagne.

No provision is made for adjusting contacts and it should not be necessary under ordinary conditions. The contacts should be parallel when brought together. If some special situation makes it necessary to adjust the contacts, it is preferable to bend the contact arm eather than the spring (except for relay \$101).

Warning: The spring assembly of \$102 is connected to the vehicle battery even when the transmitter ON-OFF switch is in the OFF position and the green pilot light is extinguished. If you find it necessary to work on this relay be sure to disconnect the battery at plug PG101. If you don't, you are very likely to destroy the relay; you may also get a nasty burn on your, band.

(2) Antenna Switching Relay 5101. The contact springs are mounted on Isolantite bars which are very brittle. Take care to avoid straining or deforming these bars. If any bending adjustment is required, it should be made on the springs. Keep the points clean.

(3) Dynamotor Starting Relay 5102. Keep the points clean at all times. When the relay is released, the separation between points should be approximately the thickness of a thin dime. When the relay is operated, the atmature travel should be somewhat more than the amount necessary to close the points. Then the contact springs will be bent slightly and will exert some pressure to hold the points in good contact.

- (4) Receiver Disabling Relay \$103. The points should be kept clean.
- g. Lubrication of the Push-button Mechanism. Inspect push-button mechanisms occasionally. Lubricate the push-button plungers with a very small amount of Univis 40 oil, or its equivalent, and the rack and gears with Univis 115 oil, or its equivalent. Use only a slight amount of oil. Too much oil may cause the plungers to stick under low-temperature conditions. (Cantion: Do not get oil on the locking wedge or friction washers.) If necessary, clean the push-button mechanism with kerosene. Under field conditions, where the recommended lubricants may not be available, cleaning should be done with great care and lubricant omitted if the equipment is to be used under low-temperarure conditions.

32. Routine Check of System.

- a. Inspection of Antenna System.
- (1) See that Wire W-128 or Coaxial Cord CO-282 between the antenna mast base and the binding post of the mounting is properly supported and that the connections are firm and not short-circuited.
- (2) Be sure the proper antenna mast sections are installed and that their couplings are firmly joined.
- (3) Inspect the antenna mast base carefully. Wipe off all dust and any vegetation that may have caught in the springs. Flex the base to be sure the springs are not broken and that the lead to the radio equipment is in good order.
- (4) Carefully inspect all ground straps, if used, and all bolted connections in the ground system. Tighten or resolder any doubtful connections.
- b. Talking Tests. Upon completion of the routine tests described in Paragraphs 28 to 32a.

inclusive, it is desirable, if practicable to do so, talk between two vehicles. Make this test wit Antenna A-83 (phantom) instead of the reg lar radiating system to prevent excessive sign radiation from either equipment. (If no Ante na A-83 is available, use an antenna constructe according to Fig. 77; if this is not possible, use 40-watt, 115-volt Mazda lamp.) A two-way on versation test should be made with vehicle equipped with Radio Set SCR-608-A or Radi See SCR-628-A

TM 11-62

33. Emergency Check of Receiver Output Ve ume and Circuit Alignment. a. General. When the testing equipment for precision servicing of a receiver is not available make a rough check of the alignment of the s

ceiver circuits. The tests described may be made with the receiver mounted in the vehicle. Mi aligned circuits so found may be realigned wit a minimum of testing apparatus by following the directions in Paragraph 34. The location of the alignment controls is shown in Fig. 51. b. Testing Apparatus Required.

- 1-Radio Transmitter BC-684-A known to be good condition.
- 1-Microphone T-17 or Microphone T-33. 1-Output meter of Test Set I-56-(*) equippe with a 31/2-foot assembly of Cordage CO-14 and Plug PL-55.
- 1-Volt-chmmeter of Test Set I-56-(*), or 1000-ohms-per-volt voltmerer, or a vacuut tube voltmeter, 3-volt scale,

c. Check of Output Volume.

(the transmitter not operating).

- (1) Install the transmitter on the mountin (2) Plug in a microphone and adjust the transmitter and the receiver to the same chann
- (3) Connect the plug and cord assembly Test Set I-56-(*) to the ± and VM terminals the output meter, adjust the meter for the 1 volt scale, and insert the plug into one of the PHONES tacks on the receiver.

- (4) Turn the SPEAKER switch to ON, throw the TUNE-OPERATE switch to OPERATE, the OUTPUT TO PHONES switch to ON, and the SQUEICH switch to OFF. Adjust the SENSITIVITY and WILLIMS CORPOLS to the extreme right (maximum volume).
- (5) Turn on the transmitter and the receiver and, after the vacuum tubes are bot, throw the BECHVER TUNE-OPERATE SWITCH On the transmitter to RUCEIVER TUNE.
- (6) Operate the microphone switch and whistle or shour for about three seconds into the microphone. The output meter should indicate 12 volts or more; if it does not, check the receiver is accordance with Paragraph 39. (Tune the receiver to the transmitter frequency.)
- (7) Check the receiver VOLUME control by uning the control to the extreme left while whisting or shouting. The output meter reading should decrease uniformly to 1.0 volt or less; if it does not, it indicates that the VOLUME control may be defective or the amplifiers may be noisy.

d. Check of Circuit Alignment.

- Remove the receiver dust cover and place the receiver in the right-hand position of the mounting. Leave the left-hand position vacant.
- (2) Turn the SPEAKER switch to ON, throw the TUNE-OPERATE switch to TUNE, and the QUELCH switch to ON. Adjust the SENSITIVITY and VOLUME controls to the extreme right.
- (3) Press any convenient channel push buttion on the transmitter. Operate both transmitter and receiver ON-OPF switches to ON. Operate the RECEIVER TUNE-OPERATE switch to RECEIVER TUNE.
- (4) Manually tune the receiver to zero-heat with the transmitter frequency. Make sure that the CALL SIGNAL lamp lights. Read the setting of the receiver dial.
- (5) Carefully adjust the tuning dial to each side of the zero-beat setting until the CALL SIG-

- NAL lamp goes out. Note the two dial readings at which the lamp goes out. The lamp should remain lighted over approximately three channel divisions, and the zero-beat setting should be close to the center of this tuning range.
- (6) Set the SENSITYETY control to the extreme left (minimum sensitivity) and carefully adjust the tuning dail to each side of the zerobeat setting. The lamp should remain lighted over approximately two channel divisions; and the zero-beat setting should be at the center of this tuning range, within plus or minus one-half channel.
- (7) If the zero-beat setting is found to be not centered, in steps (3) and (6), obtain the "reduced-voltage" points as described in Paragraph 33r following and realign the circuits as outlined in this paragraph.

e. Reduced-voltage Points.

- (1) Connect the voltmeter across the limiter cathode choke (L1), with the minus (—) terminal of the meter connected to ground. (See Fig. 51.)
 (2) Turn the SPEAKER switch to OFF, set the
- TUNE-OPERATE switch on OPERATE, and throw the squeech switch to OFF.
- (3) With the transmitter operating on RE-CHIVER TUNE, manually tune the receiver dial for a maximum deflection of the volumeter. Note the volumeter reading and the dial setting.
- (4) Carefully adjust the uning dial to each side of the maximum volumers deflection until the volumers indicases there fourths of the maximum deflection. Nose the two dial readings so obtained. These are the "reduced-voltage" joints. The data should be found adjustable to between plus or minus one-half and plus or minus one-half and plus or minus one channed division without redoing the volumeer indication to less than three fourths of its maximum efflection.
- (5) Throw the SPEAKER switch and the SQUELCH switch to ON, and the TUNE-OPERATE switch to TUNE.

(6) Twee for zero bear with the entaminite frequency. The twen-bear stering of the dial should be centreed between the "reduced-wolage" points. If the zero-bear stering is not centered, the intermediate-frequency oscillators should be adjusted as doscribed in Paragraph 34. If the zero-beat setting is centered with respector the "reduced-wolage" joints but not centered with respect to the dial settings at which the CALI.

34. Emergency Alignment of Radio Receiver BC-683-A.

a. General. When a receiver is found to be out of alignment it can be put into serviceable condition if another receiver or another transmitter in good condition is available. Whenever possible, check such emergency alignment in accordance with Paragraph 37. The method using a good receiver is described first as it permits alignment of all stages.

b. Method Using Good Receiver.

- Testing Apparatus Required. The following testing equipment is required:
- 1—Radio Receiver BC-683-A known to be in good condition.
- 1-Mounting FT-273-(*).
- 1—Insulated ¼-inch hexagon socket wrench.
 1—Resistor, 1000 ohms (not critical), equipped with clips. (To avoid accidental short circular short ci
 - cuits, the clips should be insulated, if possible.)

 1—Voltmeter of Test Sct I-56-(*) or other volt-
 - meter of 1000 ohms or more per volt, equipped with approximately 3-foot leads (preferably twisted), and clips.

 1—Twisted pair (one wire with tracer) about
 - 3 feet long, with clips on both ends, one wire to have a capacitor of 0.001 microfarad or larger between the wire and the clip.
 - 1—Wire about eight inches long, with clips at

3—Wires each about one inch long, with a clip at each end of each wire.

1-Cord CD-786.

Caution: When connecting or disconnecting these wires, turn the receiver off each time to avoid shocks or equipment damage.

(2) Preliminary Steps. The following steps in Coloriver alignment are divided functionally for convenience in description and understanding but remember that in most cases a change in the alignment of any of the parts involves checking the adjustment of the other parts. The receiver under test will be referred to as the "trouble receiver in the following discussion."

- (a) Remove the covers from both receivers.
- (b) Place all switches at OFF (or downward) in both sets. (The squeech switch may have to be turned on subsequently as explained in paragraph (3)(a) following.)
- (c) Secure the good receiver in the righthand position of the mounting. Apply appropriate power to the trouble receiver by means of Cord CD-786 or equivalent.
- (d) Turn both sets on and set the TUNE-OPERATE switches at TUNE.
- (e) Allow both sets 10 to 15 minutes to warm up.

 (f) Connect both chassis together using one wire of the above twisted pair. Use the wire
- which does not have the capacitor in series.

 (3.) Tuning of the 1/9 Outlaner and the
 1/3 Amplifier Tuned Circuits FLLA, FLEA, as
 FLEA, A signal from the intermediate-frequency
 oscillator in the good receiver is picked up by
 ELEA, A signal from the intermediate capacitie
 (which is attached to the twisted pair as just described) to terminal 7 of FLI of the good receiver. The other end of the wire in series with
 4) of the modulator (V2) in the trouble retractional control of the capacitor goes to the control grid (terminal
 4) of the modulator (V2) in the trouble retractional control of the capacity of the cap

frequency oscillator can be tuned to zero-beat with that in the good receiver. As a quantitative indicator for tuning the intermediate-frequency circuits, a 3-volt (1000-or-more-ohms-per-volt) voltmeter is bridged across L1, step (e). A rough adjustment of FL1A, FL2A, FL3A, step (f), may be necessary in order to pass enough intermediate-frequency tone for beating with the intermediate-frequency oscillator. Unless the intermediate-frequency amplifier in the good receiver is shorted, step (b), noise will be superimposed on the test signal. In order to avoid undesirable interference in the alignment, the radio-frequency oscillator in the trouble receiver is disabled by increasing the bias on the grid. step (a). In order to avoid flattened response and consequent errors in alignment, the delayedautomatic-volume-control load resistor, R14, is shorted, step (a). It may be necessary to turn the SOUBLCH switch to on and adjust the SENSTRY. my control until an accurate tuning indication is obtained. In aligning the secondary of an FL unit a 1000-ohm resistor is connected across the primary to improve the accuracy of the adjustment. Similarly, in aligning the primary the resistor is connected across the secondary.

- (a) Short-circuit R14 of the trouble receiver. Also connect reminal 5 of V3 to C25 the side to which blue-tracer wires are attached. (It may be necessary to turn the SQUILCH switch to ON and adjust the SANSTITY! Control to obtin a usable reading on the volumeter when uning the FL units.)
- (b) Short terminals 1 and 2 of FL3A of the good receiver with a short clip lead.
- (c) Connect terminal 7 of FL4 in the good receiver through the series capacitor to terminal 4 of V2 in the trouble receiver. Use for this the remaining wire of the twisted pair, the wise which has the capacitor in series. The unwisted part at the ends should be as short as possible. The capacitor should be nearest to the good receiver.
- (d) Place the SPEAKER switch of the mouble receiver at ON.
 - (e) Clip the 3-volt meter across L1 of ments, especially that of LCU4.

- the trouble receiver with the negative side on the ground lug.
- (f) If the receiver is seriously misaligned, obtain a rough alignment by adjusting the slugs in FL3A, FL2A, and FL1A, in that order, for maximum meter reading. (The 1000-ohm shunt is not used in this procedure.)

Nate II no change in meter reading is observed when the slags of FL5A are adjusted, turn the when the slags of FL5A are adjusted, turn the whole the slags of FL5A are adjusted, the of the meet. If lith does not cause any change in deflection the trouble receiver may be fauly and require service. He deflection is not small for satisfactory reading, the connection at ceminal 7 of FL4 may be moved to returned to the state of the state of the state of the LH4 to obtain a larger reading for the pediament is should be remarded to remain 3 of FL4 which gives a signal strength more appropriate for the subsequence transfer and the state of the for the subsequence that

Castion: The lock washers on the runing slugs of the tuned circuits may be damaged by turning the slugs in too far. When any adjustment of these units is made, make sure that the runing slugs bind sufficiently to insure permanency of setting. If they feel loose during adjustment, eighten the lock washers by turning them to the right with a small screwdriver.

(g) Align LCU4 of the trouble receiver for zero-beat and turn the TUNE-OPERATE switch to OPERATE.

(h) Clip the 1000-ohm resistor across terminals 3 and 4 of FL3A. Adjust the primary slug (P) for maximum meter reading.

 Remove the 1000-ohm resistor and clip it across terminals 1 and 2 of FL3A and adjust the secondary slug (s) for maximum meter reading.

(j) Repeat step (h) for FL2A.(k) Repeat step (i) for FL2A.

(I) Repeat step (j) for FL1A. (m) Repeat step (k) for FL1A and re-

move the 1000-ohm resistor when the alignment is completed.

(n) It is advisable to check all adjust-

 (n) It is advisable to check all adjustsents, especially that of LCU4.

(4) Tuning of FL4: The Discriminator Circuit. The volumeter is connected across the discriminator load resistors, step (a). The secondary is adjusted for zero d-c output in this meter, step (b). As the secondary slug is adjusted through the proper point, the d-c reading will change polarity. The automatic volume control is restored to operation and the delay bias removed, step (c), and the meter is connected across the resistor (R38) in the plate circuit of V1, step (e), thus giving an indication of automatic-volume-control action amplified through V1. The primary of FL4 can then be adjusted for a minimum reading in the meter. The 1000ohm shunt is used across the output of FL1A, step (d), to control the gain.

(a) Remove the meter and bridge it across terminals 3 and 7 of FL4. Polarity of the meter cannot be specified as it will depend on the adjustment. (b) Align the secondary of FL4 for zero reading on the meter. Note that as the slug is

the alignment meter should move up scale for one direction and down scale for the other. (c) Remove the short from R14, and

ground terminal 1 of FLA

(d) Place the 1000-ohm shunt between rerminals 3 and 4 of FL1A.

(e) Remove the meter and bridge it between terminals 2 and 3 of LCU2A, the positive lead going to terminal 3. It may be neces-

sary to use the 30-volt scale.

(f) Align the primary of FL4 for minimum meter reading.

(g) Remove both the 1000-ohm shunt and the meter.

(h) Remove the short between C25 and terminal 5 of V3. (i) Remove the lead from terminal 4 of

V2 of the trouble receiver, and from terminal 7 of FL4 of the good receiver.

(i) Remove the short between terminal 1 of FL4 and ground.

(5) Tuning of the R-f Oscillator, Assuming the Intermediate Frequency to be Exactly

2.65 MC. This involves beating the radio-frequency oscillator of the trouble receiver with that of the good receiver to give zero-beat in the loudspeaker. The stray pickup in the trouble receiver from the good receiver is sufficient so that no direct connection of the radio frequency between the two receivers is required. The intermediate-frequency oscillator of the trouble receiver has been adjusted and is thus suitable for beating purposes. The meter is bridged across L1, step (a), as an indicator to show when the current through the intermediate-frequency amplifier is increasing even though the frequencies are not close enough together to give an audible beat. It is left in this position to show when LCU1A and LCU2A are properly adjusted. The short is placed across R14, step (b), to avoid a flattened response curve, as discussed in Paragraph 34b(3). The intermediate-frequency oscillator is turned on, step (c), to provide a beat note. At the upper end of the scale the oscillator is set by adjusting the trimmer C1.7 to give zerovaried in either direction from the zero reading, beat in the loudspeaker. Since the intermediate frequency is nominally 2.65 megacycles, there must be a corresponding difference between the two oscillators involved in order to produce a hear tone which will pass through the intermediate-frequency amplifier. For the high-frequency end of the scale, set the trouble receiver dial at 39 megacycles and set the good receiver dial at (39-2.65=) 36.35 megacycles. Then the trimmer. C1.7, is set for zero-beat in the loudspeaker. For the low-frequency end of the scale set the good receiver dial at 27 megacycles and the trouble receiver at 29.65 megacycles. With this setting the slug in LCU3A is set for zero-beat, These two adjustments are then made alternately until the oscillator "tracks" satisfactorily at both

ends of the band. (a) Bridge the meter across L1 (negative terminal toward ground).

(b) Place a short across resistor R14.

(c) Place the TUNE-OPERATE switch of the trouble receiver at TUNE and throw the TUNE-OPERATE switch in the good receiver to OPERATE. (d) Assuming the intermediate fre-

quency to be 2.65 megacycles, set the good re-

reiver at (39 - 2.65 =) 36.35 megacycles and

the trouble receiver at 39 megacycles.

trimmer capacitor C1.7 of the trouble receiver

to give zero-beat in the loudspeaker. (f) Still assuming the intermediate frequency to be 2.65 megacycles, set the good receiver at 27 megacycles and the trouble receiver at (27 + 2.65 =) 29.65 megacycles, and, in the same way, adjust the slug in LCU3A for zero-

(c) Adjust the radio-frequency oscillator.

(g) Repeat the preceding two steps until the radio-frequency oscillator tracks at both ends of the hand

(6) Check of the Intermediate Frequency and Readjustment of the R-f Oscillator. In the foregoing procedure it was assumed that both the intermediate-frequency amplifier stages and the intermediate-frequency oscillator were adjusted m exactly 2.65 megacycles. Actually, a variation obtained by a slight change in the trimmer C1.7 in this frequency over a moderate range will not at the high end of the scale. The procedure to be interfere with satisfactory operation as long as followed if a correction is necessary is described the adjustment of the radio-frequency oscillator in steps (a) through (g). is consistent with the intermediate frequency. For example, if the dial of the trouble receiver a set at 39 when the intermediate-frequency amolifier (and oscillator) circuits of the good reteiver and the trouble receiver are tuned for 2.5 megacycles, then set the dial of the good rereiver at (39 - 2.5 =) 36.5 megacycles for aligning the radio-frequency oscillator in the muble receiver. Otherwise, the dial calibration will not be correct. For this reason, it is desirable to make the following tests which supplement Paragraph 34h(5) rather than supersede it. The prouble receiver is set (in the middle of the range) at 33 megacycles and the good receiver is adjusted to a frequency which will give zerobest with the intermediate-frequency oscillator in the trouble receiver. The reading on the dial of the good receiver should be very close to (33 -265 =) 30.35 megacycles. (This reading serves

as a guide. The second bear, to be obtained near 35.65, is a better indication of the accuracy of adjustment.) A similar beat, though not so strong, can be obtained by tuning the good rectiver the same distance above the trouble receiver. (If the beat note cannot be found readily, due to insufficient pickup, connect the bared end of a piece of insulated wire to the A post of the trouble receiver and extend it across the ron of the good receiver to act as an antenna. Remove this wire when the observation is complete.) This dial setting should be between 35.6 and 35.7 megacycles. This allows for the 0.05-megacycle tolerance at (33 + 2.65 =) 35.65 megacycles. If it falls within that range, the radiofrequency oscillator is properly runed and no further work on it is necessary. If not, steps (d) through (g) should be followed. Assume, as an example, that the two dial settings giving zerobeat were 30.35 and 35.35 megacycles. Half the difference between these frequencies represents the true intermediate frequency which, in this example, comes out as 2.5 megacycles. This figure is then used instead of 2.65 in steps (d) to (p). Ordinarily, the necessary correction will be

(a) Set the dial of the trouble receiver to 33 megacycles.

(b) Adjust the dial of the good receiver to give zero-beat at approximately 30.35 megacycles and note the dial reading at which it occurs.

(c) Leaving the trouble receiver runed to 33 megacycles, returne the good receiver to obtain the (somewhat weaker) beat note between 35 and 36 megacycles. Nore the dial reading.

(d) By subtraction, obtain the difference between the two dial readines obtained in steps

·(b) and (c). (e) Divide this difference by two.

(f) The value obtained in this way is the actual intermediate frequency. (g) Repeat the alignment procedure,

(5)(d) through (g), for the radio-frequency * oscillator, using this value in place of 2.65 megacycles.

(h) Make certain that the radio-frequency oscillator tracks at both ends of the band. (i) Remove the short from terminals 1 and 2 of FL3A in the good receiver.

(j) Replace the cover on the good re-

(7) Adjusting LCU1A and LCU2A. In tuning the radio-frequency circuits a shunt is placed across FL1A, step (a), to avoid limiting action. Also, R14 is shorted and the squelch switch turned to ON for the reasons just discussed. If the trouble receiver is not in a mounting, the ground on the primary at LCU1A is floating. Therefore, terminal 2 of LCU1A must be shorted directly to ground, step (b). Also, short the antenna post (terminal 3 of LCU1A) to terminal 2 and ground, step (b), as its effect on the adjustment of the secondary would be noticeable if it were allowed to float. Without the ground, this floating condition would exist as there is no termination across the primary of LCU1A when we are relying on stray pickup for the test signal. For preliminary alignment, at the top of the frequency band, adjust the trimmers C1.1, C1.3, and C1.5 to give maximum reading in the meter; at the bottom of the band, adjust the slugs of LCU1A and LCU2A for maximum meter reading. For final alignment, the 1000-ohm shunt should be removed, the good receiver turned off, and the final alignment of LCU1A and LCU2A made on noise alone at both ends of the scale. This procedure is given as step (k).

(a) Place a 1000-ohm shunt between terminals 1 and 2 of FL1A. Connect the 3-volt meter across L1 of the receiver with the negative side

on ground lug. Short R14.

(b) Short terminals 3 and 2 of LCU1A

to ground, using the shortest wires.

(c) Set the dial of the trouble receiver

to 39 megacycles.

(d) Tune the good receiver at approximately 36.35 megacycles on the dial to give a been note on the loudsnesser.

beat note on the loudspeaker.

(e) Align C1.1, C1.3, and C1.5 for max-

imum reading on the meter.

(f) Set the dial of the good receiver at 27 megacycles.

27 megacycles. (g) Tune the trouble receiver at approximately 29.65 megacycles to give a beat note.

(h) Adjust the slugs in both the primary Note: During the

and secondary of LCU2A and the slug in LCU1A for maximum reading of the meter.

(i) Repeat steps (c) through (h) until these units track at both ends of the band. (This completes the rough adjustment.)

(i) Turn the good receiver off. Turn

the SQUELCH switch of the trouble receiver to OFF. Remove the 1000-ohm shunt from FL1A of the trouble receiver.

(k) Repeat the alignment steps for LCU1A and LCU2A using noise background alone for maximum meter reading at both ends of the dial (27 and 39 megacycles).

of the dial (27 and 39 megacycles).

(1) Remove the short circuit from R14.
Remove also the meter, and the short circuits from terminals 3 and 2 of LCU1A to ground

(m) Replace all cover plates securely.
 (n) Replace the dust cover.

(o) Reset the push buttons using a transmitter as described in Paragraph 21s.

(p) Place the set in its installation and trim C1.1.

c. Method Using Transmitter.

ou Cang I ranamia

(1) General. One, or possibly two, misligned circuits in a receiver can be roughly aligned with the remaining circuits of the receiver, in an emergency, by using an associated transantier, or the transantier in a reastly we energy and the contract of the reastly and the conduct with Paragraph 37 as soon as peaced into circuit. (EU/SA) should not be attempted by this method. In the instructions which follow, it is assumed that the radio-frequency oscillator using (EU/SA) should be refreshed to the radio-frequency oscillator. It is assumed that the radio-frequency oscillator in the contraction of the radio-frequency oscillator. It is also successful. This also successful but the radio-frequency oscillator. It is also successful.

frequency testing frequency is the associated transmitter. Modifications to adapt the method to the use of a transmitter in a nearby which are obvious. (For example, when the local transmitter is used, the RECEVER TUNE-OPERATE switch is turned to RECEVER TUNE), whereas it is furned to OPERATE when another vehicle is used.)

Note: During the following tests, operate the

end.

transmitter dynamotor only when reading the meter or making an adjustment which requires

- power from the dynamotor.
- (2) Testing Apparatus Required. 1-Radio Transmitter BC-684-A known to be in good condition.
- 1-Mounting FT-237-(*).
- 1-Volt-ohmmeter of Test Set I-56-(*), or a 1000-ohm-per-volt voltmeter, or a vacuumtube voltmerer. Meter to have a 3-volt scale and also a 10- or 30-walt scale.
- t-Insulated 1/e-inch hexagon socket wrench. 1-IRC BT-1/2, 5000-ohm resistor or its equiva-
- lent with clips and short leads. 1-500-micromicrofarad mica capacitor with
- small clips and very short leads. 2-Wires, each 11/4-inches long, with a small
- clip on each end of each wire. 1-Wire, 6-inches long, with small clip on each
- (3) Emergency Alignment of 1-f Oscillator. Align a defective or replacement LCU4 tuning unit as follows:
- (a) Install transmitter and receiver on the mounting. Place the receiver in the rightbend position.
- (b) Find the "reduced-voltage" points a directed by Paragraph 33e, and make your serting halfway between.
- (c) Remove the cover plate which pernits access to the adjusting screw in LCU4. (d) Vary the setting of this screw until
- I beat note is heard. Carefully adjust for zerobest. This step brings the replacement tuning unit, LCU4, into alignment with the intermediste-frequency amplifier.
- (4) Emergency Alignment of I-f Amplifier. Biergency alignment of an intermediate-frequency filter unit (FL1A, FL2A, FL3A) may be accomplished as follows:
- (a) Install the transmitter and the reteiver in the mounting, with the receiver in the pight-hand position.

- (b) Connect the voltmeter (3-volt scale) across the limiter cathode choke. L1, as shown in Fig. 51.
- (c) Disable the automatic-volume-control circuit by short-circuiting resistor R14. Use the short jumper wire with a clip on each end. (d) Using the 6-inch jumper, wind a coil
- of four turns of 1/4-inch diameter about 1/4-inch long. Connect this coil between terminal 4 (control grid) of modulator tube V2 and the adjacent socket ground terminal. This shunt is to reduce the input to the intermediate-frequency amplifier to a point where the action of the limiter circuits will not mask the tuning point during tests. It may be found necessary to adjust the number of turns or the spacing to secure suitable values, step (h).
- (e) Turn the receiver on-OFF switch to ON; the TUNE-OPERATE switch to TUNE; the SPEAKER switch to ON; the SQUELCH switch to OFF: the VOLUME control to the extreme right. Release the tuning dial by depressing one of the CHANNEL SELECTOR push buttons part way.
- (f) Adjust the transmitter to a channel near the 27-megacycle end of its frequency range. Turn the transmitter on Place the RECEIVER TUNE-OPERATE switch on RECEIVER TUNE.
- (g) After the receiver has had time to warm up, carefully adjust the receiver dial (use the same setting as on the transmitter) for zerobear with the transmitter signal and note the maximum deflection of the voltmeter as the dial is tuned through the zero-beat point. The meter deflection should decrease as the dial is varied to either side of zero-bear. Resence the zero-bear adjustment after completing the observation.
- (h) Remove the coil from V2 and note the reading of the voltmeter. The voltmeter reading with the coil in place should not be more than three fourths of the reading with the coil removed. If it is more, adjust the spacing of the turns or change the number of turns until a satisfactory reading is obtained.
 - (i) Replace the coil.
- (i) Detune the receiver by several channels (to a point where no signals are being received) and note the minimum voltmeter read-

ing. (The voltmeter is effective as a tuning indicator only if its deflection is kept between the minimum value and the "three-fourths" reading, step (h). Therefore, keep the deflection within this range at all times during this procedure.)

(k) Remove the cover plates from the tuning unit (FL1A, FL2A, or FL3A) to be aligned.

(1) Adjust the p (primary) and s (secondary) adjusting screws of the tuning unit for a rough approximation of the maximum voltmeter deflection.

meter deflection.

(m) Connect the 5000-ohm resistor between terminals 3 and 4 of the tuning unit being

adjusted.

(n) Adjust the P screw for a maximum voltmeter reading. See the Note following step

(p).

(o) Remove the resistor from terminals 3 and 4 and connect it between terminals 1 and 2.

(p) Adjust the s screw for maximum

voltmeter reading.

Note: Check the zero-beat setting occasionally as the work progresses. Also, keep the voltmeter within the limits given in step (j) by adjusting the shunting coil as necessary. Remove the coil and the 5000-ohm resistor.

- (5) Emergency Alignment of R-f Amplifier. Make an emergency alignment of a radio-frequency tuning unit (LCU1A or LCU2A) as follows:
- (a) Install the transmitter and the receiver in the mounting, with the receiver in the right-hand resirion.
- right-hand position.

 (b) Connect the voltmeter (3-volt scale)
 across the limiter cathode choke, L1, as shown in
- Fig. 51.

 (c) Disable the automatic-volume-control circuit by short-circuiting resistor R14. Use the short jumper wire with a clip on each end.
- (d) Connect the 500-micromicroficata apacitor between terminals 1 and 2 of filter unit FLIA. (The capacitor reduces the signal input to the intermediate-frequency amplifier sufficiently to prevent limiter action from masking the desired tuning point in the test.)

(e) Remove the cover plates from the LCU1A and LCU2A runing units and from the trimmer capacitors, Cl.3, Cl.5, and Cl.7. (The cover plate of Cl.7 is beside C24.)

Caution: Do not disturb the setting of the oscillator trimmer capacitor C1.7 during this alignment.

(f) Turn the SPEAKER switch to ON, set the TUNE-OPERATE switch to TUNE, and turn the SQUELCH switch to OFF. Turn the VOLUME COBposed to the extreme right.

trol to the extreme right.

(g) Adjust the transmitter for operation near the 39-megacycle end of its frequency range and start the transmitter and the receiver. Place the transmitter in the RECEIVER TUNE condition.


(h) After the receiver has warmed up,

detuned from the zero-beat point.

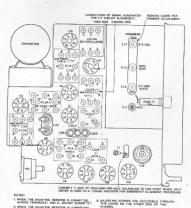(3) Remove the 500 micromicrofund capacitor shunt from teeminals 1 and 2 of the fifter unit shunted as called for in sep (g). The volumeter reading with the capacitor in plate should be not more than three fourths of the reading with the capacitor removed. If it is most, the capacitor leads are too long, or the clips are nor making apod contact.

(j) Replace the capacitor and trim the serrings of C1.1, C1.3, and C1.5, if necessary.

(k) Operate the transmitter near the 27megacycle end of its frequency range and care fully adjust the receiver to zero-beat with the transmitter. The reading of the receiver dial should correspond with the transmitter frequency.



2. WHEN THE SHUNTING RESISTOR IS CONNECTED ACROSS TERMINALS 3 AND 4, ADJUST SCREW "P".

CONNECT. THE HIGH SIDE OF THE SIGNAL-GEN-ERATOR OUTPUT TO TERMINAL 6 OF FL3 THROUGH A 0.006-MF MICA CAPACITOR FOR DISCRIMINATOR (FL4) ADJUSTMENT. THE ADJUSTING SCREWS REFERRED TO IN NOTES I AND 2 ARE ACCESSIBLE THROUGH THE TOP OF THE FILTER COVER ON THE OTHER SIDE OF THE CHARGE AND THE SECRET IN PARAGRAPHS 3.46, (PL4) ADJUSTMENT. CONNECT THE LOW SIDE OF THE SIBNAL GENER-ATOR TO CHASSIS.

Fig. 51. Radio Receiver BC-683-A: Location of Alignment and Tuning Controls

MECTED -5 DA

- (l) Adjust the ₱ (primary) and s (secmary) adjusting screws in tuning unit LCU2A and the single adjusting screw in LCU1A for
- national deflection of the voltmeter.

 (m) Readjust the transmitter and remover to the higher test frequency and trim

 (i.l. C.1.3. and C.1.5 for maximum voltmeter.
- deflection.
 - (n) Check back and forth between the two test frequencies, repeating steps (1) and (n) until no further improvement can be made.
- (n) until no further improvement can be made.
 (o) Restore the receiver to normal and theth the antenna trimmer capacitor as described is Paragraph 19a.
- (6) Emergency Alignment of Discriminasw. Align a discriminator filter unit (FL4) in an mergency as follows:
- (a) Install the transmitter and the retiver in the mounting, with the receiver in the night-hand position.
- (b) Connect the voltmeter (3-volt scale)
- in Fig. 51.

 (c) Disable the automatic volume con-
- tal circuit by short-circuiting resistor R14. Use the short jumper wire with a clip on each end. (d) Connect the 500-micromicrofarad apacitor between terminals 1 and 2 of filter unit
- BLA. (The capacitor reduces the signal input to the intermediate-frequency amplifier sufficintly to prevent limiter action from masking the tutted tuning point in the test.)

 (e) Remove the cover plate from filter
- ELC. (6) The state the cover plate from file
- (f) Turn the SPEAKER switch to ON, 1m the TUNE-OPERATE switch to TUNE, and 1m the SQUELCH switch to OFF. Turn the VOL-100 control to the extreme right.
 (g) Adjust the transmitter for operation
- star the 27-megacycle end of its frequency range and start the transmitter and the receiver. Place the transmitter in the RECEIVER TUNE condition. (h) After the receiver has warmed up.
- carefully adjust the receiver tuning dial for zeroone with the transmitter frequency. Observe that ano-beat occurs at maximum deflection of the

- voltmeter and note the maximum reading.
- Remove the capacitor from FL2A and note the new voltmeter reading. The voltmeter reading with the capacitor connected to
- FL2A should not exceed three fourths of the reading with the capacitor removed. If it does, the capacitor leads are too long, or the clips are not making good contact.
- (j) Reconnect the capacitor to terminals1 and 2 of FL2A.
- 1 and 2 of FL2A.

 (k) Ground terminal 1 of FL4 to the chassis with a short jumper wire. Remove the
- voltmeter from across L1 and connect it between terminals 3 and 7 of filter FLA (10-volt or 30volt scale, + terminal to terminal 3 of the filter). (1) Check the zero-beat setting of the
- dial while observing the voltmeter. The meter should read zero at zero-beat and reverse polaity as the receiver is tuned through the zero-beat point. If this is not the case, align the secondary by adjusting the s (secondary) adjusting screw for zero voltmeter reading.

 (m) Remove the voltmeter from FLA
- and connect it (3-volt scale) between terminals 2 and 3 of tuning unit LCU2A (+ terminal of voltmeter to terminal 3 of LCU2A). Remove the short circuit from resistor R14.

 (α) Adjust the ρ (primary) screw in fil-
- ter FLA for a minimum deflection of the voltmeter.
- (o) Reconnect the volumeter (10 volt or 30-volt scale) to terminals 3 and 7 of FL4 and recheck the adjustment of screw s in FL4 as in step (1). (p) Restore the receiver so normal.
 - 35. Emergency Alignment of Radio Transmit-
- a. General. The test procedures described hercafter are intended to apply when it is necessary to replace one or more transmitter components which are likely to affect alignment of the transmitter tuned circuits and a precision wavemeter is not available for suc. The critical components are: coils 1.101, L103A, L104, L105A, L106, L107, L108, and L110; the ganged adjustable capacitor assembly C105. C113. C115.

ter BC-684-A.

C119, C125, C152, and C156; and trimmer capacitors C107 (if used in the transmitter under test), C114, C116, C120, C126, C133, and C157. Replacement of capacitor C147 or the channel selector assembly also necessitates checking alignment of the circuits. The location of the alignment controls for the transmitter is shown in Fig. 52.

Note: During the following tests operate the dynamotor only when reading the meter or making an adjustment which requires power from the dynamotor. Paragraph 20¢ should be read and understood before the following or other servicing tests are made.

1-Narrow-blade (1/6-inch) screwdriver or, pref-

b. Testing Apparatus Required.

erably, a long-handled hexagon adjusting tool.

1-Rule (6-inches long x &-inch wide).


- c. Preliminary to Alignment. It is desirable to check the operation of the oscillator and metering circuits prior to emergency alignment of the transmitter circuits. This may be done as follows:
- Insert a low-numbered and a highnumbered crystal (preferably Channel 270 and Channel 389) in sockets numbered 1 and 10, respectively, in the crystal operating compartment.
- (2) Set the METER SWITCH to position 2 (first radio-frequency amplifier grid current), rum the TUNE-ANT CUR switch to TUNE, and unlock the channel selector. This is described in Paragraph 21a.
- (3) Press CHANNEL SELECTOR push button no. 1, start the transmitter, and operate the RE-CEIVER TUNE-OPERATE switch to RECEIVER TUNE.
 - (4) Observe the reading on the panel meter.
- (5) Repeat steps (3) and (4) for push button no. 10. If meter readings are noted for both these frequencies the oscillator is operating

d. Emergency Alignment of R-f Amplifer.

- (1) In later transmitters C107 has been omitted, but if there is a C107 in the transmitter under test, see that it is set to the minimum or pacitance position (open end of slot to left as viewed from the front of the transmitter).
- (2) Press CHANNEL SELECTOR push-button no. 10. Set the METER SWITCH to position 3 (grid current of rectifier) and the RECEIVER TUNE-OPERATE Switch to RECEIVER TUNE.
- (3) Adjust the gang capacitor assembly for maximum deflection of the meter.
- (4) Press push button no. 1 and repeat step (3).
- (5) Carefully release push button no. 1, carefully turn the gang capacitor control to the extreme front, and lock the selector unit as also


described in Paragraph 21a.

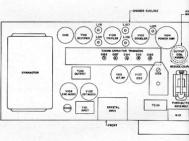- (6) Check the CHANNEL SELECTOR adjusments by pressing the no. 1 and no. 10 push bartons and observing the maximum meet edsettion at each frequency as the gang capacine assembly is rotated slightly against the restoring force of the selector. Do not attempt to retail the capacitor assembly more than a few degree. The tern meets should indicate a nanamum as the three transparent of the capacity of the observations of the capacity of the capacity of the observations of the capacity of the capacity of the observations of the capacity of the capacity of the observations of the capacity of the capacity of the observations of the capacity of the capacity of the observations of the capacity of the capacity of the observations of the capacity of the observations of the capacity of the capacity of the observations of the capacity of the capacity of the observations of the capacity of the capacity of the observations of the capacity of the capacity of the observations of the capacity of the capacity of the observations of the capacity of the capacity of the observations of the capacity of the capacity of the observations of the capacity of the capacity of the observations of the capacity of the capacity of the observations of the capacity of the capacity of the observations of the capacity of the capacity of the capacity of the observations of the capacity of the capacity of the capacity of the observations of the capacity of the capacity of the capacity of the observations of the capacity of the capacity of the capacity of the observations of the capacity of the capacity of the capacity of the observations of the capacity of the capacity of the capacity of the observations of the capacity of the capacity of the capacity of the observations of the capacity of the capacity of the capacity of the observations of the capacity of the capacity of the capacity of the capacity o
- e. Emergency Alignment of Rectifier. Size the filters following the rectifier are primarily intended for selection of the correct crystal has monic frequency, it is important that these cis cuits be disturbed as little as possible when replacing components which affect the alignment.
- (1) If L118 or L119 has been replaced, adjust the tuning slugs to about ¾ inch from the open end of the coil as measured with the scale mentioned in Paragraph 35b.
- (2) Set the METER SWITCH to position 4 (grid current of tripler).
- (3) Start the transmitter at the high-frequency end of its range (by pressing the appropriate CHANNEL SELECTOR DUSH button and



TOP VIEW OF TRANSMITTER, COVER REMOVED, SHOW LOCATION OF GAMMING ADJUSTMENTS AND TURNING

Fig. 52. Radio Transmitter BC-684-A: Location of A

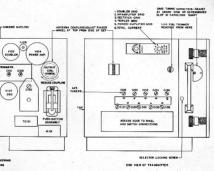

smitter BC-684-A: Location of Alignment and Tuning Controls

of the coil.

throwing the RECEIVER TUNE-OPERATE switch to

- RECEIVER TUNE).

 (4) Adjust C153 and C157, respectively,
- for maximum deflection of the meter.

 (5) Adjust the transmitter to the low-frequency end of its range (by pressing the appropriate CHANNEL SELECTOR push button and throwing the RECEIVER TUNE-OPERATE swirch to
- RICEIVER TUNE) and adjust L119 and L118, in turn, for maximum meter deflection.

 (6) Repeat steps (3), (4), and (5) until no further increase in more deflection can be
- obtained.

 (7) Surt a nearby receiver, throw the BYRAKER wisick 1000, the TUN-10-PERCE which BYRAKER wisick 1000, the TUN-10-PERCE which BYRAKER wisick 1000, the TUN-10-PERCE wisich the SHRAKER wisick 1000, the SHRAKER wi

f. Emergency Alignment of Tripler.

- (i) If L106 or L107 has been replaced, adjust the tuning slugs to about three-fourths inch from the open end of the coil.
- (2) Set the METER SWITCH to position 1 (grid current of doubler).
- (3) Adjust the transmitter at the high-frequency end of its range. (See Paragraph 35c.)
- (4) Adjust C114 and C116, in turn, for naximum deflection of the meter.
 (5) Adjust the transmitter to the low-fre-
- quency end of its range and adjust L106 and L107 for maximum meter deflection. (6) Repeat steps (3), (4), and (5) until
- (6) Repeat steps (3), (4), and (5) until to further increase in meter deflection is obtinable

- g. Emergency Alignment of Doubler.
- (1) If L108 has been replaced, adjust the tuning slug to abour 3/4 inch from the open end
- (2) Set the METER SWITCH to position 5 (grid current of power amplifier).

maximum meter deflection.

- (grid current of power amplifier).

 (3) Adjust the transmitter at the high-frequency end of its range and adjust C120 for
- (4) Adjust the transmitter to the low-frequency end of its range and adjust L108 for maximum deflection of the meter.
- (5) Repeat steps (3) and (4) until no further increase in meter deflection is possible.
- h. Emergency Alignment of Power Amplifier.
- (1) If the L110-L111 coil assembly has been replaced, adjust the tuning slug at the bottom of L110 to the center of its range of varia-
- (2) Set the METER SWITCH to position 6 (total plate and screen current) and make sure the RECEIVER TUNE-OPERATE switch is at OPER-ATE and left there for the following power amplifier tests.
- (3) Set for minimum coupling of L111 to L110 (rotation of the coupling control to the right). Detune C136 by setting it to the maximum capacitance position and detune C127 by adjusting it to the minimum capacitance position.
 (4) Start the transmitter at the high-fire-
- quency end of its range. (For this test the dynamotor must be started by operating a microphone switch.) Adjust C126 for a minimum deflection of the meter. If a tuning point cannot be found, try a different setting of the L110 adjusting slug.
 - (5) Adjust the transmitter to the low-frequery end of its range. Adjust the slug in 1.110 for a minimum deflection of the meere. Adjust this slug by inserting a screwdriver through the hole in the end of the transmitter and turning the slug adjusting gear.

(6) Adjust C126 at the higher frequency and L110 at the lower frequency until no further reduction in the meter deflection can be made ar either end

36. Emergency Sources of Test Tones. In the absence of a test oscillator, test tones can be obrained from a receiver or a transmitter known to be in good condition. The methods of doing this are discussed in detail in Paragraph 39g(6) for the receiver and Paragraph 39g(7) for the transmitter. Signal sources other than a signal generator may be summarized as follows:

a. A-f Signal.

- (1) A good receiver will provide audiofrequency noise when there is no input signal.
- (2) If two good receivers are available they can be used together to provide a beat note. (3) A good transmitter may be used with
- a microphone into which the operator hums or whistles. The resulting audio output can be picked up for test purposes.
 - b. I-f Sional. This may be obtained from a good receiver.
 - c. R-f Signal. This may be obtained from either a receiver or a transmitter.
 - d. Atmospheric Noise. Atmospheric noise may be used as a signal source in the absence of other signal source. Since noise is an indefinite sort of signal (no precise frequency) and theintermediate-frequency band width is considerably wider than the range of frequency which may be heard, the number of circuits aligned by this means should be a minimum.
 - e. Signals from Distant Vehicle. Signals from a vehicle about 10 miles distant may be used as a rough check of receiver sensitivity, particularly when such signals are compared to the noise background when the distant transmitter is off the air.
 - f. Signals from Nearby Vehicle. Signals from a nearby vehicle which is operating into

- Antenna A-83 (phantom), or the antenna shown in Fig. 77, or a 40-watt Mazda lamp, instead of the regular antenna structure, are strong enough for testing purposes.
- 37. Precision Alignment of Radio Receiver BC-683.A
- a. General. Whenever a complete inspection of a receiver is made, check alignment of the tuned circuits in accordance with the following procedure:

b. Testing Apparatus Required. 1-Adapter FT-384-(*).

- 1-Insulated 1/4-inch hexagon socket wrench. 1-Output meter from Test Set I-56-(*), or its
- equivalent. 1-Volt-ohmmeter I-107-(*), or its equivalent
- 1-Signal generator (frequency-modulated). 1-Cornell-Dubilier capacitor. Type 1W, 0.006-
- microfarad, or its equivalent, with suitable 1-IRC resistor, Type BT-1/2, 1000 ohms, or its equivalent, equipped with insulated clip con-
 - Caution: When connecting or disconnecting these wires, turn the receiver off each time to avoid shocks.
 - Adapter FT-384-(*) is a switching box for connecting test meters in various parts of the circuit to facilitate alignment procedure. Photographs and a circuit diagram are shown in the following figures:
 - Fig. 53. Adapter FT-384-(*): Front View. Fig. 54. Adapter FT-384-(*): Back View. Fig. 55. Adapter FT-384-(*): Application to Radio Receiver BC-683-A
 - Fig. 56. Adapter FT-384-(*): Schematic and Wiring Diagram.
- c. Alignment of Discriminator Circuit (FL4) and I-f Oscillator Circuit (LCU4). When aligning the intermediate-frequency amplifier or discriminator, if no shielded room is



Fig. 53. Adopter FT-384/*\ Front View available and disturbing interference from nearby electrical equipment is observed, this inter-

ference can be minimized by connecting a short strap lead from terminal 5 of V3 to C25 (the terminal to which blue-tracer wires are connected), whenever using the intermediate frequency.

- (1) Remove the dust cover from the receiver.
- (2) Make sure that a dynamotor of the cornet primary voltage rating is in place. (3) Loosen the cover plates from LCU1A,

LCU2A, FL1A, FL2A, FL3A, FL4, and LCU4. (The places may be loosened by removing the otter pin at one end.)

Custion: Do not remove the cover from LCITAA

- (4) Set the receiver controls as follows: The speaker switch at on, the sensitivity and VOLUME controls to the extreme right, the TUNE-OPERATE switch at OPERATE the REC switch or OFF until ready, the OUTPUT TO PHONES switch at ON. and the SOUELCH switch at OFF.
- (5) Set up Volt-ohmmeter I-107-(*) as follows: Connect the battery plug attached to the short cable at the bottom of the volt-ohmmeter to a Battery BA-40. Set the SELECTOR switch for -volts and the RANGE switch for 3 V.D.C. Short the COMMON and D.C. VOLTS leads together and tun the ZERO ADI knob for zero indication on the meter. It is advisable to leave Volt-ohmmeter

Fig. 54. Adapter FT-384-(*): Back View

I-107-(*) on for approximately five minutes before using it, to allow the zero adjustment of the meter to become stable. Connect the volt-ohmmeter leads to the v.T.v.M. posts of Adapter FT-384-(*).

- (6) Connect the high side of the signal generator output through the 0.006-microfarad capacitor to the limiter control grid (terminal 6 of FL3A) and connect the low side of the generator to the chassis.
- (7) Adjust the generator for an output of between 1.0 and 2 volts at 2.65 megacycles.
- (8) Plug Adapter FT-384-(*) into receptacle PG1 of the receiver and connect to the battery. Turn the switch of the adapter to DISC (discriminator output voltage).
- (9) Turn the receiver to ON and, after allowing sufficient time for the vacuum tubes to heat, adjust screw s (secondary) in filter FL4 for zero current in the voltmeter. The meter should reverse polarity as s is varied to either side of the zero-current point. The selector switch of Volt-ohmmeter I-107-(*) can be turned from -volts to +volts to note this effect. This is an accurate indication of frequency and can be used as a check during the test. A check may be made from time to time to make sure that this meter still reads zero. If it does not, the signal generator should be readjusted to restore the reading to zero.
- (10) Throw the TUNE-OPERATE switch to TUNE. Adjust the slug in tuning unit LCU4 for



Fig. 55. Adapter FT-384-(*): Application to Radio Receiver BC-683-A

zero-beat. Set the TUNE-OPERATE switch to

- (11) Turn the switch of the adapter to ALRON and adjust the P (primary) adjusting screw in FLA for maximum indication on the volcommerce.
- (12) Restore the adapter switch to DISC and thim the a screw setting for zero meter current. Adjust the signal generator 50 kilocycles above and 50 kilocycles below 2.65 megacycles and make sure that the readings of the volt-ohmeters are approximately the same (but of opposite polarity).
- (13) Vary the signal generator frequency above 2.65 megacycles until the test meter deflection is greatest. Note the meter reading and the generator frequency. The frequency should be between 2.725 and 2.745 megacycles.
- (14) Repeat step (13) below 2.65 megacycles. The meter reading should be within 0.75 vote of the previous reading and the frequency should be between 2.560 and 2.580 megacycles.
- (15) Place the switch of the adapter at CAYH, with the signal generator see for 1.0-volt output at 2.65 megacycles and note the reading of the volt-ohmmeter for later use in testing the intermediato-frequency amplificr.

d. Alignment of I-f Amplifier.

- (1) Reduce the signal generator output to zero and connect its shielded cord to the control grid of the modulator (terminal 4 of V2). Exposed unshielded wires are dangerous and should be kept as short as possible, preferably less than 2 inches, including the clip.
- (2) Adjust the generator to a small output at 2.65 megacycles and adjust it for zero-beat with the intermediate-frequency oscillator when the TUNE-OPWRATE switch is set at TUNE. Then restore the switch to OPERATE.
- (3) With the switch of the adapter at CATH, increase the generator output sufficiently to cause a reading of 0.9 on the volt-ohnunceer. Adjust the generator output from time to time during the following alignment to maintain a meter reading of between 0.6 and 0.9 volt.



Fig. 56. Adapter FT-384-(*): Schematic and Wiring Diagram

(4) Connect the 1000-ohm resistor between

terminals 3 and 4 of filter unit FL3A and adjust the primary of FL3A designated P, for maximum voltmeter reading.

(5) Connect the resistor between terminals

- 1 and 2 of FL3A and tune the secondary of FL3A, designated s, for maximum voltmeter indication.
- (6) Repeat steps (4) and (5) for filter units FL2A and FL1A, respectively. Upon completion of these adjustments, note the signal generator output required to obtain the same meter deflection as in Paragraph 57(C15). It should not be necessary to increase the signal generator output beyond 50 microvolts to obtain this reading.
- (7) Vary the signal generator frequency through the 2.65-megacyele setting and note that the selectivity is approximately symmetrical about the mid-frequency.
- (8) Adjust the generator frequency to 2.65 megacycles and the generator output as required for a meter current of 0.9 volt.
- (9) Double the signal generator output voltage (6 db increase) and determine the frequencies above and below 2.65 megacycles which 0.9 volt is obtained. The band width between the two "6 db down" frequencies should

be not less than 75 kilocycles and the mid-band frequency should be within 5 kilocycles of 2.65 megacycles.

- (10) Repeat steps (8) and (9) for a 1000fold voltage increase (60 db) of generator output. The band width between the two "60 db down" frequencies shall not exceed 350 kilocycles.
- (11) Remove the strap between C25 and terminal 5 of V3.
- e. Alignment of R-f Oscillator (LCU3A) and R-f Amplifier Circuits (LCU1A and LCU2A).
- (1) Reduce the signal-generator output to great and connect is shielded output cord directly to the A and 6 binding posts on the receiver, with short leads. (This will be a test through the whole receiver except the connections from the front a and of binding posts to the regular A and c reminals in the plug RG1. It may be wise, therefore, to cest for conditing between these two sets of terminals.)

 (2) Rotate the uning did to the stop at the
- 27-megacycle end of the scale. The reference line on the dial should be in approximate alignment with the tuning index. If the error is ½ inch or more, repair the unit. This involves removing the front panel and adjusting the glass with the hairline on it. It should be done only if unavoidable.
- (3) Adjust the dial and the signal generator to 39 megacycles.
- (4) Loosen the cover plate (near C24) from C1.3, C1.5, and C1.7 and the cover plate of LCU3A.
- (5) Turn the switch of Adapter FT-384-(*)
- to DISC.

 (6) Place the TUNE-OPERATE switch of the
- receiver at TUNE.

 (7) Adjust the trimmer Cl.7 for zero-beat in the loudspeaker. The (discriminator) volumeter should read zero when the frequency is correct. This is an additional check on the frequency of the intermediate-frequency oscillator.
 - (8) Set the signal generator and the receiver

- dial at 27 megacycles and adjust the slug in LCU3A for zero-beat.
- (9) Repeat steps (7) and (8) until the oscillator tracks satisfactorily at both ends of the band.
 - (10) When the oscillator is satisfactory as took ends of the band, check the 5-3, 3, and 90-ben ends of the band, check the 5-3, 3, and 90-ben engacycle points also. Zero-bear should be charted within one-half dial division at each of these frequencies. If tracking at these frequencies is not assisfactory repeat step (7) using 58 mega-cycles and step (8) using 28 mega-cycles. After the dial tracking is regarded as strikatory, rake care to avoid rouching C1.7 and the slug of LCUAA, when makine further advisatories are sufficiently assistant to the control of the control
- (11) Turn the switch of Adapter
 FT-384-(*) to CATHODE and restore the TUNE-
 - (12) Increase the signal generator output sufficiently to cause a meter reading of 0.9 vol. Adjust the generator during the course of the following procedure to maintain a reading of between 0.6 and 0.9 volt on the meter.
- Note: During the final alignment adjustments is usually impossible to keep the meter deflection below 0.9 volt by reducing generator output. Under these conditions modulate the generator with 100 cycles and a frequency swing of ± 15 kilocycles. Connect the output meter of Tex Set 1-56 (*) to Adapter ET-384 (*), and speplement the test meter deflection by observing the output meter deflection.
- (13) With the signal generator at 39 megacycles, tune the receiver dial for zero-beat at 39 megacycles. Adjust, in turn, trimmer capacitors C1.5, C1.3, and C1.1 for maximum test meter deflection.
- (14) Adjust the generator and the receiver to 27 megacycles as in step (13).
 (15) Adjust, in turn, the slugs in the
- (13) Adjust, in turn, the slugs in the LCU1A and LCU2A shield cans for maximum deflection of the meter.
 - (26) Readjust the trimmer capacitors at 39 megacycles and the inductance trimmers at 27 megacycles alternately until no further improvement can be obtained.

f. Check of Sensitivity and Stability.

- (1) Set the signal generator to 39 megacycles and adjust the receiver to zero-beat at 39 megacycles. Then reduce the signal generator
- to zero output.

 (2) Switch the squelch control to on and adjust the SENSTITITY control so that the CALL
- SIGNAL lamp is barely extinguished.

 (3) Increase the generator output sufficiently to illuminate the CALL SIGNAL lamp. A signal of 1.0 microvolt or less should suffice
- signal of 1.0 microvolt or less should suffice.

 (4) Repeat steps (2) and (3) at 27 mega-
- cycles.

 (5) Set the signal generator to give 3 microvolts output at 39 megacycles. It should be possible to extinguish the CALL SIGNAL Jamp by
- turning the SENSTRIVITY control to the left. Repeat this test at 27 megacycles.

 (6) Throw the TUNE-OPERATE switch to TUNE and adjust the tuning dial for a low-
- pitched beat note.

 (7) Vary the signal-generator output from about 1.0 to 1000 microvolts. The pitch of the beat note should remain within audibility over the entire range of signal voltage.

g. Output Power Measurement.

- (1) Adjust the signal-generator frequency to 27 megacycles and 1.0-microvolt output.
- (2) With the SPEAKER switch at ON, and the TUNE-OPERATE switch at TUNE, set the OUT-PUT TO PHONES switch to ON, and the SQUELCH switch to ON. Turn the SENSITIVITY and VOLUME controls to the extreme right.
- (3) Tune to zero beat with the signal generator and operate the TUNE-OPERATE switch to OPERATE. Turn the SPEAKER switch to OPE.
- (4) Modulate the signal generator with 400 cycles with a frequency deviation of 15 kilocycles and read the output meter. The meter should read over 18 volts.
- Noise Test. With the signal-generator output at 1.0 microvolt, remove the modulation

from the signal. The output meter should not read more than one fifth of the reading obtained in Paragraph 37g(5).

i. Check of Limiter Action.

- With conditions as in Paragraph 37g, increase the signal-generator output to 10 microvolts and observe the reading of the output meter.
- (2) Increase the signal-generator output to 100, 1000, and 10,000 microvolts successively. The voltmeter reading should stay within ± 5 volts of the reading obtained in (1).
- j. Volume Control. Remodulate the signal with 400 cycles with a frequency desization of 13 kilocycles and 1.0-microwsi input, and gradually kilocycles and 1.0-microwsi input, and gradually formate the vouxient control to the left. The control to the signal of the control to the control to the left. The control to the

Precision Alignment of Radio Transmitter BC-684-A.

a. General, Whenever a complete inspection of a transmitter is made, check alignment of the tuned circuits as follows:

b. Testing Equipment Required.

- 1—Antenna A-83 (phantom), or an artificial antenna (Fig. 77), or, if radiation is permissible, a vehicle antenna of correct dimensions (including lead-in and ground).
- 1—Sensitive precision wavemeter, 4- to 20-megacycle range.
 1—Narrow-blade (1/6-inch) screwdriver or long-
- handled hexagon socket wrench for adjusting the trimmer capacitors and coil slugs. 1—Ye inch screwdriver for locking the selector,
- etc.

 1-6-inch rule (narrow blade).

1—Cord CD-786 for connection of the transmitter under test to the power supply through a convenient mounting or equivalent.

c. Preliminary to Alignment.

- Throw the transmitter switch to off, the receiver tune-operate switch to operate, and the tune-ant cur switch to tune.
- (2) Insert Crystal Holder FT-241-A, Chanred 700, into socket no. 1 and Crystal Holder FT-241-A, Channel 389, into socket no. 10 in the crystal operating compartment. If these particular crystals are unavailable, others within five channels of these may be used.
- (3) Remove the top and bottom cover plates from the ransmitter and by the transmitter on its back so the bottom and top sections are accessible. Plug one end of Cord CD-786 into the left end of the transmitter and the other end into the left connector of the mounting which is connected to a large 12- or 24-volt battery supply. Make sure a dynamotor of the correct input voltage rating has been inserted in the transmitter.
- (4) Unlock the channel selector (see Paragraph 21a) and then set the gang capacitor for minimum capacitance (plates all out).

d. Alignment of First R-f Amplifier.

- Set the METER SWITCH to position 2 (grid current in the first radio-frequency amplifier) and turn the TRANSMITTER switch to ON.
- (2) Set C107 to the minimum capacitance position (open end of slot at left as viewed from front of the transmitter).

Note: Capacitor C107 has been omitted from later transmitters.

(3) Press push button no. 10 and start the dynamous by placing the succurse TUNN-OFFE-ATE switch on RECEPUR TUNN. If the oxillator and meeting circuit are working, the meter will deflect, indicating current in the first radio-frequency amplifier gel circuit. Stop the dynamotor by by throwing the RECEPUR TUNN-OPERATE switch to or DERATE. Do not let the dynamotor run for long periods of time during the following tests.

- (4) Set the METER SWITCH to position 5 (grid current in rectifier).
- (3) Start the dynamotor (auckinvar Tutsdoppaners switch to scillurar Tutsdoppaners switch to scillurar Tutsdoppaners of the space and observe the relative position of the capaction places. Rorate the gang capacitor by inserting a screwdriver in the slot on the end of the gang capacitor shaft (located near the handle on the right end of the transmitter) or by the associated small knob.
- (6) Press push button no. 1 and repeat step (5). The observed rotation of the gang capacitor in passing from no. 10 to no. 1 should be at least 75 per cent of the total possible rotation.
- (7) Carefully release push button no. 1, turn the gang capacitor to the extreme right, and lock the selector unit.
- (8) Stare the transmirer (dynamous), Check the selector adjustment by pressing the no. 1 and chen the no. 10 push button. Observe the maximum meter deflection at each frequency as the gung capacitor is warted slightly against the control of the c

e. Alignment of Rectifier.

- Set the METER SWITCH to position 4 (grid current in tripler).
 Adjust the tuning slugs in L119 and
- L118 to about ¾ inch from the open end of the coils. This may be measured with the 6-inch narrow blade rule inserted in the open end of the coil form.
- the coil form.

 (3) Sec C153 and C157 to the mid-capacitance position (open end of slot toward rear of

set).

Note: Steps e(2) and e(3) are unnecessary if there is reason to believe that there has been no major change in the coils or capacitors in this stare.

(4) Adjust the wavemeter to one sixth of the output frequency (38.9/6 = 6.48 megacycles) and place the pickup coil near L118 and L119.

Caution: The wavemeter may affect the tuning of L118 and L119 if it is coupled too closely to these coils.

(5) Press push button no. 10, start the dynamotor, and adjust C153 and C157 for a maximum deflection of the transmitter panel meter at the wavemeter frequency. Take care that the circuits are being tuned to the correct frequency. Wavemeter resonance is indicated by a dip in panel meter reading. If the circuits cannot be raned, try a different setting of the L119 and L118 tuning slugs. Repeat this procedure until a panel meter deflection is obtained, and with the wavemeter determine the frequency to which the riscuits are puned. If the tuned frequency is higher than the correct frequency, increase the tuning inductance or capacity, or both; if the tuned frequency is lower than the correct frequency, decrease the tuning inductance or capacity, or both, until the correct frequency is obtained. The transmitter employs copper tuning slugs in the coils and, therefore, the coil inductance is decreased as the slug is inserted farther into the coil winding.

(6) Press push button no. 1 and adjust the slugs in L119 and L118, respectively, for maximum deflection of the panel meter. Do not adjust C153 and C157. Check the frequency being unsed (270/6 = 4.50 megasycles) with the wavermeer and proceed as in step (5) if the frequency is incorrect.

(7) Repeat step (5) (adjusting only the capacitance trimmers on button 10) and step (6) (adjusting only the coil slugs on button 1) until no further adjustment is required. In some cases where the circuits do not appear to align

properly at both ends of the band it may be desirable (with the MRTER, SWITCH in position 3) to adjust and look selector button 3 at some frequency near the middle of the band (say 33 megacycles) and align between buttons 10 and 5 to get the coil slugs and capacitors near their correct positions. Then finally align between buttons 10 and 1 as described.

f. Alignment of Tripler.

 Set the MEYER SWITCH to position 1 (grid current in doubler).

(2) Adjust the tuning slugs in L106 and L107 to about ¼ inch from the open end of the coils.

(3) Set C114 and C116 to the mid-capacitance position (open end of slot toward rear of set).

Note: Steps f(2) and f(3) are unnecessary if there has been no major change in the coils or capacitors in this stage.

(4) Adjust the wavemeter to one half of the output frequency (38.9/2 = 19.45 megacycles) and place the pickup coil near L106 and L107.

(5) Press push button no. 10, start the dynamotor, and adjust C114 and C116 for a maximum deflection of the panel meter at the wavemeter frequency. Take care that the circuits are being tuned to 1945 megacycles. If the circuits cannot be tuned to the proper frequency, try a different setting of the L106 and L107 tuning slugs.

(6) Depress path botton no. 1 and adjust the graph of the meter. Check the frequency being fluction of the meter. Check the frequency being tuned (27.0/2 = 13.5 megacyles) with the wavement. If the frequency is incorrect, it will be necessary to recheck the frequencies to which the rectifier stage has been aligned in accordance with Paragraphs Sec(4) and 38e(6).

(7) Repeat step (5) (adjusting only the capacitance trimmers on button 10) and step (6) (adjusting only the coil slugs on button 1) until no further adjustment is required.

g. Alignment of Doubler.

- (1) Set the METER SWITCH to position 5 (grid current in power amplifier).
- (2) Adjust the tuning slug in L108 to about 3/4 inch from the open end of the coil.

Note: This step is unnecessary if there has been no major change in the coil or capacitor in this stage.

- (3) Press push button no. 10, start the dynamotor, and adjust C120 for a maximum deflection of the meter. If a runing point cannot be found, try a different setting of the L108 tuning slug. Prequency measurements are not required in this stage if the alignment of the preceding circuits has been done correctly.
- (4) Press push button no. 1 and adjust the slug in L108 for a maximum meter deflection.
- (5) Repeat step (3) (adjusting only C120 on button 10), and step (4) (adjusting only L108 on button 1), until no further adjustment is required.
- (6) Replace the bottom corer plate of the transmitter and firm all alignment adjustments previously mode, the specific the procedure described in Paragraphysis (f. p. and g. The bottom corer makes only such as the procedure critical expactions or indistances and so only small changes in the trimmer capacitors or coil align will be required. They are necessary, however, if most satisfactory performance and tube life are to be obtained.

b. Alignment of Power Amplifier.

- (1) Set the MHTER SWITCH to position 6
- (total plate current).
 (2) Throw the RECEIVER TUNE-OPERATE
 - (2) Infow the RECEIVER TUNE-OPER switch to OPERATE.
- (3) Adjust the coupling of L111 to L110 under the center of coil L111 is opposite the top of coil L110 as seen through the vertical slot in L110. This may be accomplished by rotation of the haurled finger wheel accessible through a rectangular hole in the right end panel. (See Fig. 52.)

- (4) Connect an antenna (artificial or red; see Paragraph 386) to the transmitter. (Duning manufacture this stage is adjusted with the attificial antenna (Fig. 77) plugged into the a and c posts on the front panel of the tranmitter.)
- (5) Press push burton no. 10, plug in microphone, and start the dynamotor by operating the microphone switch. Immediately adjust C126 on top of the selector unit for minimum deflection of the panel meter (minimum plate current).
- (6) Adjust antenna trimmer capacitor C136 (marked as no. 10 on the right-end panel of the transmitter) for maximum antenna current in the artificial antenna meter.
 Note: If an Antenna A-83 (phantom) or a real
 - antenna is used for these coupling adjustments it will be necessary, in order to have an indication of antenna current, to throw the TURN-ANT CUR switch to ANY CUR and observe the deflection of the panel meter. Restore the TURN-ANT CUR switch to the TUNE position whenever adjustments are to be made to capacitor C126 or to the inductance trimmer of L110.
- (7) Adjust the coupling between L110 and L116 maximum antenna current, then reduce the coupling to lower the antenna current to approximately 60 per cent of maximum and readjust the antenna capacitor, C136, for maximum antenna current.
- (8) Press selector button no. 1 and adjust the tuning slug (inductance trimmer) of L110 for minmum place current (with the TUNEANT CUR switch at TUNE). The tuning slug is operated by a toothed wheel which is turned by inserting a screwdriver through the hole opposite the bottom of L110 in the right-end panel of the transmitter.
- (9) Adjust the antenna trimmer, C127 (no. 1), for maximum antenna current.
- (10) Shift alternately between selector buttons no. 1 and no. 10, making the proper adjustment of L110 and C126 for minimum plate current until no further adjustment of L110 and

C126 is required. When on button no. 1, adjust the tuning slug L110 for minimum plate current, and adjust the antenna trimmer, C127, for maximum antenna current. When on button no. 10, adjust the trimmer capacitor, C126, for minimum plate current and adjust the antenna trimmer. C136 for maximum antenna current.

mer, C156, for maximum antenna current.
As the minimum meeter reading may not be sharply defined when the inducance trimmer it among, it is sometimes easier to adjust the capacity trimmer. L126 for minimum place current when on selector branen no. 10, then operate selectors branen no. 10, and again and just C166 for minimum place current. Then adjust the inductance trimmer by a few unrus and repeat the province already outlands, noting the position of doctance trimmer by a few unrus and repeat the province already outlands, noting the position of doctance trimmer of L110 new say or the other unrush of the contract of the contract

The radio-frequency stages have now been ganged and should track satisfactorily at all frequencies.

i. Coupling to the Antenna Circuit, When

the procedure in Paragraph 386 has been propcriy accomplished, the transmitter is ready for coupling to a suitable antenna. The method of making coupling adjustments is described in Paragraph 21a.

 Location of Trouble in Radio Receiver BC-683-A.

a. General. The following tests aid in isolating the source of trouble. To be effective the procedure should be followed in the order given here. A faulty receiver will be referred to hereafter as the "trouble" receiver.

Refer to the following figures to aid in the locating of trouble in the receiver:

Fig. 51. Apparatus Location Diagrams. Fig. 51. Location of Alignment and Tuning Controls.

Fig. 57. Voltage Diagram. Fig. 58. Resistance Diagram. Figs. 43, 72. Wiring Diagrams. Remember first, servicing procedure should cause no further injury to the receiver. Second, trouble should be localized to a single stage or circuit. Third, the trouble may then be isolated within that stage or circuit by appropriate voltage, resistance, and continuity measurements. The relationship of the various steps of this suggested procedure to these considerations, graphically illustrated in Chars 2 and 3 at the end of

Paragraph 39, may be summarized as follows: The purpose of inspection is to locate any visible trouble. Through this inspection alone, you may frequently discover the trouble, or determine the stage in which the trouble exists. This inspection is valuable in avoiding additional damage to the receiver which might occur through improper servicine methods, and in

forestalling future failures.

The power supply test prevents further damage to the receiver or the dynamotor from certain possible short circuits. Since this test gives an indication of the operation of the dynamotor and filter circuits, its function is not merely preventive.

The operational test is important as it frequently indicates the general location of the trouble. In many instances the information gained will determine the exact nature of the fault. To utilize this information fully, interpret all symptoms in relation to each other.

The principal advantage of the signal tracing method is that it usually enables you to localize a trouble accurately and quickly to a given stage when the general location of this trouble is not immediately evident from the above tests.

In all these rests the possibility of intermittents should not be overlooked. If present, this type of trouble may be made to appear in most cases by tapping or jarring the set. It is possible that no crouble will be found in the receiver itself but that the crouble is in the installation (mounting, interphore system, or vehicle), or, possibly, is due to external conditions. In this event, test the installation, if possible.

 General Precautions. Whenever a receiver is to be serviced, observe the following general precautions very carefully.

place.

- With the cover removed, dangerous voltages are exposed when the set is operating.
- (2) Whenever a receiver is suspected of being in trouble, make the inspection and power supply test. Be sure to remedy the cause of any abnormal heating before continuing the procedure.
- (3) Don't allow the dynamotor to run for any appreciable period of time at the start of the inspection until you are sure there are no short circuits which will cause burning of receiver parts.
- (4) When making resistance and continuity measurements, first remove the power plug and dynamotos.
- (5) Don't remove the shield can of the tuned units (LCU or FL) from any unit unless you definitely know that trouble exists within that unit. Whenever one part of the tuned circuit is replaced, realign the unit.
- (6) Whenever you suspect intermittent trouble, make a thorough check of wiring and parts. In many cases you can make intermittent troubles appear by jarring the receiver.
- (7) Take care, when inspecting wiring and soldered connections, not to damage the insulation. Don't leave the insulation in a broken or frayed condition. Don't pull or bend wires unnecessarily, nor pry cable open to trace wiring.
- (8) Don't remove more than one vacuum tube from a receiver at one time. Remember to return each tube to the socket from which it was removed, unless it is defective.
- c. Inspection. When a receiver is brought in from the field for check or repair, remove the cover and make the following inspection.
- (1) Examine for burnt insulation and resistances. Examine for wax leakage and any discoloration of apparatus and wire. Notice any odor caused by overheated apparatus.
- Note: These symptoms may have been caused by a trouble previously repaired and serve only as a guide. In general, confine examination to

- s parts readily visible with the cover removed.
 Usually more harm than good will be caused by
 the removal of the front panel, the FL or LCI
 can covers, and other enclosed parts. Trouble in
 these parts should be localized by signal tracing
 and voltage and resistance measurements.
 - (2) Inspect for broken connections to tube sockets, plugs, and other apparatus as well as for defective soldered connections. Examine for bare wires touching the chassis or other wires.
 - (3) Be sure that the labels on the tubes in turnious sockets correspond to the correct tube numbers given in the technical manual for these positions. Replace any tubes which have the wrong numbers. Inspect for loose tube sockets.
 - (4) Inspect the active and spare fuses. Check carefully for short circuits whenever a receiver with a blown fuse is encountered.
 (3) Inspect the selector mechanism for
 - loose or bent parts. Be sure that the dial turns smoothly and that the push buttons operate satisfactorily.

 (6) Inspect the power plug and replace of
 - repair it if there are any bent or broken prongs

 (7) Inspect for loose or missing screws, especially those which fasten the tube sockets in
 - d. Power Supply Test. This test assumes that a voltmeter of at least 1000-ohms-per-volt with a range of at least 250 volts, and an ohmmeter, are available.
 Throw all switches to OFF, or downward. Re-
 - move the cover from the receiver for the following procedure.
 - The dynamotor marking must agree with the battery voltage available.
 - (2) Remove the dynamotor and examine it for loose or badly worn brushes and worn or dirty commutators. Test the continuity of the dynamotor plug. Clean and replace the dynamotor in the set.
 - (3) Connect the appropriate battery to the

receiver, using Mounting FT-237-(*) or Cord CD-786.

CD-786. (4) Throw the SPEAKER switch to ON.

- (5) Place the volumerer across C25 (the posterie side should go to the terminal to which the write with the red reacer is attacked). Turn the power switch to to Nove that the meet red incise issuediately about volume the worth is turned on. If a bear not, cut the server of switch go appearance of the server of switch goal and also, check the worlage disheler, the dynamotor, and the associated copies ment. A how reading of the volumerer rany in dictor a faulty dynamotor or a short circuit in the system.
- (6) If the dynamotor fails to start or if the fuse blows, turn the set off, and inspect the dynamotor and the associated equipment, as well as the fuse, plug PG2, the filament wiring, etc.
- (7) Assuming that the dynamotor starts correctly and that the voltage is satisfactory, inspect the inside of the receiver with the dynamotor running. See that no sparks occur and that nothing smokes. Stop the dynamotor immediately and repair the fault if trouble is indicated.
- (8) After the dynamotor has been running for a few moments, feel the tubes cautiously to see if they are all warm. No other tube should be a har as Yu, which is a YT-117-6, (6V6-GT) rube. No tube should remain cold. If a rube we have a seen as a few should remain cold. If a rube we have a seen as the should remain cold. If a rube we have a seen as the should remain cold in the socker in question and examine the width the tube socker in question and examine the socker consecution of the socker consecution. If there is no writing trouble and the tube does not warm up, test it (or replace it if no vacuum-rube cere set is available).
- e. Vacuum Tube Testing Procedure. As the space around a vocum tube is often small it is desirable either to use a tube extractor or to rook the tube with the fingers at the rop while pushing it up gently from the bostom. To rest a vacuum tube, use a rest or if available, if not, try the tube in a receiver which is operating satisfacsorily. If snother receive is not available, try replacing the tube by another one.

- f. Operational Test. To make an operational test, you will need a header and a weak signal between 27 and 39 mergeryles. A signal processor of the signal processor of the signal processor of the signal processor of the signal source. The transmitter requires on metallic connection with the receiver. A second receiver with a lead to brigg the radio frequency to the A (antenna) post of the receiver under test is satisfactory, See Banagarsh 390f.6 (cc).
- Serious distortion and abnormally low output are trouble indications. Compare with a good receiver for output, if the condition of the trouble receiver permits. Irregularities of operation help to localize the trouble. Operating personnel may supply useful inpelementary data.
- Turn the trouble receiver to ON and allow it sufficient time to warm up. All other switches should be at OFF (down).
- (2) CALL SIGNAL Lamp. With the SQUELCH switch at OFF, the CALL SIGNAL lamp should be lighted.
- (3) Noise from Loudspeaker. Turn the SPEAKER switch to ON, and with the VOLUME control turned to the extreme right, listen for a rushing noise from the loudspeaker.
- (4) VOLUME Control. The speaker output should vary smoothly from maximum until the noise has vanished at the extreme left position of the control.
- (5) Headset Sidetone. With the OUTPUT TO PHONES switch at OFF, plug the headset into one of the PHONES jacks. There should be no sound in the headset.
- (6) Noise in Headses. With the VOLUME control adjusted for normal output from the speaker, turn the OUTPUT TO PHONES switch to ON. There should be a rushing noise in the headset.
- (7) Noise in Headset, Second Jack. Repeat step (6) for the second PHONES jack.
- (8) Headset Volume. Turn the SPEAKER switch on and off. The headset volume should remain constant if R30 is intact.

- (9) Turn on a source of radio-frequency signal and wait for it to warm up.
- (10) Beat-Note Indication. Now place the TUNE-OPERATE switch at TUNE. Roughly check the tuning of the receiver, both manual and pust-button, against the radio-frequency test signal, using the beat note produced by the intermediate-frequency oscillator as a tuning indication. The dial should curn freely.
- (11) Beat-Note Indication, with Squelch.
 With the SQUELCH switch at ON and the SENSITIVITY control adjusted for maximum sensitivity (full right rotation), repeat the beat-note test at one frequency.
- (12) Squelch Operation. With conditions as in (11), the CALL SHONAL Imps should light when the signal is tuned out, turn the sansarrown control on the left to reduce the sensitivity until it does. The noise from the loudspeaker should cease whenever the CALL SHONAL lamp is extinguished. When the signal is runed in again the lamp should light.
- (13) Sensitivity Control. Reduce the signal, with conditions as in (12), just short of the frequency where the CALL SIGNAL lamp would go out. Turn the SENSITIVITY Control to the left and the lamp should go out.
- (14) Intermittents. Test the receiver for intermittents by jarring it while listening to a beat note.
- (15) Tests Involving Transmitter and Receiver. If the tests are being made in a mounting with a transmitter as a source of radio frequency, the following checks may be made quickly:
- (a) Disabling Action.—Turn the transmitter RECEIVER TUNE-OPERATE switch to OPER-ATE. Pressing the microphone button should cut off the rushing noise in the receiver.
- (b) Sidetone.—Plug into either PHONE jack and set the SIDBTONE control on the right end of the transmitter (Fig. 14) to give sufficient headset volume. Sidetone should be heard when someone is speaking into the microphone.

g. Signal Tracing.

(1) General. Signal tracing tests require one of the following signal sources, listed in

order of preference:
A signal generator.

A good receiver. (See (6) of this paragraph for instructions.)

A good transmitter (provides audio and radio

A good transmitter (provides audio and radio frequencies only). (See (7) of this paragraph for instructions.)

Caution: When connecting or disconnecting these sources, turn the receiver off each time to avoid shock or equipment damage.

You will also need a voltmeter (not less than 1000-ohms-per-volt), an ohmmeter, and a headset. If no vacuum-tube test set is available, check the tubes in a good receiver, or substitute new tubes. (See Paragraph 39e.) This recommended procedure begins at the output and works back. For the location of parts, see Figs. 43, 45, 46, 51, and 72. An output meter plugged into one of the PHONES jacks, as described in Paragraph 33r(3), or an alignment meter bridged across L1 as described in Paragraph 33e(1), helps greatly in judging the performance of the receiver. If a signal generator having a 1.0-volt output at 2.65 megacycles is used, test the discriminator circuits, as described in step (3)(i), as soon as step (3)(b) is completed. In this event, apply the signal generator output to the grid of the limiter (terminal 4 of V6). In all other cases, make this test in the following order:

(a) At the beginning of the test, turn all switches to OFF (downward), and release all push buttons.

(b) Don't remove the thirld can of a tuned unit until the trouble has been traced to that particular unit. Don't remove the front panel of the receiver more often than necessary. Don't damage the wiring by puthing it back and forth during inspection. Do at little damage to the receiver as possible, Take it east;

(c) Use a dynamotor known to be in good condition, and of correct voltage, and place it in the set before the test.

(d) Except as otherwise noted, ground

one side of the signal generator and connect the

other side to the receiver being tested. (e) Note the volume, and listen for serious distortion from the loudspeaker at the various points in the signal tracing procedure. Ex-

perience helps. If possible, compare with a receiver known to be in good condition. (f) Check the wiring and soldering in

each stage as you proceed. (g) Misalignment of one or more stages

of the receiver will cause reduced output. Misalignment of the radio-frequency oscillator may,

however, prevent any output. (h) In this outline, "no signal" or "no beat note" means either no signal from the loudspeaker, a signal that is weaker than it should be,

or a seriously distorted signal. (i) When trouble is localized in a given wage, first test the tube if such a test is indicated

in the procedure, then the voltage, and finally the resistance (Paragraph 39b(4)), at the tube socket of that stage. (j) Trouble in a circuit or stage may not

show in voltage and resistance measurements at the tube socket. Hints included in this section are merely a guide and should suggest other procedures, such as voltage and resistance measurements on individual parts.

(k) Remove only one tube at a time when testing. Check the number of the tube, test it, and return it to its proper socket before another tube is removed

(1) If the receiver appears to be good, test the control circuits of the associated transmitter for short or open circuits. Check the wiring in Mountine FT-237-(*), as well as the remote circuit wiring. (m) It frequently helps to connect (with

a clip lead) terminal 5 of V3 to the negative side of C25 (to which blue-tracer leads are attached) when performing the audio- and intermediare-frequency tests outlined in Paragraphs 390(2) and (3). This stops the radio-frequency oscillator and reduces interference. Be sure to temove this clip lead before proceeding with the tadio-frequency tests.

(n) Each step assumes you have satis-

factorily completed all previous steps. Isolate and clear any trouble located before you proceed with the next step.

(o) When you have found all sources of

trouble, follow the procedure for routine check of the receiver as described in Paragraph 30.

(2) A-f Tests. For reference to audio-frequency-test signal sources, see Paragraph 39g (a) Secondary of T1 (Speaker Circuit). -Throw the SPEAKER switch to ON and connect

an audio signal through a series capacitor to the blue-brown tracer (fifth terminal counting from the front panel) on the output transformer T1. Listen for noise output in the speaker. Notice that it is not necessary to remove the front panel in order to gain access to the terminals of trans-

former T1. The volume of noise will be very low.

If no output is heard, check the circuit elements such as the SPEAKER switch D3, the output

transformer, the loudspeaker, etc. Note: In replacing the front panel (if it has been removed) be sure that the wires are all

pushed down beside the potentiometers P1 and P2 and preferably ried in place. (b) Secondary of T1 (Phones Circuit) .-Throw the OUTPUT TO PHONES switch to ON and

connect the signal to the blue-green tracer on the output transformer T1 (third terminal counting from the front panel). Try the headset in both puones jacks. Noise should be heard when the headset is plugged into either jack. If no signal is heard, remove the front panel and test (by resistance measurements if possible) such items as resistors R22, R23, and R33, switch D2, the iacks, and reeminals 12 and 14 of PG3 and I3. lacks and headsets may be at fault, or a permanent ground may exist on the receiver disabling lead.

(c) Primary Circuit of T1.-Place the audio signal on the blue-vellow tracer (second terminal counting from the front panel) on the output transformer T1 and listen for the signal from the speaker or headser. If no signal is present. C33 may be shorted or terminals 16 and 17 of plug PG3 may not be making good contact.

(d) Terminal 5 of V8 (Grid of Second Audio Amplifier) .- Turn the receiver on. Put the signal on terminal 5 of V8. Listen for output in the speaker. If there is no output, test the tube and the voltages at the socket terminals (see Figs. 57 and 58). C21, R19, or R18 may be faulty. Check continuity to terminals 5, 6, and 10 of PG3 or J3:

(e) Terminal 2 of V10 (Plate of First Audio Amplifier) .- Introduce the signal at terminal 2 of V10, and listen for a signal from the loudspeaker. If there is no signal, R18, C19, or C21 may be at fault. Check terminals 5, 6, and 10 of PG3 or J3 for continuity.

(f) Terminal 1 of V10 (Grid of First Audio Amplifier) .- Put the signal on terminal 1 of V10. Reduce the signal input. If there is no signal from the loudspeaker, test the tube. Circuit elements such as C11, C12, C13, C26, or R10 may be faulty. Note that when the SQUELCH switch is at OFF it should connect ground to R12 -the side away from the tube. (g) Terminal 5 of V10 (Plate of the I-f

Oscillator).-Place the signal on terminal 5 of V10. Throw the TUNE-OPERATE switch to OPER-ATE. If there is no signal from the loudspeaker, R6. C26. C10. or D5 may be faulty.

(h) Junction of C11 and R10.-Put the signal at the junction of C11 and R10. If the signal is not heard from the speaker, R10 or C11 may be faulty.

- (i) Terminal 4 of V7 (Output of the Discriminator).-Place the signal across the output resistance (R81 in series with R83) of the discriminator (terminal 4 of V7). If there is no signal in the loudspeaker, check circuit elements such as V7, C81, C82, R81, R82, R83, or R84,
- (3) I-f Tests. For reference to intermediatefrequency-test signal sources, see Paragraph 39g
 - (a) Terminal 8 of V6 (Plate of the Limiter).-With the intermediate-frequency signal applied through a series capacitor to the place of the limiter (terminal 8 of V6), place the SQUELCH switch at OFF and the TUNE-OPERATE switch at TUNE and listen for a beat note from the loudspeaker. If this bear note is not heard,

note the setting and then vary the slug adjustment in LCU4 to obtain a beat note. If the best note cannot be obtained, such circuit elements as C10, LCU4, FL4, or D5 may be faulty. Retune the slug in LCU4 for a beat note with the intermediate-frequency source after the trouble has been cleared.

(b) Terminal 4 of V6 (Grid of the Limiter).-Put the signal on terminal 4 of V6. If there is no beat note from the speaker, with the TUNE-OPERATE switch at TUNE, test V6 and other circuit elements. Voltage and resistance measurements at the tube socket terminals may be useful. (See Figs. 57 and 58.)

(c) Terminal 8 of V5 (Plate of the Second I-f Amplifier) .- With the signal on terminal 8 of V5 repeat the procedure given for the preceding stage. If there is no signal, FL3A may be misaligned or faulty. If the alignment is not at fault, test such elements as V5, R13, C14, C15 or C7. If the alignment has been altered, re-align FL3A after the trouble has been corrected

(d) Terminal 4 of V5 (Grid of the Second I-f Amplifier) .- Place the signal on terminal 4 of V5. Repeat the procedure which was followed on the limiter stage. If the test of the tube is satisfactory, there may be trouble in circuir elements such as FL2A, C7, or R8.

(e) Terminal 8 of V4 (Plate of the First I-f Amplifier).-Feed the signal to terminal 8 of V4. If no beat note is obtained from the speaker, test the tube. FL2A may be misaligned or may be faulty.

(f) Terminal 4 of V4 (Grid of the First I-f Amplifier).-Introduce a signal on terminal 4 of V4. If no beat note is obtained and the tube is satisfactory, the trouble may be in FL1A, C6, or associated circuit elements.

(g) Terminal 8 of V2 (Plate of the Modulator) .- With the signal on terminal 8 of V2, listen for a beat note from the loudspeaker. If none is obtained, test the tube and make voltage and resistance measurements. (See Figs. 57 and 58.) FL1A may be misaligned or faulty. Check the associated circuit elements.

(h) Terminal 4 of V2 (Grid of the Modulator).-Place the signal on terminal 4 of V2. If a beat note is not obtained, test the tube. The trouble may be in LCU2A. Check for a short

- circuit of C1.5 or C1.6. (i) Terminal 4 of V2 (Discriminator Test) .- With the intermediate-frequency signal still on the grid of the modulator (terminal 4 of V2), measure the voltage across the series combination of R81 and R83 (between terminals 4 and 8 of V7. or between 3 and 7 of FL4). Turn off the intermediate-frequency oscillator by setting the TUNE-OPERATE switch at OPERATE. Align the secondary of FL4 to obtain a zero reading on the voltmerer. As the alignment is varied either way from this point, the reading of the voltmerer should change polarity. In order to test the primary of FLA, connect the meter between terminals 3 and 8 of FL4. Adjust the primary slug of FL4 for maximum reading on the voltmeter. This is not an alignment but merely a check on the alignment capability of this circuit. Leave the circuit in approximate alignment after clearing any trouble that may have been present in FL4 or associated circuits.
- (4) R-f Tests. For reference to radio-frequency-test signal sources, see Paragraph 39g
- (a) Terminal 4 of V2 (Grid of the Modulator). - Apply a radio-frequency signal through a capacitor to the grid of the modulator (terminal 4 of V2). Set the TUNE-OPERATE switch to TUNE. Manually set the dial of the trouble receiver to approximately the frequency of the radio-frequency source and rune for a beat note. If it is impossible to obtain a beat note, either the source of radio frequency is not providing voltage on the grid of V2 or the radiofrequency oscillator of the trouble receiver is not functioning. In the latter case check V3, LCU3A, R4, R5, C5, and associated circuit elements. C1.7 and C1.8 may be shorted. Make resistance and voltage measurements at the tube socket terminals. (See Figs. 57 and 58.) In order to isolate the trouble in the oscillator stage, put the radio-frequency signal on the suppressor grid of the modulator (terminal 3 of V2). If the characteristic no-signal rushing noise is heard from the loudspeaker with the test signal but is

not heard when the test signal is absent, then the oscillator stage is faulty. However, if the oscillator stage is operating but not properly aligned, the rushing noise may be present, but a weak beat note may appear more than one channel away from the proper setting. A realignment of

the oscillator is indicated.

Caution: Any attempt to vary the adjustment of the slug in LCU3A will result in a Change in the tracking of the socillator stage. This stage probably will then require careful alignment. This procedure is described in Paragraphs 34b(5) and 37e. No adjustment of LCU3A and CL7. should be attempted until the method is fully understood.

- (b) Terminal 8 of V1 (Plate of the R-f Amplifier).—Place the signal on terminal 8 of V1. If no beat note is heard in the speaker, test V1. It may be that LCU2A, C1.3, or C1.4 are shorted. Make voltage and resistance measurements.
- (c) Terminal 4 of V1 (Grid of the R-f Amplifier).—Place the signal on terminal 4 of V1 and listen for the beat note. If no beat note can be obtained and the tube is not at fault, check LCU1A, C1.1, and C1.2 for short circuits. LCU2A may be misslipened.
- (d) Antenna Post.—Put the signal on the A (antenna) post. If there is no bear note, LCU1A may be misaligned or faulty. Test the antenna connections to LCU1A.
- (e) Squelch Circuit and Sensitivity Control.—Check these functions as described in Paragraphs f(f2) and f(f3) preceding. If operation of the squelch circuit and sensitivity control is not normal, test V9. Circuit elements such as R15, R16, R17, C17, C18, C20.2, or C12 may be faulty.
- Note: The voltage divider circuits bear an important relation to proper squelch action. See Figs. 57 and 58.
- (f) Tuning.—When all troubles have been removed, the runing for all channels should be checked. If an LCU or an FL unit has been repaired or replaced or if its adjustment has been changed, that unit should be realigned. If several

units have been changed or there is any question of alignment, the whole receiver should be realigned.


- (5) Short Cart. Signal tracing procedure may be simplified by determining at the outset, whether the trouble is in the audio, intermediate, or radio-frequency circuits. This may be determined in the following order:
 (a) A.f. Circuits.—Pura naudio-frequency
 - (a) Not circuits—Fut an audio frequency signal on the output of the discriminator (terminal 4 of V7). If output from the speaker is missing or weak, the trouble is probably located in the audio-frequency circuit.

Caution: Unless you are familiar with these sets, you may fail to recognize a loss of amplification in the set in these tests. It's a good idea to make a comparison with a receiver known to be in good condition.

- (b) If Circuits.—Put an intermediate-frequency signal on the grid of the modulator (terminal 4 of V2). When the YUNE-OPERATE switch is at TUNE, a beat note should be heard. If step (a) gave a beat note but none is heard now, the trouble is probably in the intermediate-frequency part of the circuit.
- (c) Bel Circuits—Place a radio-frequency signal on the A (neurona) post. Tune the receiver to the frequency of the test signal. Throw the SQUELCH with to ON. The squelch circuit should operate satisfactorily with the SINSHTY. TY CONTROL near its minimum or extreme left position. Throw the SQUELCH switch to OFF; a bear one should be heard from the speaker. The tuning dial sering should agree approximately with the test signal frequency. Test the squelch and sensitivity control operation as described in Paragraphs 1/(21) and f/(3) preceding.
- (6) Use of a Second Receiver as a Signal Generator. It you have no signal generator, it will help a lot to have a second receiver handy. Keep it in good operating condition at all times to use as a source of test signals. The audio, intermediate, and radio-frequency signals may be obtained from the following points in the good receiver, in the following manner:

- (a) Audio Trousency Audio-fraquency injust navy be obtained from one of the retotat justs of the good receiver. The vortime count in this receiver may be adjusted to give a usic factory level of no signal noise for use in setting the sudio stages of the rutoble receiver. If the signal strength is too great, the sudio stages of the trudole receiver may be overloaded, thereby giving deseptive results. Connect the 1th of the play no a capacition of 0.001 miterfacts and or great or expectance. Insert the play im soo not of the TROUSE jacks to Ottomia an analist-frequency source. Countex the classist of the two receivers out of the play of the play of the control of the control of the play of the play of the control of the control of the play of the play of the control of the control of the play of the
- (b) Intermediate Frequency.-You may obtain the intermediate frequencies from the secand receiver, with the TUNE-OPERATE switch at TUNE, at terminal 7 of FL4. You can pick up a somewhat higher output on terminal 2 of FL4; use the former (lower level) point for all cases except where the circuits are badly misaligned. In all cases make the connection through a capacitor, preferably 0,001 microfarad or larger, located close to the source of test tone. If you have no capacitor, twist two insulated wires for about 18 inches, making sure that there is no metallic connection between the wires. These two wires (at the far end) form the two ends of the lead which carries the test frequencies. In order to prevent unwanted pickup and singing, combine this lead (in a twisted pair) with the ground wire which forms the circuit return. Mark each wire so it may be identified, equip each end of the pair with clips, and run it directly from the signal source to the point of use, preferably under the bottom of the good receiver (if it is at the left side). Leave the untwisted part as short as possible. This twisted pair for pickup and test frequency will then consist of:
- An insulated wire about 3-feet long used for connecting the chassis of the trouble receiver to the chassis of the source.
 - (2) Another insulated wire about 4feet long cut in the middle and with the two

GAUTION: DAMEROUS VOLTAGES ARE EXPOSED

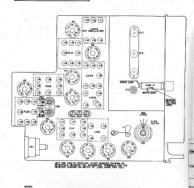

ALL MOLTANDE SHOULD BE MEASURED SCINED THE DESCRIPTO TERMENT. AND THE RECEIVED DISSESS.

ALL SHETCHES EXCEPT THE TANG-OFFMAT AND THE ON-OFF SHOULD BE IN THE TRANSPORTED THROUGH THE TANGENT THROUGH THE TANGENT THROUGH THROU

A MOLITIMEN BYTH AN EXPENDED THE THE CYCLATA AND THE ON-OFF SHOULD BE IN THE COMMISSION SHOP AND ANYTHING PROCESS. A RECOVERY WHICH IS DEPENDED AND RECOVERY MEANING SHOP AND DEPENDED ON THE COLUMN SHOP AND ANY THE STREET, AND ANY THE SHOP ANY THE SHOP

 Employ some seek memb on of on 10 years, 15 from the sattlers con other sattlers washased the majories come sould be adviced to a proportion.
 Accordance requirem that on measurements with a member of 1000 deem mem volt, full-scale majories and/of set needed them the Expected with America.

WOUND TIME VOLTHETER MEASUREMENTS AND RADED ON A VOLT-DAMMETER HIEF OR SOURCEME.


6 MEANS NOT TO EXCEED 0.5 VOLTS ON METER OF 1,003 OHMS FOR VOLT.

PL

HPUT COMESTION *				01 *	PERCENTY	TO OPERATE SOURLES	OUTPUT METER				
TERM.	40	14	-	04555	2.45 MG		LVOLT	IN VOLTS (APPROX.) 6	W- 644		
-						2 VOLTS (MAX)		-	-		
TEN	• •	12					0.05 VOLT (APPROX.)	IS VOLTS (APPROX) 40	0 091		
		-				D J WOLT (MPPROK)			_		
		176	-			A CONTRACTOR OF THE PARTY OF TH	1500 MCROVOLTS (IPPROX.)	16 VOLTS (MPROV. 40	0.00		
		-	-			NOOD MY IMPROVED		-	_		
-		vi	-				SO MEDROVOLYS SMAX.)	IN VOLTS (APPROL) 40	O CP		
						100 UV MAX.)		-			
					39 MC		NOO MICROVOLTE (MPRICE)	HE VOLTE (ANNESE) 45	2 2		
						600 JV (APPROL)					
75796		- 93					100 MCROVOLTS CAPPROX.	IN YOUTS INPRESS OF	O CP		
					-	200.HV (APPROX.)			_		
15.83e	•	- 41	-				I.S MICROYOUTS (APPROX.)	6 VOLTS (\$19900) 40	90 08		
						3.4V (APPROX)			-		
AUT I	w)	90	72.5	menal 5	27MC	Lary OMAGO			_		
	-	-			30 40	1 800	TOVO, T INPUT	- VOLTS (WPMOX.) IS	0 00		
						- 1		20 4	00 0		
				*		- 1		20 * * 10	00		
	-	-						01 25	00		
-		-	-			-			100		
Name .	Ġ	7 10	***	DAMES	1030 OPS. 4		I WO.T .		~~		

- THE DESIGN GENERATOR CONNECTION SHALL ALWAYS BE MADE THROUGH A JOSE OF SERIES CONDENS
 AN APPLY I VOLT OF 2-65 MIGACINGLES BETWEEN TERMINAL A OF VALUED CHARGES TO CRITICAL THE SOLI
 - .. Begin bring that some manager of the freeze white

					70,5	HE 1	f va	DAM	T/ME	100	***	TENNE	841.5	-	_
					600	CHAN I	en,	2.7	V9.7	10	, m	A SUR	(WEN	18	
								12 W	R.T.		r.				
					TERM HOS.	WI	v2	¥3	44	¥5	16	¥7	ve	17	YI
VOLTAGES AT	TERRORALI	OF FL AND	LOU UNITS		1	0.0	920	855	9	1	å	4.00	1	8	70
FL UNIT		-	LOU LINETY		-	2	I.O.	0		٠				0	199
VOLTA:		PERMINE.				145	45	18	15	89	88	8	§	13	
200	105 m		MOR. SOC.	La Calling		in	h	8	in	93	55	ŝ	8	8	A
\$40 FE 5 9 75	OMOTE 61	14	INOTE 5 & 7	BASIL 4)				24	WOLF	84	TEN				
70	17	CON	0	-1	1	000	0 0 0	90	90.00	99 80	0.5	9.5	185 170	90.50	0.5
3	-1	7		-2	4			000	3050	9225	950	20.0	9 0 M	000	90
		LOUBA		-	100					-		_		-	_
	180	1 1	133	18			_								_
		- 4	-0		4000	. 1086	VA.					ers (s		21K (
		5	0	0	77794 MOD .	- 93	**					Tva	100	Ten	1
-1	1		175	100	1	9	0 2	00	8	98	9	9	0	15	0 75
44	40	FERM	0	0	1	0	1	145	1.5	1.5		1 8	150	15	14
0 0	0 0	1	135	146	1	100	7	80.			6.0	B 0	- 00	100	180
60	60	3	- 1	*12		160	75					22	6	0	4
-2	-2				-			-	VOL!	841	TERY	Te		Tes.	
22	22.	LONA	183	192	1	0 0	-2	ins o		907	1.2	155	190	. 80	15
53	13.	3	136	160	5	0	13	-10	2	90	0.5	20	-2	20	160
90 90					i	190	75	0	180			25	6	24	
	Fig. 1981 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1	PL GREET PL GREET		March Marc	No. No.	COLUMN ST TORNING ST TORNI	Column C	Column C		No. No.		Column C	Company	Company Comp	No.

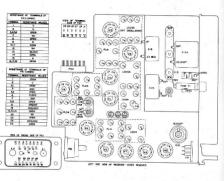

AL RESERVOY VALUE BROWN ARE MEASURED RETHREEN THE RECEIVER CHASOS AND LESSON WIED TERMINAL PICKY.

E. A WHERTON OF A 2015, PRIOR THE INDICATE WALKS SHOULD NOT SE RECEIVED AS 1 HEROTON OF A DEFECTIVE RECEIVEN.

3. OCETIVA DEGREENANTS NAT SE DESCRIVE.

 CESTAIN DECRETANCES MAY BE DESCRIBED INTEGER THE SOCIEMAND DIMENSION OF INTEGER REPORTING DAY THE LARGE APPLIES OF THE RECEIPER. I DECRETANCES ARE DIE TO CAMPE IN INTEGER DAYLOS METABLES, TO COLO THE MINISTRUME. IN SUCH CAMPE THE LIGHT, APPLIES METABLES, TOOL OTHER LIGHT, APPLIES METABLES, APPLIES LIGHT, APPLIES LIGHT, APPLIES LIGHT, APPLIES LIGHT, APPLIES LIG


THE DIMEMOTOR MESTINGS MEASUREMENTS.
 PLACE ALL SWITCHES IN THE "CET" OF

DOMESTIC SHOOTED IN THE COPY OF DOMESTIC AND THE CHIPPY TO PROMES SHOOT SHOULD POINT UP.

4. THEN THE VOLUME AND SENSITIVITY CONTR. TO THEIR HELDRUN CLOCKWISE ROTATION



Fig. 58. Radio Receiver BC-683-A:

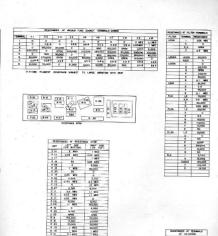



ends connected through a capacitor or wrapped together for about 18 inches where they overlap.

- (c) Radio Frequency.-The radio frequency may be obtained from the good receiver at the suppressor grid of the modulator (terminal 3 of V2). For most alignment purposes, the stray pickup between two receivers placed shour 2 feet apart is sufficient. For signal tracing, more pickup may be necessary. In this event, connection may be made by using a capacitor or two wires twisted together as described in (b). This frequency will be about 2.65 megacycles above the frequency indicated by the dial. Therefore, tune the receiver being tested to a frequency which is approximately 2.65 megacycles above that to which the good receiver is tuned.
- (7) Use of a Radio Transmitter BC-684-A as a Signal Generator. If neither a signal generator nor a good receiver is available, you may use a transmitter in good operating order to provide a tone for tracing signals in the audio- or radio-frequency stages of a trouble receiver.
- (a) Audio Frequency.-If the transmitter is in a mounting, an audio-frequency tone can be obtained from terminal 1 of the terminal strip TS401. You can see this terminal in the base of

the mounting when the door in the mounting at the left receiver position is opened.

- Caution: Use a 0.001 to 1.0-microfarad capacitor in series with the lead, as one side of the audio source is grounded.
- If the receiver is placed in a Mounting FT-237-(*) with this transmitter, throw the OUTPUT TO PHONES switch of the receiver to OFF. Turn the transmitter on. Audio frequencies will be available if the operator presses the microphone button of the transmitter and whistles or hums into the microphone. Use a throat microphone if you have it.
- (b) Intermediate Frequency.-Since no source of 2.65 megacycles is available in the transmitter, no direct method of signal tracing in the intermediate-frequency section is available with the transmitter.
- (c) Radio Frequency.-In general no direct connection between transmitter and receiver is necessary for picking up test radio frequencies for alignment work. In signal tracing where direct connection may be needed, use a shielded wire, with one end connected to the antenna terminal and the other hung near the transmitter. Connect a capacitor in series with this wire to prevent accidental short circuits.

Chart I. Equipment Required for Servicing of Radio Receiver BC-683-A

- 1. Schematic Diagram of Circuit
- 2. Volcage Measurements


Multirange d-c voltmeter of at least 1,000-ohms-per-volt

Maximum range required: 0-250 volts Intermediate range: 0-30 volts approximately Low range:

0-3 volts approximately

- 3. Resistance Measurements Ohmmeter with a maximum range of 5 megohms
- 4. Tube Tests
- a. Suitable tube tester with short circuit tests, or b. A second Radio Receiver BC-683-A in good condition, or c. Complete set of new tubes
- 5. Signal Tracing
- a. Suitable signal generator, or
 - b. A second Radio Receiver BC-683-A in good condition, or
 - c. A Radio Transmitter BC-684-A in sood condition.

RADIO	SE		-A AND	SCR-62	
	Location of Trouble Unknown	Receiver is inoperative, or partially inoperative (signals weaker than normal, etc.), and location of trouble is not known. The sirral tracine to localize	trouble in one stage In case of low signal output, use a volume indicator	When in doubt, compare results with good receiver.	When trouble is localized in one stage:
to Discover All Symptoms	Location of Trouble Suspected	Signal is received satisfactority, but some feature does not operate correctly. Signal is not received satisfactority, but trouble has been localized to	one stage by inspection. (1) Check tube. (2) Messure volence in groce.	(3) Measure resistances in stage (dynamotor removed). (4) Check for open capacitors by bridging suspected unit with most over 100 per	
Test Receiver Thoroughly to Discover 4/1 Symptoms	Oscillation	laspect for: (1) loose counctions. (2) tightness of sockets. (3) tightness of ground connections to chasts.	Localize oscillations with switch in TUNE position by grounding grids of various stages through a 0.1-mf	capacitor When oscillations are localized, test for:	(1) bad resistors (2) open capacitors, (3) bad rades
	Noise	Replace dynamotor if possible, Inspect for wires, broken patts, etc.	Test for: (1) bud tubes (short circuits, ecc.). (2) had resistrate	(3) leaky capacitors. Watch for intermittents.	

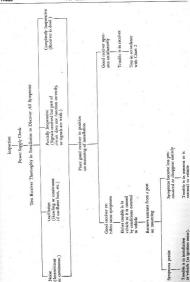

123

40. Location of Trouble in Radio Transmitter

a. General. The following procedure is designed to locate rouble quickly and with as little damage as possible to the transmitter. A report from the operating personnel on the trouble experienced will usually aid in making repairs. Refer to the following figures as an additional aid in locating trouble:

Figs. 47-50. Apparatus Location Diagrams. Fig. 52. Location of Alignment and Tuning

Controls.

Fig. 59. Voltage Diagram.

Fig. 60. Resistance Diagram. Fig. 75. Wiring Diagram.

b. Inspection. Remove all covers from the transmirer and impact for obvious defexts. These may include broken parts, burned resistors. These may include broken parts, burned resistors, because the connection plugs, or loose pieces of wire or metal. Smell for evidence of overheared parts. There may be broken gears, or the rack connecting the selector to the runing capacitors may be out of alignment. Check for loose tubes or looseness in the grap of the socker receptuales on the contact prins of the tubes. Check for loose wires and repair any broken leads. Clear the inside, both top and

Note: If an air hose is used, be sure any water condensed in it is blown out before applying the air stream to the equipment. Use only air intended for cleaning purposes and don't blow hard enough to dislodge or damage any apparatus.

bottom, with compressed air, paying especial at-

c. Preliminary Precautions.

tention to the selector mechanism.

Caution: When the transmitter is operated with covers removed, dangerous voltages are exposed. Be careful.

Never run the dynamotor for long periods in either the RECEIVER TUNE or OPERATE position. The design requirements of the dynamotor are based upon 5 minutes operation with 15 minutes off. In addition to this, prolonged operation of the set may cause objectionable heating effects within the transmitter. Never start the dynamotor with the transmitter ON-OPF switch filament switch). Start the dynamotor with the BERUFER TUNE-OPPERATE SWITCH or the microphone switch after the filaments have been heated for about 5 seconds (by closing the ON-OPF switch).

d. Power Supply Check. Lay the transmitter on its side with the panel up so you can read the meter and see the under chassis parts. Dea't connect a microphone to the set.

Plug in auxiliary Cord CD-786 to connect the battery to the power receptacle on the transmitter. If the dynamotor starts, look for a stuck dyna-


motor relay or shorted relay contacts.

Turn the main on-ore switch to on. The green signal lamp should light. If the lamp does not light, check for a burned-out pilot lamp or loose wiring at retminals 1 and 2 of PGIGI.

Watch carefully for other obvious trouble as soon as the switch is turned on.

If desired, a voltmeter may be connected across the power supply during these tests. Operating the filament supply switch (Paragraph 40c) should not cause an appreciable change in the voltage reading if no trouble is present. If the dynamotor is short-circuited, the main fuse will open or there will be a continuous low-voltage

reading when the dynamotor starts. Assuming that the dynamotor does not start when the filament supply switch is operated and that no other trouble is noticed after operating the switch, connect a microphone to the set. Momentarily operate the microphone push button and note that the dynamotor starts. If the dynamotor does not start, inspect relay \$102 for breakage, contact failure, or defective wiring. Inspect the dynamotor jacks and wiring. Check the dynamotor and also the microphone cord and jack. The dynamotor may start but may indicate by high-speed whine that it is operating at no load. Inspect for an open high-voltage fuse and other open-circuit trouble on the high-voltage supply leads. If the dynamotor starts but operates ar low speed, check for a high-voltage overload. Remove the high-voltage fuse. If the dynamotor still labors, remove the battery cord from the set

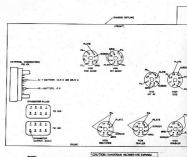


HOTES

L LOCATION CONSISTENCY IN RELIEN OF THERMATTER, EACH SAME WILL TRANSPORT IS CONTRIBUTED IN CHARACTER IN CONTRIBUTED IN

									VOLTAGES AT W	ACIAIN TUB	E SOCKE	T TERM	NALS.	1000	
		MEASURE.	CHENTO	BITH YOU	THE THE C	# 1000 ¢	HES PU	LON I		1	MINISTRA	ENTS YE	N WORK	TUBE V	Ž.
E291, H05.	W964	20W	W03	VID+	WOS	1006	VAC?	1606		TERM NOS.	Acce	Acc	1905	1994	105
	400	400	400					400							
	130	245	190		22										
							-14								

Fig. 59. Radio Transmitter BC-684-A: Voltage Di

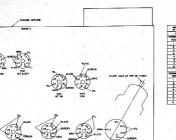

AT PU		TAGES EALS
12,5	VOLT BATT	ERY
MOS.	PG 103	PG 104
	0	12.0
•	٥	12.5
2		12.5
. 4	*22///	4.5
- 6	0."	0
•	-	12.8
7	0	0
	800	0
20.7	WOLF BA	TTERY
HOS-	PG 103	PRIOR
-	0	25.5
1	. 0	12.2
2	12.5	25.5
•	-22	20.0
9	0	0
-	_	12.5
7	2.5	

TOR, OUTS TRACE WHILE PRAYEMITER IS CHEMITING OF CHIEF TO FRAME OF TRACEMITTER.

MALES SHOWN REGARDS OF OF VOLTAGE SUPERINFORED ON DE VOLTAGE AT SOME TERMINALS REN THERMODYNY UNCOURANTO. 2 SOULES AS FOLLOWS: 0-3M, 3 VOLT SCALE 3 - 30M, 30 WELT SCALE

						ON FOUNDED	
CO						YICE -	
6							
2.5						7.5	
100		100				400	
70		100	180		220	299	
4.0						-60	
70						400	
		7.0					

Fig. 59. Radio Transmitter BC-684-A: Voltage Diagram

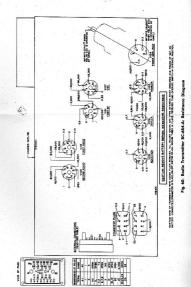


Table VI. Meter Switch Readings*

Switch position	1	2	3	4		. 6
Circuit	Doubler Grid	First R-† Grid	Rectrier Grid	Tripler Grid	Power Amplifer Grid	Total Plate and Streen
Meter reading (27.0 mc)	30	30	20	20	. 30	30
Meter reading (38.9 mc)	20	25	25	25	. 30	30

TYPINGENING RECEIVER TUNE OPERATE switch at RECEIVER TUNE.

and determine where the short circuit is and check the dynamotor.

e. Check of R-f Stapes. Assuming that the dynamotor starts satisfactorily and that no other trouble is noticed upon operating the microphone push button, proceed to a rough check of the operation of the radio-frequency stages.

Check that all crystals are in place.

Caution: High voltage is present on the crystal pin-iacks when the transmitter is operating. Don't take chances.

Operate the push button for the highest frequency channel. Place the RECEIVER TUNE-OPER-ATR switch on RECEIVER TUNE and the TUNE-ANY CUR switch on TUNE. Turn the METER SWITCH on the right end of the transmitter to position 2 and observe the oscillator output to the first radio-frequency stage. This current will be considerably different for crystals of different activity. Any reading is probably satisfactory. (Note: This current may be high for sets with a 1000-ohm resistor R106: see Paragraph 44.) Onerate the METER SWITCH successively to positions 3, 4, 1, and 5, observing the grid current to the rectifier, tripler, doubler, and power amplifier. The current readings given in Table VI may be used as a guide, but it is recommended (on account of possible wide tube and circuit variations) that the normal current readings for each transmitter be recorded for use in locating trouble. (Also see Paragraph 31e.) If you obtain a considerably different reading from that shown in Table VI at one point, your trouble may be near the point of such reading. Voltage and resistance readings in accordance with Figs. 59 and 60 should be made at the stage in which trouble is suspected to be present; if necessary, replace the tube in that stage. Low-voltage readings

indicate short circuits or high series resistance; high-voltage readings in general indicate defective tubes or open circuits or shorted series resistors.

Start the transmitter and check the selector adjustment by depressing the no. 1 push button and observing the maximum meter deflections with the METER SWITCH in positions 3, 4, 1, and 5, as the gang capacitor is varied slightly against the restoring force of the selector springs. Do not attempt to rotate the capacitor control more than a few degrees. The meter should indicate a maximum deflection at the capacitor setting determined by the selector. If the selector does not properly position the gang capacitor, it should be reset in accordance with Paragraph 21a. If the transmitter has been incorrectly tuned to the crystal frequency, incorrect peaking with METER SWITCH positions 1 and 3 will probably result. Improper alignment (assuming that the tuning was done properly) will probably result in low meter readings in positions 1 and 5

Do not operate with the switch on RECEIVER TUNE for more than a few minutes at a time. If no trouble is indicated by the meter readings with the push button for the highest-numbered channel operated, take similar readings on the other channels in sequence.

f. Tuning Check. If your meter readings indicate need for tuning the channels, perform the tuning adjustments in accordance with Paragraph 21s and check as discussed in Paragraph 40s preceding.

g. Power Amplifier Check. To check the operation of the power amplifier, throw the RE-CEIVER TUNE-OPERATE switch to OPERATE. Throw the TUNE-ANT CUR switch to ANT CUR and see if the power output can be varied by

variation of the antenna trimmer capacitor. An antenna (see Paragraph 38b) must be connected for this test. Also read the plate current (METER switch in position 6 and TUNE-ANT CUR switch on TUNE) with the RECEIVER TUNE-OPERATE switch first at RECEIVER TUNE and then at OPER-ATE (microphone button pressed). The difference in readings should give the normal power amplifier plate current. Watch for sparking and overheating in the power amplifier tube itself. If there is output from the preceding stage and none from the power amplifier, check the voltage and resistance readings for the stage and the tube itself. Also check alignment of the power amplifier stage.

b. Check of Audio Stages. Replace the bottom cover plate and place the transmitter on the mounting for check with the associated receiver. Turn the SIDETONE control to maximum. Speak into a microphone. Sidetone should be heard in the associated receiver. As an over-all check of the audio stages and the transmitter itself, operare the transmitter and listen on the receiver of another set. This should give a satisfactory check for both operation and noise in the transmitter. If there is trouble in the audio stages, make a voltage and resistance check of both stages. Operating the transmitter with its own receiver will also give you a satisfactory check of the operation of the control circuits

i. Intermittent Trouble. Whenever a complete inspection of a transmitter is made, every effort should be made to locate and clear intermittent trouble. Do this by complete inspection of parts and wiring and by gently shaking or jarring the transmitter.

41. Maintenance of Dynamotors.

a. Service Tools. No special tools are required for the ordinary care of Dynamotors DM-34-(*), DM-35-(*), DM-36-(*), and DM-37-(*). The following tools and material are desirable:

1-31/5-inch cabinet screwdriver. 1-Small pair of pliers.

1-Toothbrush

1-Clean cloth

1—Can of light machine oil.

1-Can or tube of Type S-58 lubricant, or its equivalent.

1-Light hammer.

1-Center punch.

A few sheets of grade 0000 (4/0) sandpaper.

b. Troubles and their Remedy.

(1) Pailure to Start, or Dynamotor Stops: Passible Cause Correction Check d-c supply and

No d-c supply: open or loose connection. Brushes not seating

properly; dirty, sticking, or worn brushes. Poor commutation; dirty or rough commutator.

tighten connections Remove brushes, Clean thoroughly and reseat or replace as required. Clean commutator and brushes; if rough, sand with 4/0 sandpaper; turn commutator.

Worn bearings; arma-

Replace bearings. ture strikes pole faces or

connections. Defective armature: short-circuited or opencitcuited.

Replace dynamotor

(2) Excessive Arcing at Brushes: Possible Cease Poor commutation; dirty or rough commutator.

Correction Clean commutator and brushes; if rough, sand with 4/0 sandpaper; turn commutator.

Brushes not seating properly; dirty, sticking, or worn brushes. Defective brush spring. Short circuit between bars: dirty commutator.

Remove brushes, Clean thoroughly and reseat or replace as required. Replace brush assembly. Clean commutator, or replace dynamotor.

Open-circuited armature Replace dynamotor. (3) Rapid Brush Wear:

Possible Cense Excessive ascing.

High mics. Replace dynamotor. Dirty-commutator.

Correction Clean commutator and brushes; smooth with 4/0 sandpaper.

Sec (2).

arcuited.

(4) Excessive Noise Picked Up in Radio

Possible Gente Correction

Sparking at communator. See (2).

Lose connections. Tighten connections.

Capacitor open- or short- Replace capacitor.

(5) Excessive Noise and Vibration:

Possible Cance Correction
Amature striking in- Restrange wiring.

amature striking astend wiring.

Amature striking pole Replace dynamotos.

Armsture striking pole Replace dynamotos.

Worn bearings. Repface dynamotos.

c. Routine Maintenance. If the radio equipment is operating normally, the dynamotors should need servicing (including lubrication) only about every 300 hours of use. The life of the dynamotor will be extended substantially if the end bells are removed and the dust wiped from the conversaces and the hours have been described to the conversaces.

the end bells are removed and the dust wiped from the commutators and the brush holders very 100 hours or oftener. Unnecessary dressing of commutators, manipulating of brushes, or tressive greasing is likely to be harmful. Note: In the following paragraphs, numbers in

Note: In the following paragraphs, numbers in prentheses correspond to numbers in Figs. 41 and 42, exploded views of the two dynamotors, which are found on pages 67-68.

(1) Lubrication. Remove the end covers (13) by cutting the safety wires on the ends of the dynamotor and removing screws (14), washers (16), and lock washers (15). Wipe our loose dast and dirt. Take out the screws (28) holding the bearing bracket end plate (27) and remove the end plate, being careful not to lose any shims from the end of the shaft. With the toothbrush and cloth remove all old and hardened grease. Apply two or three drops of light machine oil to the ball bearings, and repack the outer side of the bearing with a small amount of Type S-58 lubricant as made by the New York and New Jersey Lubricant Company, or the equivalent. Do not get oil or grease on the commutator or hnishes

If there is gift in the bearings, you can clean them emporarily by removing the atmatuse and swelling the bearing back and both the clean swelling the bearing back and both the clean line, or carbon eteratholoide. Be careful not no insert the ammater face cough into the fluid to permit the windings to become wer. After cleaning, whate of its most cheaning fluid as possible, then insert the bearings into a both of light mathies of, remove, and allow to dain before repudding with grease as outlined in Paragraph 444(2).

(2) Commutatori. A highly polished commutator surface is very desirable. Don't mistake a dark color for a burned condition. If the sutface is smooth and is polished and the commuration satisfactory. Jeave it alone. Slight sparking does not necessarily mean poor commutation. If the surface of a commutator becomes dirty, wipe with a clean cloth. If necessary, wipe with a cloth moistened with cleaning fluid such as perroleum spirits, kerosene, or gasoline, followed by a dry cloth. Keep bearings and housing clean. Remove the covers and clean out the dust and dirt frequently. This cleaning should include removing the brushes and wiping the inside of the brush holders and the external surfaces of the broshes

(3) Brushes, Each brush has a flexible pigtail and spring designed to limit the rotation of the spring and pigtail to a minimum when replacing a brush cap. Replace brushes when they are less than 1/4-inch long as measured from the bearing surface to the spring. Brush pressure is satisfactory if 1/4 inch or more of the spring extends out of the brush holder when the holder cap is removed and the end of the brush is bearing on the commutator. Run in new or re-dressed brushes for several hours at no load when possible, to obtain proper fit before the dynamotor carries full load. It is desirable that the brushes be so seated that they bear over 100 per cent of their arc and have at least 75 per cent of their area in contact with the commutator. When brushes are replaced after removal, be sure you return them to the same holders from which they were removed. Insert the brushes in their respective holders with the polarity mark facing upwards. When checking or replacing brushes make sure they slide easily in the brush holder; if they do not, the spring cannot force the brush against the commutator.

It is very important to keep brush resistance

as low as possible, so make sure the brush pigtail is in good condition. If a brush pigtal is broken or loose in the brush or end cap, the current has a tendency to go through the brush spring. This causes the spring to overheat, losits temper, and give low brush pressure.

SECTION V. SUPPLEMENTARY DATA

4. Replacement of Parts.

4. Mounting FT-237-(*).


(1) Method of Removing Coaxial Cables

inn L and T Connectors. (a) Remove the covers from the rear and

ed channels of the mounting. (b) Unsolder at the ground clips the ground wires running from the ferrule of the mail cable to the ground clips in the channel; remove the varnished sleeving and bend the wires back from the channel.

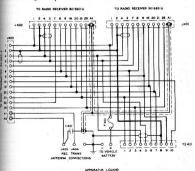(c) Remove the cover clips from the connectors and unsolder the connections inside the connectors. (d) Loosen the Bristo set screw on the

under side of the connectors, cut the tie strings which hold the coaxial cable in position, and pull out the coaxial cable and connectors from the rear channel.



0,0001 UF 500V J403 TRANSMITTER CONNECTION TRANSMITTER ANT CONNECTION AMPERE FUSE (W.E. 668) 1404 1405 RECEIVER ANT CONNECTION JACKS RECEIVER A CONNECTION TS 40 TERMINAL STRIP 1401

1407

RECEIVER & CONNECTION

Fig. 61. Mounting FT-237-(*): Schematic Diagram

(e) Cut the tie strings holding the coaxial cable in position in the end channel, unsolder the connection between the coaxial cable and the capacitor, remove the screw and nut from the coaxial cable ground clamp, and pull

our the coastal cable from the end frament.

(1) With the connector held as pair of gas pliers in the left hand, place the connector plant are proposed to the connector held as the connector plant the right of 2000-aut coldening time. (In the stationary), and remove the cable from the connector has been based out from the connector has been based out friendly to become fluid. Hemore the excess solder in the conpercor has been based out from the connector hy spraping it while hot against a solid object. (This permits ready reuse of the connector). The ground clips at the end of the constall cable may be removed and presented for reuse in the same nament as for connectors.

 Method of Soldering Coaxial Cables to L and T Connectors.

(a) Assemble the ground wire to the retrule by wraping bars, named 22-gauge wire approximately three quarters of a turn around the called close to the ferralle and approximately three turns around the ferral as close to the end of the ferral as a paracitable. (The wire should not of the ferral as a paracitable to the standard of the ferral as paracitable.) Spec solder to this bead end of the called 5 per solder to of the wire of the wire come speci and cut off the wire close special and cut off the wire distributed to the called the ferral programmarely is include long. Do not hear the coxisal any more than is absolutely receivant you solder it, otherwise the beads in the

(b) Insert the cable into the connector (L or T) far enough so that the bead is a ppecuimately 4-inch inside of the milled-out portion of the connector. Hold the connector and the cable in a vertical position; solder the ferrule of the cable and the ground wire to the connector, using a 200-wart soldering iron. Avoid unnecessary heating of the cable.

(c) With the cable in a horizontal position, solder the ground clamp to the ferrule at the end of the cable. To avoid twisting the cable, solder the ground clamp at approximately 90 degrees to the long axis of the portion of the connector having the Bristo set screw.

(d) Place the cable in a position adjacent to and approximately parallel with the rear channel. Assemble the varnished tubing on the ferrule ground wires and connect and solder the ground wires to the ground clip at the J401 and J402 recepcacles.

(e) Place the coaxial cable in the chanel, pash the connectors into position on the radio-frequency terminals of the J401 and J402 receptacles, and righten the Bristo set screws with a ½-inch Bristo hexagonal wrench. Assemble the ground clamp in the end channel with the screw and nut.

(f) Inside the connectors, twist together, solder, and clip the coaxial cable wires and the wires from the radio-frequency terminal on the J401 and J402 receptacles.

Note: Be sure the beads are in position on the wire from the radio-frequency terminals on the receptacles before twisting the wires together. If necessary, replace the beads.

Twist together, solder, and clip the coaxial wire and the capacitor terminal in the end channel.

(g) Tie the coaxial cable to the hexagonal nut of the plunger pin assembly and to the local cable (approximately seven ties).
(h) Replace the channel covers.

b. Radio Receiver BC-683-A.

(1) Replacement of a Channel Selector Unit. To replace a channel selector (tuner) unit in a receiver, perform the following operations.

(a) Connections to be Unsoldered.—Unsolder seven (sometimes eight) electrical connections at the tuner unit (channel selector) to release it from other receiver apparatus.

(b) Screws to be Removed.


(1) Remove the four screws releasing


the front guard of the receiver.

(2) Remove the eight screws releasing

the front panel.

(3) Loosen the five screws in the rear

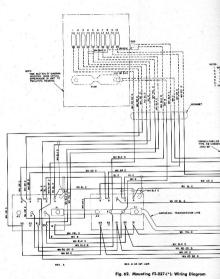

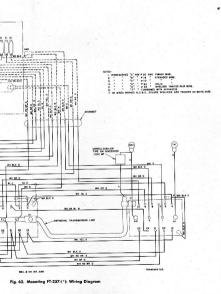

of the tuner, releasing the tuner unit from the mover chassis.

- (c) Method of Replacing Channel Se-
- With the front panel guard and the more panel removed from the receiver, insert the more unit through the front panel opening to the classis.
- (2) Loosely fasten the unit to the musis by five screws. Do not tighten these must. See operation (5) for tightening.
- must. See operation (5) for tightening.

 (3) With the runer loosely in place add the front panel with its apparatus, and fustern securely to the chassis (six screws) and the
- (4) Add the front panel guard to the activer, secure it firmly with four screws.
- (1) Supplement operation (2) by some distinct of the many fining the thouse fixing the thouse fixing the three fixing the three fixeness in the rear of the toure. Be ware to the toure of fastening the fixeness as it avoids sterting up a strain while more in position. (The six other serves which hold the nor in position. (The six other serves which did the from panel do not affect the toure.) Such possible strain might permanently impair the securacy of the tuner. Once to use that all pash buttons operates smoothly and do not bind once receiver panel.
- (6) Resolder the seven (sometimes eight) electrical connections at the tuner unit. (2) Replacement of a Push-button (Plun-
- (a) Assembly in a Channel Selector.
 (a) Release the push button setting as described in Paragraph 21b. Release all push

homons

- (b) Screw Removal Operation.

 (1) Remove four screws to release the
- front panel guard.

 (2) Remove eight screws to release the
- front panel.

 (3) Remove four flathead screws to release the runer front plate and the latch-plate
- assembly.

 (c) Removal of Latch-plate and Pushbutton Assembly.—Pull the lower end of the lath-plate assembly outward slightly. Grasp the

- edges of the latch plate just behind the face plate and pull the latch plate downward. Pull the entire assembly outward gently to prevent jamming, and muse the top end of the latch plate past the edge of the mounting bracket. Pull the assembly further until it separates from the connecting rods.
- (d) Substitution of Push Button.—With the push buttons hanging downward, pull the latch plate back against its spring. Remove the faulty button and replace it with a new button making sure that the north is in line with north on other buttons. Allow the latch plate to return to normal.
- to Neumon Ommun.

 The Mich (2) Applications of Latch-plate and Policy (2) and Pol

c. Radio Transmitter BC-684-A.

- Replacement of a Channel Selector Unit. To replace a channel selector (tuner) unit in a transmitter, perform the following operations.
 - (a) Connections to be Unsoldered.

 (1) Unsolder the short and long co-
- axial cables at antenna post A on the rear of the front panel. Also unsolder R155 from this post.

 (2) Unsolder the short coaxial cable at
- (2) Onsolder at the relay (S101) the capacitor (C161) which connects a long coaxial
 - cable to this relay.

 (4) Unsolder, at the relay, the bare wire which connects the top of the L111 coil to the antenna relay.

- (5) Unsolder, at the bottom of the L110 output coil, the bare wire (covered with varnished tubing) which leads to the power amplifier screen resistor (R114) located in the bottom compartment of the chassis. Also unsolder the black red wire leading from the coil to the
- local cable of the transmitter.

 (6) Unsolder, at the insulated stud r, the bare wire leading to the bottom of the left-hand tuner contact spring assembly.
- (7) Unsolder, at the crystal oven, the ten electrical connections to the runer spring contact assembly.
 - (b) Screws to be Removed.
- (1) Remove the screw on top of the selector to release the ground rerminal lug and wire leading to ground post 6 on the rear of the front panel.
- (2) Remove six screws from the thermocouple, releasing it from its electrical connections and mounting.
- (3) Remove the screw which secures the ground lug to the top of the tuner,—the lug to which the ground wires leading to the short and long coaxial cables ferrules are connected.
- (4) Remove the screw from the top of the tuner, releasing the clamp that holds the long coaxial cable in place across the top of the unit. Carefully bend this cable to the left so that it will not interfere with vertical movement of the tuner.
- (5) Remove four screws, releasing the antenna relay (\$101) from its location. Rotate the relay upward and to the right.
- the relay upward and to the right.

 (6) Remove the gear from the bottom end of the tuner shaft by loosening the set screws with the Righty weech, and remove the rack
- connecting the tuner to the six-gang capacitor.

 (7) Remove the three screws at the base of the tuner, releasing it from the chassis.
- (8) Remove the four screws in the panel guard and remove the guard; unscrew the seven front panel screws and rotate the panel about its right-hand edge (where cables are locuted) to remove the panel apparatus from the panel opening. Lift the channel selector unit out through the top opening of the transmitter.

- (c) Method of Replacing Channel Selector.

 (1) With the front panel guard re-
- moved and the front panel swung out of the way, insert the selector unit into the chassis through the top opening of the transmitter.

 (2) Lossely fasten the unit to the
- chassis by the three screws applied into the base of the selector through the bottom opening of the transmitter.
- (3) Repeat, in reverse order, the remaining steps of (a) and (b) preceding with the exception of (b) (6).
- Castion: When fastening the tuner firmly in position (affect the from panel and its apparasis have been secured to the transmitter), observe that the couner shaft coracts freely if it does not, loosen the three mounting screws and shift the tuner until the tuner shaft is free to rotate with our binding action. When locating the from panel and the tuner in position, he sure the push buttons do not rub in the panel openings.
- (4) With the six gang capacitor fully engaged and the pin (on the disk by which the capacitor is manually roated) retring against the front use in the semicircular opening in the right end of the chassis, and with the single section tuning capacitor at the top of the tunera also fully dotted (maximum capacitance), insert the geat on the unter that, assemble the rack in place, and securely tighten the set serve on the gar. Note that the rack is centrally located and that it moves freely back and forth over its total reavel.
- (2) Replacement of Capacitor Assembly (Including Six-gang Capacitor and Trimmer Capacitors). To replace a capacitor assembly in a transmitter, perform the following operations.
- (a) Connections to be Unsoldered.—Unsolder, through the bottom opening of the transmitter, all wires connecting to the six-gang capacitors.
 - pacitors.

 (b) Screws to be Removed.

 (1) Remove, at the left-hand end of the gang capacitor, the screw which holds a bracket and insulated terminal in place.

(2) Through the bottom of the transmitter remove four screws from the trimmer capacitor assembly bracket, releasing the entire capacitor assembly from the chassis.

capacitor assembly from the chassis.

(c) Replacement of Capacitor Assembly.

—Remove the capacitor assembly, replace with a new unit, and reassemble in reverse order from

(a) and (b).

(3) Replacement of Gang Capacitor in the Gan-capacitor Assembly.

(a) Repeat operations of (2) (a) and
 (b) preceding to release the entire capacitor
 assembly from the transmitter chassis.

(b) Unsolder all electrical connections between the six-gang capacitor assembly and the

timmer capacitors.

(c) Remove four elastic stop nuts on the six gang capacitor assembly to release the brack-

six-gang capacitor assembly to release the bracket on which the associated trimmer capacitors are mounted.

(d) Separate the six-gang capacitor from

the trimmer capacitor assembly bracket released by the stop nuts.

(c) Replace the six-gang capacitor with a new unit and reassemble, with the trimmer

a new time and reassemble, with the triminer capacitor assembly, into the transmitter chassis.

(4) Replacement of Trimmer Capacitor Assembly.

(a) Repeat the operations of (3)(a) and (3)(d) preceding.

(b) Replace the trimmer capacitor section with a new unit and reassemble, with the six-gang capacitor assembly, into the transmitter chassis.

(5) Replacement of a Push-button (Plunger) Assembly in a Transmitter Channel Selector. To replace a channel selector push button in a transmitter, perform the following operations.

(a) Unsolder the long and short coaxial cables ar antenna post A on the rear of the front panel.

(b) Remove the screw from the frame at the top of the selector unit to release the ground terminal wire leading to ground post G on the rear of the front panel.

(c) Remove the tie-string which supports the short coaxial cable in the position near the left-hand post of the panel meter.

(d) Remove the four screws holding the front panel guard.

(e) Remove the seven screws holding the front panel and rotate the panel outward about its right-hand edge.

its right-hand edge.

(f) Remove the four screws on the tuner front plate and latch-plate assembly in order

to release the push buttons.

(g) Pull the defective plunger (push button) forward to separate it from its associated

tod.

(h) Replace plunger and reassemble.

(6) Removal of Tuning Coils in Low Power Stages.

(a) Unsolder the leads to the upper and lower terminals of the defective coil winding

(L106, L107, L108, L118, or L119).

(b) Break the Glypral seal at the bottom of the cylindrical metal tube in the top compart-

ment.
(c) Unscrew the metal tube from the

coil form.

(d) Remove the coil winding assembly from the chassis by withdrawing it from its location hole into the bottom compattment of the

transmitter.

(7) Removal of Coaxial Cable Terminals from Plug PG101.

 (a) Unsolder the ground straps between the coaxial cable ferrules and the chassis.

(b) Remove two screws and hexagonal nuss from each end of the plug to release the two metal plates (clamps) that hold the cable terminals in place.

(c) Remove the metal clamps and pull the cables and terminals from their locations in the plug.

43. Modifications during Manufacture.

a. General. The radio equipment described in this manual has been produced in large quantities over a relatively long period of time. During this period the equipments have been under continual study in the manufacturing plants and in the field. Some changes in the equipment have resulted from these studies. By far the greatest number of changes has been due to the necessity of using a different material, or a part from a different manufacturer. In general, you will find that the units which comprise your radio see will differ in some slight respect from other similar units bearing the same order number.

This apparatus has not only been made in large quantities but also has been constructed by a number of different subcontractors, which means that there may be minor differences in construction or parts. Watch for these variations although in most cases they will not affect serv-

icing procedure

Changes in materials or in the source from which similar parts are obtained do not in general affect the servicing procedure, so this type of change is not described in this manual. Circuit and apparatus changes which should be known to aid the proper servicing of the unit are described in some detail in Paragraph 436 for the receiver and Paragraph 43c for the transmitter.

Figure 70 is a schematic diagram of the receiver showing how it was before these changes were made. The parts that have been changed are crossed out and the new arrangements shown. Figure 73 gives corresponding information for the transmitter.

If you wish to make any of these changes in an earlier equipment and if the change has been authorized, all the items listed under a particular minor heading in the change must be made as a group in order to obtain the desired improvement.

(1) Changes Affecting R17 and R19, R17

h Radio Receiver BC-683-A.

has been changed from 1 megohin to 0.25 megohm. R19 has been changed from 1 megohm to 2 megohms. The purpose of this change was to increase the voltage on the CALL SIGNAL lamp.

(2) Changes Affecting L72 and L71. In earlier drawings these two inductors were shown interchanged. L72 should be the primary winding in the plate circuit of V5. L71 should be the secondary winding in the grid circuit of V6.

(3) Changes Affecting C11. C11 has been reduced from 0.01 to 0.006 microfarad. The purpose of this change was to reduce the number of 0.01-microfarad capacitors.

(4) Changes Affecting C82 and C20.3. C82 has been reduced from 0.01 to 0.006 microfarad. C20.3 has been connected in parallel with C82. (It was previously in parallel with C20.2.) The purpose of this change was to reduce the number of 0.01-microfarad capacitors. It was found that the audio-frequency impedance of the circuit at the points across which C82 is connected should be reduced to improve circuit operation. This was accomplished by connecting C20.3 across C82 after which C82 could be reduced. It was found, also, that when C20.3 was so connected, the stability of the circuit was better than it had been with C20.3 connected across C20.2.

(5) Changes Involving R8, R21, R71, R72, R74, and C71 (Limiter Characteristics of V5). R8 has been increased from 20,000 to 70,000 ohms (V2-watt type).

R21, which is a 30,000-ohm (2-watt) type, has been added.

R71 has been increased from 100,000 ohms to 250,000 ohms

R72 has been decreased from 43,000 ohms to 30,000 ohm. R74 has been decreased from 10,000 to 1,000 ohms (1/2-watt type)

C71 has been docreased from 100 to 50 micromicro-

These wiring changes were desirable because. on very strong signals, the output of the limiter previously fell off so much as to interfere with the operation of the squelch circuit under some conditions. In addition, the changes improved the reception of weak signals through high noise levels. In general, the changes were:

To make the second intermediate-frequency amplifier, V5, a more effective limiter by lowering screen and plate voltages. This involves R8 and R21 and a change in the plate return of V5. R74, formerly 10,000 ohms, could be reduced to 1000 ohms as drop in this resistor was no longer required. R71 was increased to improve the limiting action. This necessitated reducing C71 to mirrain the proper time constant. R72 was decreased to obtain optimum load cross L71.

Is remore the second intermediate-frequency uplifier from the influence of the delayed autouniv-volunce-control circuit. This improved remonan through strong noise. It involved moving the gid return of V5 from the automatic-voluncoatrol circuit to the negative end of the immotor.

These changes are indicated graphically in Bg. 70 which shows the old arrangement crossed so and the new arrangement added.

the actual changes in wiring are as follows

(a) Move one pigtail of R8 from ter ninal 5 of FL2A to terminal 2 of FL2A.

(b) Remove a wire (covered with a black

steeve) from terminal 6 of VS5 and terminal of FL3A.

- (c) Connect one pigtail of R21 to ter minal 5 of FL2A and the other pigtail to terminal 5 of FL3A.
- (d) Remove the green (tracer) wire from terminal 4 of VS9 and connect it to that terminal of C25 to which the blue (tracer) leads are connected.
- (e) Add a blue-brown (tracer) wire from terminal 5 of FL3A to terminal 5 of FL4.
- (6) Change Involving C44. This 30-micromicrofinand capacitor in the radio-frequency osillator circuit was changed from silver mica to in N-080 Ceramicon. The change was made to improve temperature stability.
- (7) Change Involving C26, C26 has been reduced from 0.001 to 0.0005 microfarad. This was done to permit the use of a ceramic capacitor as an alternate. This change also improved the operation of the bear oscillator by reducing the pull-in at low frequencies.
 (8) Changes in Capacitors of Dynamotors.
- in Dynamotors DM-34-(*) and DM-36-(*), all the filter capacitors in some units have been reduced from 0.005 to 0.003 microfarad. No reduction in circuit performance results from this

change. Where a replacement problem involves a substitution of a filter capacitor, either a 0.003 or a 0.005-microfactad unit may be used in any position in the dynamotor without regard to the capacitance of the remaining units, but the replacements must meet the voltage rating perscribed in Paragraph 45, Table of Replaceable Paris.

 (9) Change in C35. This unit was reduced e from 0.01 to 0.006 microfarad.

(10) Changes Affecting C53, C54, C55, C56, C63, C64, C65, C66, C73, C74, C75, C76, C84, C85, C86, C87, C88. These changes are tabulated as follows:

		Capacitance Value			
Filter	Original Unit	Oviginal	Replacio		
FLIA	C53 and C54	*50 + †10	160		
FL1A	C55 and C56	†10 + *50	160		
FL2A	C63 and C64	*50 + †10	160		
FL2A	C65 and C66	†10 + *50	160		
FL3A	C73 and C74	*50 + 110	160		
FL3A	C75 and C76	†10 + *50	160		
FL4	C84, C85, and C86	†5, *50, and	\$60 and		
FL4	C87 and C88	*25 + †10	135		

*Silver-mica. †Ceramic N-6 ‡Ceramic N-0

Ceramic N 080. In filter units FL1A, FL2A, FL3A, and FL4 of the receiver, small ceramic capacitors were used originally in combination with silver-mica capacitors to provide temperature-compensated tuning capacitances. In later equipments these combinations of two capacitors have been replaced by single ceramic units each having capacitance and temperature compensation equal to those of the combination which it replaced. This is possible because a ceramic capacitor can be provided with any desired temperature coefficient (over a substantial range of positive and negative values). The single ceramic capacitor may be used as a direct replacement for the combination or vice versa. All the changes listed here fall in this class. Most of them are combinations where two units were in parallel and the changes involved a single ceramic with capacitance equal to the sum of the two and a temperature coefficient equivalent to their combination. In FL4, however, C85 and C86 (each a 50-micromicrofazad silver-mica capacitor) were in series and C84 (a 5-micromicrofarad Ceramicon) was in parallel with the combination, making a total of 30 micromicrofarads. C85 and C86 have been changed to 60-micromicrofarad Ceramicons with the desired remperature coefficient which makes C84 unnecessary.

(11) Change in Designation of Switch D2.
Switch D2 on the receiver was originally designated anno AEXT-EXT ONLY. This designation was changed to OUTPUT TO PHONES ON-OFF to provide a better conception of the function of this switch.

(12) Change to Seeled Unit LCU-Sc. (LUS)-Curius are sometimes applied as spore parts in place of LCU-Sc units to replace the LCU-Sc units are unit. The LCU-SC unit is essentially the same as the LCU-Sc unit, exceptant it has been sealed to exclude moisture, there, by improving frequency schelling of the receiver under high hamfully conditions. The terminal under high hamfully conditions. The terminal that the condition of the condition of the LCU-Sc unit call in the backetin such of the LCU-Sc unit call in the place of the condition of the best of the unstacled LCU-Sc unit.

If difficulty is encountered with frequency stability of a receiver under high humidity conditions, replace the LCU3-A unit with an LCU3-C sealed unit as follows:

Wire the LCU3-C unit in place without disturbing the cap. The adjustable slag of the LCU3-C unit has been preset as the facrory and should seldom require adjustment during the alignment procedure. The capacity frimmer CL7, should be adjusted for that tracking at 38 megacycles and the fall tracking theseled at 28, 32, and 35 megacycles. In many instances a slight readjustment of CL7 will improve alignment.

readjustment of C.1.7 will improve alignment. A maximum dial tracking error at any frequency of three-fourths channel division is considered quite sainfactory providing the maximum error at the other two check frequencies is the contract of the contract of the consomewhat in excess of these values are found, the contract of the con Caution: This unit is sealed against moisture. Do not remove the cap unless absolutely necessary.

Should a slug adjustment at 28 megacycles be found necessary, use the following procedure:

(a) Find as dry a place as possible.(b) Run the receiver about an hour with

the dust cover in place to warm the unit.

(c) To remove the cap, heat the single

point solder seal of the cap with a soldering from while exerting a turning motion on the cap. (d) Complete the alignment as quickly

as possible.

(e) Replace the cap and re-solder in

place.

(f) If the cap was off for more than five

minutes, run the receiver at least an hour with the dust cover in place and the cap off the unit. (g) Remove dust cover, replace cap, and re-solder.

c. Radio Transmitter BC-684-A.

(1) A Change thin Should be Made in Existing Equipment: Fase F101. Fuse F101 should be of V₂-ampere rating. Some of the early equipment had 1-ampere fuses which do not always give adequare protection. One-half ampere fuses (as supplied in the spare parts groups) should be substructed for any 1-ampere fuses in this position.

(2) Changes in Parts

(a) Change in Cl47—The unit used in later production is a ceranic-type capacitor of cylindrical form covered with a black blacking finish. This is the preferred replacement part. It is specified with plus or misus 2 per cent tolerance and zared a 850 volte, working. If it cannot be obtained it is satisfactory to use the single 173micromicordand onti of the CD Type 1R capacitor or four 173-micromicrofarad units of the CD Type 5R capacitor in series-parallel, It is not satisfactory to use a single CD Type 5R unit.

(b) Changes in Dynamotor Relay S102.

—This relay has been changed from a Type AO to a Type BO relay with increased contact pres-

are in the operated position. The latter unit is referable but either can be used as available.

(c) Change in R107.-R107 was changed from 1/4-watt to 1-watt rating at 30,000 ohms in oler to care for the higher current taken by me vacuum rubes.

(d) Changes in Resistors R119 and RISS.-Two resistors R119 and R155 were nignally specified as IRC Type F resistors. The BC BT or BW types are just as satisfactory at test places and are or may be used interchangeels with Type F. The BT and BW types ste preferred, however, because they mount in de mansmitter more easily and with less chance of short-circuiting to adjacent parts or the chas-

(e) Changes in Capacitors C138 and C42.-Capacitors C138 and C142 have been beined from a number of different manufacmers and therefore it will be found that the "mermon" rerminal (marked c on the capacitor can and in the wiring diagrams) will be located stone end of some capacitors and on the other end of other caracitors. Be careful in replacing acapacitor of this type to see that the c terminal is connected to the proper wires as shown in the wiring diagram of the transmitter.

(f) Changes in Transformers T101 and T102.-Some of these transformers were wound in the reverse direction from the majority. In many instances this will not cause poor operation but in some transmitters a reverse-wound transformer will be indicated by a high poise level on the radio carrier or on the interphone output. This can be cured by reversing (interchanging) the leads (red and blue) to terminals 5 and 6 on transformer T102. Transmitters using rerersed transformers will have the wires interchanged at these terminals. Replacement transfurmers should be checked in this respect.

(3) Changes in Arrangement. (a) Change in Connections of C122 and

C123 and Addition of L123,-C122 was connexted previously from the screen of V104 (power amplifier) to ground. Its ground termigal has been moved to the ungrounded side of the filament of V104. C123 was connected previously

from the ungrounded side of the filament of V104 to ground. It has been changed to connect between ground and the filament of V103. L123 has been added in the filament lead between

V103 and V104. The purpose of these changes was to climinate a tendency to spurious oscillation at very high frequency, which occurred in rube V104 of a few transmitters if a selector

button was not depressed.

(b) Change in R118 and Addition of R162 and R163.-R118 has been changed to decrease the power dissipared in it. It was a 30,000ohm. 2-watt unit, but has been changed to a 100,000-ohm, 2-watt unit, shunted by two other similar units (R162 and R163) mounted in the same resistance group. Thus the total resistance of the combination is not greatly changed but the power capacity is substantially increased. If a field replacement becomes necessary, it is desirable to use three 100,000-ohm, 2-watt units if possible. If they are not available a single 30,000chm. 2-wart unit may be used until the 100,000ohm. 2-watt units can be obtained.

(c) Change in R102 and R107 and Addition of R160.-Some manufacturing variations caused the total current through dropping resistors R102 and R147 to exceed the allowable dissipation in these resistors. The later production units, therefore, were changed to add another resistor, R160, so that the three resistors could reliably dissipate the maximum heat. The total resistance of the three units was kept the same by reducing R102 and R147 from 1000 ohms each to 667 ohms each. R160 is 667 ohms.

(d) Change in R111 and Addition of R161.-R111 was changed from 15,000 ohms to 30,000 ohms, and R161 (30,000 ohms, 1 watt) was added in parallel to care for the increased erid current occurring with some tubes.

(e) Change in L106, L107, C111, C112, and Addition of C164.-During production it was found that some variations in wiring caused the coupling between L106 and L107 to be decreased below a suitable value. This was corsected by interchanging the coils and adding C164. The wiring changes are shown in the wiring diagram, Fig. 75. In the revised circuit some of the coupling is obtained by mental inductions. Determen the see out is an additional coupling is obtained by the capacitor network Clofe, Cltl. is obtained by the capacitor network Clofe, Cltl. and Cltl. It will be noted in the writing diagram that in order to assure satisfactory operation, the table as Cstll. (Cltl.) and Cloff must be held to the length indicated. The tolerances of the expansions must be held to those shown in Paragaph 45, Table of Replacacite Parts. If these expansions are proposed for the companion of the proposed proposed to the companion of the companion and the feed to those shown in Paragaph 45, Table of Replacacite Parts. If these expansions are properly fasted as shown by the writing diagram and the feed on touched in making this change in the field. This change need not be fasted to the change in the field. This change need not be factored.

(f) Change in Wiring of R109.—One end of R109 was formerly connected to the boxtom terminal of L106. This connection was moved in later transmitters to terminal 6 of VS108 in order to reduce the current through resistor R157.

(g) Shortening of Souls E and F and Relocation of L117-R1-0—In the entity production these studs were longer than necessary. This secess length produced coupting which caused poor oscillator operation in a few cases. Along with the shortening of the studs there were some writing changes which are discussed in paragraph (3) following. The arrangements can be visualized by reference to Figs. 50 and 73. If this change I found necessary it will be facilitated design found necessary it will be facilitated output. The set place and the change are as guide. The set place making the change are as follows:

(1) On stud F, interchange the top and bottom halves of the stud insulator and clip off the unnecessary part of the stud at the under side.

(2) On stud E, interchange the top and bottom halves of the stud insulator and clip off the unnecessary part of the stud at the under side.

(3) The coil-resistor combination (L117-R149) was previously connected from the end of stud s to R101 (the end away from the chassis). It crossed L102 on the side away from the chassis. This unit should be reconnected from the shortened stud E to R101-the end nearest to the chassis. The wire previously connected to that end of R101 should be removed and reconnected to R101 at the end away from the chassis. With this rearrangement the coilresistor combination passes between the chassis and coil L102.

(4) The two wires coming to L102 should be interchanged.

(h) Arrangement of Thermocouple Connections.-In order to permit adjusting the antenna current (TUNE-ANT CUR) meter reading over a wider range, the slide-wire adjustment was removed from between the terminals of the thermocouple and placed between the ends of the short coaxial transmission line connecting the antenna relay and the antenna binding post (A) on the front panel of the transmitter. This change cannot be made unless the replacement metering length of coaxial line is available. In installations where the antenna current reading on M101 is too low for convenient use, the reading may be raised by unsoldering the thermocouple slider tap and moving the tap to increase the reading. Take care that the antenna current reading will not go off scale under the highest voltage conditions. If the antenna current reading is too high, the direction of change should be reversed. This adjustment is most effective with the newer type arrangement of the thermocouple circuit.

(i) Meters and Thermocouples.-Meters from three manufacturers and thermocouples from two manufacturers have been used in the transmitters in order to maintain production when the meter or thermocouple from any one manufacturer became temporarily unavailable. Any of the meters and thermocouples will operate satisfactorily in a transmitter although there may be an inconsequential difference in meter readings when different meters are substituted. and the slide-wire tap may need slight adjustment when different thermocouples are substituted. The Weston thermocouples are somewhat faster in operation than the vacuum type marked with a number (ES-680241-7). The Weston meter originally had three connection studs, the two top ones going to the meter movement, the lower one going to the scale plate and magnet.

The lower stud is not and should not be used (see the wiring diagram, Fig. 75). In later meters this third stud has been eliminated. During the change-over from three to two studs, a number of the meters (about 1000) were incorrectly constructed to include a strap connection from the moving coil to the magnet and scale plate. This does not affect its operation at the TUNE position of D121 nor its operation with vacuum thermocouples for ANT CUR position of D121. Howerer, in some transmitters a Weston meter having the incorrect connection may not operate properly with a Weston thermocouple. This will be indicated by very sluggish action of the meter when the antenna trimmer (usually at the highest frequency) is tuned. The meter reading will not drop to low values as it should when the antenna circuit is detuned by the trimmer. The approximately 1000 transmitters which have the incorrectly wired meter are satisfactory because they are equipped with vacuum thermomuples. When a Weston thermocouple is to be substituted for a vacuum thermocouple, tests as mentioned should be made to check the operation of the thermocouple-meter combination. If the trouble appears to be present, three methods

(1) Use a vacuum thermocouple if available; or

of correction are available

(2) Use a Hickok or Triplett meter if

(3) Remove the Weston meter and suscret and lift of the front portion of the case; open-dictuit the connection between the scale plate and moving out of by clipping the strap which must from the left series and nut on the moving out support and under the scale plate to the scale plate series. Do not remove the nut on the moving out support as that might cause the moving coil to become incorrectly positioned in the beinging and cause unstatificatory operation.

(4) Changes in Values.

 (a) Reduction in the Capacitance of C501, C502, C601, and C602.—C501 and C502 in the 12-volt dynamotor have been reduced from

0.003 to 0.002 microfarad. The same is true for C601 and C602 in the 24-volt dynamotor. Either value (0.002 or 0.003 microfarad) is satisfactory, however.

howevers. Quality and the Voltage Rating of the Postage samp Gynostion—Some off the postage-samp type of mice capacitions were changed to most kaving a higher voltage rating. Capacitors having the voltage rating, Capacitors having the voltage ratings shown in Paragraph 4.7 Table of Replexable Parts, should be used for explacement purposes. Many capacitions of the desired control of the property of the property

(c) Change in Resizor R106.—R106 has been decreased from 1000 ohms to 100 ohms. The purpose was to keep the meter reading from ognoging off scale when the battery voltage is high and switch D125 is in position 2. The resistor furnished in the party parts has a resitance of 100 ohms. Replacement of a good existing 1000-dm unit is not necessary unless the meter reading good off scale when the battery voltage is high. Since this affects the meter reading you should allow for this when checking the operation of different transmitters.

(5) Elimination and Addition of Parts.

(a) Addition of R159.—R159 was added in later transmitters from the screen of the doubler V103 to ground, in order to make this tube operate more uniformly with wide variations of input voltage.

(b) Elimination of Capacitors (102 and C10.—C102, formerly connected to the filament of V101, and C110, formerly connected to the filament of V102, have been eliminated from the later transmiters. The purpose of this change was to reduce the use of mica capacitors. Either or both of these units may be omitted or removed without impairing the operation of the transmitter.

(c) Elimination of C160. — Capacitor
 C160 (across the primary of T102) has been

(d) Elimination of C107.—This capacitor has been found unnecessary because the units with which it was associated can be held to close rolerances during manufacture.

(e) Elimination of C503 and C603.— These capacitors across the low-voltage end of the 12- and 24-volt dynamotors, respectively, can be eliminated without causing trouble. d. Changes Affecting All Units. All units of Racio Sets SCR-608-A and SCR-628-A use fasteners to hold covers in place. Most of the units employ Dzus fasteners but a number employ a Shakeproof fastener. Spare Shakeproof fasteners should not be used as replacements on units that have Dzus fasteners and vice versa.

e. Relative Characteristics of Various Types of Capacitors and Resistors. It has been necessary to substitute other types of capacitors in secte places where mica units were specified. This has been done where such substitutions do not interfere with satisfactory operation of the radio cquipment. In many cases the replacing units differ from the original units in size or

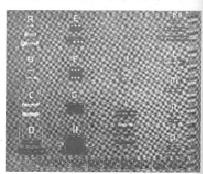


Fig. 63. Types of Capacitors and Resistors

shape or both. The relative appearance of the various capacitors and resistors used in these radio sets is shown in Fig. 63. The first column (A-D) shows ceramic capacitors. The second (E-H) shows mica capacitors and the third (I-1) shows oiled paper capacitors. In the fourth column (K-O) are various kinds of resistors. The general characteristics of such units are given in Table VII and discussed in more detail later. While Fig. 63 covers the range of types, it does not necessarily include all the varitrions produced by different manufacturers.

they are the most suitable for the use for which they are specified. Other units, particularly ceramic capacitors, should not be used indiscrim-

inately as replacements. There are two general types of dielectric (insulation) which are often used in capacitors in place of mica. They are (1) ceramic material and (2) oiled paper. The ceramic capacitor consises of silver fired on ceramic insulation, the composition of the ceramic being varied to obtain different temperature coefficients. These are extremely stable and can be made to cover a wide

		Table VII	Capacite	or Characteristics		
			as Used in sipment			
Group Latter (Fig. 63)	Type	D-C Valti, Working Rating	HAT Coperitorer	Advantages	Disalvanages	Typical Use
First Column	- 77)		
Λ	Insulated Ceramicon (trade name)	800	200	Stability and	Size limitation for large	Temperature compensation
В	Uninsulated ceramic	800	500	temperature	(apacitance; also B, C, and D must	
C	Uninsulated Ceramicon	800	500	Compensation	noe touch metal	mics units
D	Uninsulated ceramic	800	500			
*Second Column						
E (red)	Insulated silver-mica	800	700	Scability		Timed circuits
E (brown)	Insulated mica	800	500	liase of manu- facture		By-pass
F (red)	Insulated silver-mica	1000	1000	Stability		Tuned circuits
F (brown)	Insulated mica	1000	10,000	Ease of manu- facture		By-pass
G (brown)	Insulated mica	1000	10,000	Ease of manu- facture		By-pass
H (brown)	Insulated mica	1200	10,000	Ease of manu- facture		By-pass
*Third Column						
I	Insulated ciled paper	800	10,000	Does not require	Not suitable for tuned circuits or	By-pess, replacing
- I	ciled paper	800	10,000	war marerial	large r-f	F and G

1	Insulated oiled paper	800	10,000	Does not require	Not suitable for tuned circuits or	By-pess,
J	ciled paper	800	10,000	mica, a critical war material	large r-f currents	F and G

closes are not obtainable with controlled or

per degree Centigrade.) For a given size of unit, the capacitance increases as the remperature coefficient becomes more negative. Therefore, no range of capacitance values can be assigned to a particular size without specifying the temperature coefficient. For a given temperature coefficient some coefficient, for apparature coefficient, the capacitance of a ceramic unit can be increased only by increasing the length or diameter of the rube.

The three sizes shown under group A (Fig. 63) cover the range of physical sizes in which these insulated ceramic capacitors are manufactured. These units were supplied originally in small sizes to provide temperature compensation for the combination of coil and mica capacitor in a tuned circuit. More recently, they have been specified in larger sizes in some tuned circuits to eliminate the need for a mica capacitos and provide temperature compensation for the coil. Since ceramic units with equal capacitance may differ greatly in temperature coefficient, it is not safe to use a ceramic unit for a replacement (where stability is needed) unless the temperature coefficient is known to be correct for that use.

Five sizes of ceramic capacitors are shown in Fig. 63. The two smallest are those in B. The next two are those in C, and the largest is the lower unit in D. Except for insulation the largest unit in group A corresponds in characteristics to the small unit in group C.

It will be noticed that with uninsulated ceramic capacitors, the leads are sometimes as unequal distances from the ends of the unit. The lead which is farther from the end is connected to the outer surface of the capacitor. Whenever possible, this lead should be connected to the ground, or low potential, side of the circuit.

In the conventional type of mica capacitor, strips of metal foil are interleaved between sheets of mica deflectric (insulation). Changes in temperature cause an undesirable amount of variation in the capacitance of such units. The salver-mica unit gives a much more stable capacitor or which is suitable for nued circuits. It consists of sheets of mica with electrodes of silver bonded to each surface.

Groups E and F illustrate the two types of color code discussed in Paragraph 44. Groups F, F, and G are made in both foil-mica and allver-mica units. Group H is used in the transmitter. It is a larger capacitor with higher voltage rating and has a more rigid mounting arrangement.

All the mica capacitors shown in the second column of Fig. 63 are insulated by a molded backlife sicket and can be allowed to rest against meral. In general, the foil-mica units have a brown jacket, and the silver-mica units have a red jacket. Capacitors with a straw-colored backlife jacket, as used in this equipment, may be either foil-mica, silver-mica, or paper units.

be either foil-mica, silver-mica, or paper units Ceramic capacitors are used where high stability is necessary and paper capacitors elsewhere whenever possible.

The capacines thown in the third column of Fig. 65 set oil integrated paper for insulation. For stability, they do not compare with altermica types but they can be used as replacements for foil-mica types for screen grid and filament positions of vacuum tubes where they do not need to pass much radio-frequency current. In general, they are good substitutes for mica unity for most by-pass purposes. The voltage rating decreases as the capacitance increases as follows:

Capacitance (microfarads) 0.003 0.006 0.4
Rating (d-c volts, working) 800 600 40

Group I shows a molded bakelite case which is adequate insulation. In general, such units will be black though they may be straw-colored. Group J shows cubular-shaped units. The top unit has a thin bakelite cover and may be allowed to rooth metal. The second unit in this group has a metal case and may have either one or both leads insulated from this case. If one lead is not insulated, it should be connected to ground or lead to the lower voltage connection. The bottom unit in group J is identical with the second except for cover which gives some insulating protection but it not sufficient to permit resting the unit against metal.

In summary, the unit specified in the Table of Replaceable Parts for a particular circuit symbol may be different in appearance from the one which it replaces and may require some inequality in mounting. Groups 1 and J are intereded to six the place of F and G in some application. Groups A, B, C, and D replace silver-nice units of groups E, F, and G where stablely it required but must be used only as specified because of the wide range of management one efficiency and the six of the place of of the p

The fourth column (groups K-O) shows various small resistors. They vary considerably in size and shape for the same warrage ratings due to differences in manufacture. The units shown in group K are 1/2 watt, 1 watt, and 2 watts, respectively. They are bakelite-insulated and may touch metal. The unit shown under L is a 1-watt unit. The unit shown at M with side leads is a high-frequency resistor. This has metal ends and is not insulated. This unit is used only in a few places in the transmitter. It is rated at 1/4 watt. The units shown at group N (brown body) are bakelite-insulated resistors of the 1/4- and 1watt sizes made by another manufacturer. (This manufacturer also makes a similar uninsulated resistor with a black body.) These are directly interchangeable with the upper two units in group K, above. The units shown at O are 1/4- and 1watt sizes from still another manufacturer and are interchangeable with corresponding units already mentioned.

Similar units of other manufacture not shown may be used to replace those illustrated. 44. Color Codes on Components. The various types of capacitors and raintens used in Radio Sen SCR-600-8, and SCR-620-8, are illustrated in Fig. 63 and discussed in Paragraph &c. Some capacitors and resistons have their values sampled on the unit, but in many cases colored does and bands are used instead. The various color rodes used for capacitors and resistons are stown in Figs. 64 to 68 inclusive, and are discussed in the following paragraphs:

a. Molded Mica Dielectric Capacitors. Capacitors of this type are illustrated in groups E, F, G, and H of Fig. 63. Three different color codes are used on these units:

The three-dot code.

The RMA (Radio Manufacturers Association)
six-dot code.

six-dot code. The AWS (American War Standard) six-dot

code.

(1) Three-dot Code for Molded Mica Capacitors. This code, which was widely used for a number of years, is gradually being replaced by the other two codes. However, many components so marked are used in Radio Sers SCR-608-A and SCR-628-A. Also, this code is likely to be encountered in parts stocks. As indicated in Fig. 64, the basis of the code is a series of three colored does which indicate the capacitance, in micromicrofarads, of the unit. Two auxiliary colored dots indicating, respectively, the voltage rating and the capacitance tolerance, are sometimes, but not always, added. There is usually a molded or stamped arrow to show the sequence in which the does are to be read. Dots one and two indicate the first two digits, while dot three tells the decimal multiplier to be used. Take, for example, a 0.006microfarad capacitor. Its capacitance in micromicrofarads is 6000; the three dots, in sequence. are: blue (6), black (0), red (100).

The dot indicating the tolerance, when used, is usually located above or below the third (decinal multiplier) dot. As shown in Fig. 64, the various colors correspond to tolerances between plus or minus 1 per cent and plus or minus 20 per cent.

The voltage dot, when used, is ordinarily locared above or below the first (first digit) dot. The various colors tell, according to the code of Fig. 64, the d-c working voltage.

When either or both of the auxiliary dots are omitted, it indicates that the capacitance tolerance is plus or minus 20 per cent and that the d-c working voltage is the lowest rating for the particular type and size of capacitor.

(2) RMA Code for Molded Mica Capacitors. The RMA (Radio Manufacturers Association) code illustrated in Fig. 65 is used to a limited extent. It uses six colored dots with an arrow to show the sequence. The first three dots give the first three digits of the capacitance in micromicrofarads; the fourth dot (directly below the third) gives the decimal multiplier. The fifth indicates the tolerance in capacitance, and the sixth, the d-c working voltage. For example: a capacitor of 0.006 microfarad (6000 micromicrofarads) plus or minus 10 per cent. 800 volts d-c, working, would be marked with dots in the following order: blue (6); black (0); black (0); brown (multiplier 10); silver (plus or minus 10 per cent); gray (800 volts).

(3) AWS Code for Molded Mica Cabacitors. The AWS (American War Standard) code for molded mica capacitors is shown in Fig. 66a. Like the RMA code, it uses six colored dots, but with somewhat different significance. The first four dots give the capacitance in micromicrofarads, as follows: first significant figure: second significant figure; third significant figure; decimal multiplier. It will be noted that this scheme makes provision for marking units in three significant figures. For example, consider a capaci



		NATING DOLON	1 2 3		
	First Dos	Second Dol	Third Dot		Voltage
Color	Color First Digit Second		Decimal Multiplier	Tolerance	Rating
Black	0	0	1	±20%	
Brown	1	1	10	± 1%	100
Red	2	2	100	± 2%	200
Orange	3	3	1,000	± 3%	300
Yellow	4	4	10,000	± 4%	400
Green	3	5	100,000	± 5%	500
Blue	6	6	1,000,000	± 6%	600
Violet	7	7	10,000,000	± 7%	700
Gray	8	8	100,000,000	± 8%	800
White	9	9	1,000,000,000	± 9%	900
Gold	_	-	0.1	± 5%	1,000
Silver	-	-	0.01	±10%	2,000
Body	_		_	±20%	

[.] When no color is indicated, the voltage rating may be as low as 500 volta.

Fig. 64. Molded Mica Capacitors: Three-dot Color Code

tor of 1,250 micromicrofarads. With the AWS code, the 1,250-micromicrofarad capacitor would be marked: brown (1), red (2), green (5), brown (10); the precise value of 1,250 micromicrofarads would thus be shown by the color

code. In practice, the precision markings just described are seldom necessary. In fact, none of the capacitors standardized under the AWS code requires more than two significant digits to specify its capacitance. For example, molded-micadielectric capacitors of the size known as "CM30" are standard in capacitances of 1000, 1100, 1200, 1300, 1500, 1600, etc., micromicrofarads. Intermediate values, such as 1,250 or 1,530, are not at present incorporated in the code. This is taken advantage of, as follows: The first dot on all capacitors now standard is black (0), and the two necessary significant figures are given by the second and third dots. The black first dot thus becomes a distinguishing feature or identification symbol, as it were, for a capacitor marked according to the AWS code. A couple of examples may serve to make this clear. Take, first, a 120-micromicrofarad capacitor; it is marked: black (0); brown (1); red (2); brown (10)-0120 micromicrofarads.

Or, consider a 9,100-micromicrofarad capacitor: black (0); white (9); brown (1); red (100)— 09100 micromicrofarads. It will be noticed that in both these instances the first dot is black.

The fifth doe in the AWS code indicates the expectance releases in the AWS code indicates the expectance releases in per cent of noneint per potationers. For principal design characteristics, as indicated in Fig. 66a, is the remperature coefficient. For example a 0.000-microfarad (6000 micromicrofarads) plus or minus 10 per cent micro lays acquarior would be marked black (0): blue (6): black (0): red (100): sixter (plus or minus 10 per cent); black (micromicrofarads) bypass, with no temperature coefficient specified.

It will be noted that this color code does not include the voltage rating. This is considered



-	First Dot	Second Dot	Third Dot	Fourth Dat	Fifth Do	Sixth Dat	
Color	First Digit	Second Digit	Third Digit	Decimal Mulsiplier	Tolorance	Voltage	
Black	0	0	0	1	-	-	
Brown	1	1	1	10	196	100	
Red	2	2	2	100	2%	200	
Orange	3	3	3	1,000	3%	300	
Yellow	4	4	4	10,000	4%	400	
Green	5	5	5	100,000	5%	500	
Blue	6	6	6	1,000,000	6%	600	
Violet	7	7	7	10,000,000	7%	700	
Grav	- 8	8	8	100,000,000	8%	800	
White	9	9	9	1,000,000,000	9%	900	
Gold		2 -	-	0.1	5%	1,000	
Silver		-		0.01	10%	2,000	
Body	-		-	-	20%	500	

unnecessary, since with few exceptions, all capacitors marked with this color code are rared at 500 d-c working volts. The exceptions, all of which are rated at 300 volts, are:

Type CM35 capacitors (53/64-inch maximum length) with capacitances of 6,800, 7,500, and 8,200 micromicrofarads.

Type CM40 capacitors (1-1/32 inch maximum length) with capacitances of 9,100 and 10,000 micromicrofarads.

Further details of the American War Standard for fixed-mica-dielectric capacitors will be found in Standard C75.3 of the American Scandards Association.

b. Molded Paper Dielectric Capacitors, A new AWS color code for small molded paper dielectric capacitors is shown in Fig. 66b. Although this code has found little application to date, it is possible that some units so marked may be encountered in future equipment or stocks Like the code for mica capacitors just discussed it employs six colored dots, together with an arrow to indicate the sequence. Units marked ac cording to this system can readily be identified by the fact that both the first and fifth dots are always silver. The other dots are used as follows: the second dot gives the first digit of the capacitance in micromicrofarads; the third dot gives the second significant figure: the fourth dot in dicates the decimal multiplier; the sixth tells whether the unit has a maximum operating temperature of 167 degrees or 185 degrees Fahrenboir

No indication of the working voltage is given by the color code. In general, it can be said that molded paper dielectric capacitors meeting the AWS specification have d-c working voltages be-



	First Dut	Second Dee	Third Det	Fourth Dot	Fifth Dot	*Sinth Det
Color	First Digit	Second Digit	Third Digit	Decimal Mulciplier	Tolerance	Characteristics
Black	. 0	0	0	1	生20%	٨
Brown	1	1	ĭ	10	-	В
Red	2	2	2	100	± 2%	. с
Orange	3	3	3	1,000		D
Yellow	4	4	4	a, "w	-	E
Green	5	5	5		-	F
Blue	. 6	6	6	10 m	-	G
Violet	7	7	7	-	-	-
Gray	8	8	8		-	-
White	9	9	9	-	_	
Gold	-	-	-	0.1	# 5%	-
Silver	_	_	- 7	0.01	±10%	_

^{*}A. Ordinary mica by-pass.

B. Same as A. low-loss case

Fig. 66a. Molded Mica Capacitors: AWS Six-dot Color Code

Same as n, low-loss case.
 By-pass or silver-maca capacitor (semperature coefficient: ± 200 parts/million/C).

D. Silver-mica capacine (temperature coefficient ± 100 persyminon).

K. Silver-mica capacine (temperature coefficient ± 100 persyminon).

K. Silver-mica capacine (temperature coefficient 0 to + 100 persyminon).

G. Silver-mica capacine (temperature coefficient 0 to + 50 persyminon).

G. Silver-mica capacine (temperature coefficient 0 to -50 persyminon).

	First Dat	Second Dot	Third Dot	Fourth Dat	Fifth Det	Sixth Dor
Cober	First Digit		Second Digit	Decimal Multiplier		Cheatteritics
Black		0	0	1		*A
Brown		1	. 1	10		†B
Red		2	2	100		-
Orange	indicate	3	3	1,000	indicate	-
rellow	to indica capacitor	4	4	-		-
Green		5	5		5 g	0.00
Blue	silver paper o	6	6		silver	-
Violet	A doc	7	7		A WS	-
Gray	N A	8	- 8	-	A M	-
White	ш.	9	9	-	100	-
Gold		_	-			-
Silver		-	-			-

*A. Operating temperature range, -67 to +185 F. †B. Operating temperature range, -67 to +167 F.





Fig. 66b. Molded Paper Capacitors: AWS Six-dot Color Code

	Tip	First Det	1 (Fourth Dot	
Color	Color Coefficiens		Second Dos Second Digit	Third Dat Decimal Multiplier	†Talerance	
Black	0	0	0	1	±20	
Brown	0.00003 neg.	1	1	10	st: 1	
Red	0.00008 neg.	2	. 2	100	± 2	
Orange	0.00015 neg.	3	- 3	1,000	± 3	
Yellow	0.00022 neg.	4	- 1	10,000	± 4	
Green	0.00033 ncg.	- 5	5	100,000	± 5	
Blue	0.00047 neg.	6	6	1,000,000	± 6	
Violec	0.00075 neg.	7	7	0.001	± 7	
Gray	-	8	8	0.01	± 2.5	
White		9	9	0.1	±10	

*The temperature coefficient is expressed in microniccolateds per microniciofated per degree Centigrade. Some expacitors are marked with a numeral instead of a color code; for example, N-030 expectent n00030 at the properties of the degree of the microniccolated on the control of a microniccolated instead of percopages. †Tolerances for capacitars of 10 microniccolated on the color in entire of a microniccolated instead of percopages.


Fig. 67: Tubular Ceramic Capacitors: RMA Color Code

PAR. 44

c. Tubular Ceramic Dielectric Capacitors. Tubular ceramic dielectric capacitors, which are widely used for temperature compensation, are sometimes marked according to the RMA color code shown in Fig. 67. As will be seen from the figure, the negative temperature coefficient is in:

TM 11-620



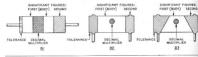

Color	Piess Significans Figure	Second Significant Vigare	Decimal Multiplier	Tolerance
Black	0	0	1	-
Brown	1	. 1	10	± 1%
Red	2	2	100	± 2%
Orange	3	3	1,000	± 3%
Yellow	4	4	10,000	± 4%
Green	5	5	100,000	士 5%
Blue	6	6	1,000,000	± 6%
Violet	7 .	7	10,000,000	± 7%
Gray	8	8	100,000,000	± 8%
White	9	9	1,000,000,000	± 9%
Gold	-		0.1	士 5%
Silver	-	-	0.01	±10%
No color	-	-	-	±20%

Fig. 68. Fixed Resistors: RMA and AWS Standard Color Codes

sicared by the color of the hand or tip at one end of the unit, the capacitance in microarcusfactable of the time, the capacitance in microarcusfactable observator, either in per cent or to micro da a micro-microfactal, depending upon the size of the unit, is indicated by the footn and last ode. Example: a 30 microarcostarcal pelse or minus 5-per cent proportion with an apparise remperature conflicient of 80 parts per million per degree Centigrade of 80 parts per million per degree Centigrade of 80 parts per million per degree Centigrade of 80 parts per million per degree (-80); for 60 per description of 80 parts per million per degree (-80); for 60 per description (-80); necessity (-90); necessity (-90); for 60 per degree (-90); for 60

A Fissed Resistents, Statil fased resistons, both compositions type and write-wound, as frequently marked with colored banels and does to indicate the resistance and olerance. Two color codes are wisely used: the RMA and the AWS. The two codes are not identical in all particular, but they are similar in many respects. One they are similar in many respects, they will be teen that in all cases the various continuation to the color of the color o

As illustrated by Fig. 68, two basic methods are used for indicating the resistance and tolerance:

Method A. This uses four colored bands, starting at one end of the unit, to show resistance and tolerance. The bands, reading from left to right, indicate: first significant figure; second significant figure; decimal multiplier; per cent tolerance. (The significance of the body color under this method will be explained later.)

Method B. Several variations of this method are in use (B1, B2, B3 of Fig. 68). With all of these, however, the interpretation of the code is practically the same: left end, tolerance; body, first significant figure; right end, second significant figure, central dot

or band, decimal multiplier.

To illustrate the basic schemes, consider a 5,600-ohm = 10-per-cent fixed resistor. It would be marked:

Method A. First band, green (5); second band, blue (6); third band, red (100); fourth band, silver (± 10 per cent).

Method B. Left end, silver (± 10 per cent); body, getcn (5); righe end, blue (6); central band or der, red (100).

In Method A, where the body color plays no part in indicating resistance or otderace, it may be used to indicate the type of resistor unit. Under the RMA colo, a black body if frequently used to indicate an unimulated composition unit; a tan, olive, or whire body, an insulated composition unit; and a dark brown body, an insulated wire-wound unit. The AWS code requires that an uninsulated unit using Method A have all back body; the body of an insulated unit may be any color, although a natural tan is preferred.

When there is doubt as to whether a particular resistor is composition or wire-wound, it is well to remember that any resistor of 100 ohms or less is very likely to be wire-wound—also, to remember that it may be wound inductively.

156

NOTE: The list of stock numbers is inclemed to supplement the older, force desart obtaing until such time as the catalog is system to force outside the stock numbers in this table, finds replacement put by stock numbers and shoulded.

tame and Description of Part

Signal Corps Stock Number

Number a. Media

Receiver Ec. 683-

101.8,03.8 101.1,01.3

915 36 98 200 17.50 406 Second I-F Spress By-pass Soculator Screen Dy-pass First Audio Orio Couplin Liniter Cathode Sy-pass 1-F Decillator Counting Lintter Screen Sy-pass Seating Geoillator Flate Filter brasitor. 0.75 ± 0.25 and, 500 volts de Purlable aly capacitor, 60 mpf, part of push-button turer assembly Cylmnor ospication, 16 pmf, part of pash-button Sumer assembly Capacitor, 0.006 pd. 300 rolts do Capacittor, 0.006 Mr. 300 volts do Caracter, 0.006 pf, 300 volts de Chrackter, 0,006 hg 300 volts de Sapacitor, 0.006 pf, 300 vella de barnettor, 0,006 uf, 300 volts de barnathor, 0.006 pf, 340 velts de Caraction, 0,006 pf, 900 rolls do Sapaeltor, 500 paf, 500 velts de indio Receives NO-683-4

> PA6-10 DE-20 D46-10

01-940

M 11-620

Piret Audio Grill Mas Filter

apacitor, 0.01 pf, 300 velts ds

5410-48

DA6-10

DA6-10

TM	11-6:		ę	12		v	. 5	UF	PI	EM	ENT.		DA	TA					
		E30-650354-7	250-680394-5					\$20-650334-4				350-650594-1							
0-D 2320 54	VI out?	0-D Type DER-6050	\$770 TLA-6020	0-D 773e 1U	0-D 7ype 3D	2-D Type 18		Cycle Vo-9's		52 E	T off	D-D Fer drawfrg	0-D 77pc DI-6100	2884	O-D Fype 1W	C-D Type 1v	35.3/2	E 1/2	
S-F Cutoff, First Audio Grid	I-F ANG Palter	AVC PILLOS	Plate Supply Filter	Squelch Tining	Squelch Timing	H.P Outeff, Second Audio Dria	Beater by-pass	Squelching Toltage Pilter	Pirst Audio Piete Pilter	Second Justs Orid Doupling	E-P Dutoff Become	Second Audio pathods By-pass	Second Audio Screen Sy-page	Fiate Supply Filter	I-F Cacillator Coupling	I-7 Caullister Coupling	B-F Screen Filter	Mobilator Serves Filter	
do still ood 786 ood farrande	Capacitor, 0.006 pf, 900 volta do	Capacitor, 0.5 pf, 53d voits do	Ospiettur, 2 pf, 600 valta da	Capacitor, 0.01 pf, 300 rolts do	Capaciter, 0.01 pf, 500 volts de	Capacitor, 0.002 pg 500 volts de		Ompasitor (3 x 0.1 pc) 630 veits de		Capacitor, 0.01 pf, 300 veits de	OMPAGITOR, 0.005 pf. 900 volta da	Special capacitor, 40 pf. 25 rolts do	Capacitor, 1 pf, 600 volts de	Capacitor, 2 pc, 600 rolts do	Cajasitor, 0.001 pf, 500 velta do	Objection, 0.0005 pf, 500 value de	Sealator, 20,000 obse s 105	Resistur, 0.25 nagohn a 10\$	Section and over a part
- I	Capacito	Ongwalto	Ospirates	Capacito	Capacito	Capacito		Ospanito		Capacifor	Capacito	Special	Capacitos	Capacitor	Capasitor	Capacitor	Sealator,	Kesistur,	Bareles Lan
-	3DA6-10	3EA500-30	XX88 - 6020	35410-48	SEATO-48	3042-16		30AL00-27		3000-48	8-Smx	30640-1	3561-61004	3082-88A	3041-13	329900-60	384550	324562	Subank
	1014	1015	1016	1017	1018	1019	1020.1	1020.2	1020.3	100	1022	1023	NOS N	6259	940	1026	187		183

157

Parotton Marks, Code and Contractor's Traction Towards Indice
William positions 1980, p. 198

M	1	1	6	
	Ī	ī		

IRC 2

Valtage Divider Shunt Phone Series

Masiator, 30,000 obms : 106

32630-7 324540

11188

W ************

													6-3				5-2
												K6-9712	BSL-684082-3				225-66A082-3
 IRO 805-1/5	280 HT-1/2	290.2/2	37-1/2	32-1/2	230 MY-1/P	275	1300 811-2	Z.be Z.	200	EC-1/2	H-1/2	E-3	N-E For drawing	C-D 2ype 58	U-D	Type Sh	Srão mresa
Phone Series	Separal Audio Servez Filter	Vollage Dividing Between	Voltage Elviding Network	Voltage Etwishing Network	Valtage Mulding Setwork	Voltage Dividing Setvork	Wolfage Diwiding Network	Audie Oniput Dumny Load	Waltago Elviding Setwork	Phone Series	Prome Series	Lighter Delhode Choke	First I-P Repti	First L-P Grid pergiling	First L-F 20th Filter	Mobiletor Plate Flack Undag	Tengentiure Competantor
Resistor, 90,000 come a 10%	Resistor, 5,000 chms : 106	Restator, 50 ches 2 56	Peninter, 9,500 chas + 56	Sesistor, 1,200 obns a 56	Seatstor, 2,900 chms a 96	Soutstor, 2,500 ches : 5#	Bosistor, 13,000 obse 2 96	Seafator, 5 obse z 56, 1 in.	Besistor, 6,800 chos # 56	Sesistor, 30,000 ohus = 10%	Besister, 90,000 ohme z log	Choke (50-1002)	Piller	Capacitor, 100 maf # 596, 500 walts do year of FLIA	Caracttor, G.001 af. 960 volta de Part of Fila	Capacitor, 50 par 7 Mg, 500 voite de Part of Fila	Onpueltor, 10 1 1 ppf, 500 volts do
324540	324526	326005-13	926250-6	326120	326290-6	326250-6	326613	324805	325568-1	324540	324540	2C4403A/07	2011/00-6834/91	3291co-19A	SUA1-22	309050-13	309010-5
													•				

*Notification during manufacture; see Foregraph 43.

1833

1926 1926 1926 1929


10 1 10 10 10 10 10 10	Nadio R	Netho Receiver NO-685-A (continued).	Name And Description of Part continued).	Pasction	Type Suster	Drewing Rusber
1999-3-1	60	35010-5	Ospacitor, 10 a 1 was, 500 volts de Fart of Falk	Terperature Compensator	Price addon.	
	99	309050-13	Capacitor, 50 ppf 2 36, 500 volts do	First I-F 6rid Fired Tuning		
1900 Outside 15	25	3246-10	Capacitor, 0.006 pf, 300 volts do Fart of Fild	Modulator Flate Filter	O-D type 1W	
19500 Section 185 State 185 Stat	22	324990	Resistor, C.1 megaba # 105	First 1-F Grid Leak	130 137-1/2	
1990	95	6 326643	Remistor, 45,000 otus a 106	First 3-F Input Filter Tormination	130	
1990	2	324550	Neatator, G.1 megotm # 10#	Piret I-F Grid Filter	M7-1/P	
1999 Parties 198	×	324550	Sealstor, 0.1 magehm # 10%	McCulator Plate Filter	200 20-1/2	
	5	324550	Sesistor, 0.1 megolm : 106	Modulator Plate Filter	34-1/2	
		80440M/09	Coll Part of Filk	First 1-P Grid Tuned Coupling	NE drawing	880-680859-1
	2	2044034/09	COLL PAPE OF PLIA	Modulator Flate Tuned Coupling	NE drawling	1-56099-01
NORMAN AND AND AND AND AND AND AND AND AND A		204460-683A/92	Filtor	Swoond I-P Input	NE Deving	B51-684062-1
Mal. 20 Section 2, 50 at 1,50 at 1		XD5100-19A	Capacitor, 100 mpf * 55, 500 volts de Part of PLSA	Second I-P 2:16 Coupling	0-D Type 58	
20090-1.3 Operating that 1 kg, for onth in Figure 1 7 fines from the fining of the first fine from the fining of the first fine fine fines from the fining of the fining o	.00	3DA1-22	Capacitor, 3.001 pf, 500 volte do Part of Filsa	Second 1-9 Orid Pilter	0-D 7376 18	
19910-5 Ougstire, 12 1. ps. 5, 90 raits de fraggalere compansion 19910-5 Ougstire, 12 1. ps. 5, 90 raits de fraggalere compansion 19900-1 Ougstire, 12 1. ps. 5, 90 raits de fraggalere compansion 19900-1 Ougstire, 17 ps. ps. 1 2 56, 90 raits de fraggalere compansion 19900-1 Ougstire, 17 ps. ps. 1 2 56, 90 raits de fraggalere compansion	20	X05050-13	Capacitor, 50 pp. 2 pp. 300 volts de Part of PLEA	First I-F Plate Fixed Tuning	0-D 75pe 53	
N9010-9 Ogsatica, io 1 km/r, 500 valts do Passeshiwa Campasaston Passe of Files. 100 valts do Passes 1-7 deals Files N9050-13 Ogsatica, 5 mf f 2 %, 900 valts do Remai 1-7 deals Filesa N9050-13 (1972) 5 mf f 2 %, 900 valts do Remai 1-7 deals Filesa		359010-5	Capacitor, 10 t 1 pp.f., 500 welts do	Temperature Compensator for 053	Eric Sele	
309050-13 Oppution, 50 pag 2 5%, 500 rolts do Second 1-P Orid Fixed C-D Part of Figh		329010-5	Capacitor, 10 ± 1 pp.f. 500 rolts do yest of FLAA	Praparature Compensator for 056	Erie Heson	
-	19	309050-13	Capacitor, 50 paf 2 96, 500 rolts do Part of FLAM	Second I-F Orld Fixed Puning	D-D 1700 SR	

					M30-680859-1	MSO-680255-1	ESL-684082-2	ESL-6540B2-2										
Type 1V	ER-1/2	IRC BF-1/2	275	5	The Graving	Ter Graving	For drawing	7730 58	25.00	VI out?	Sys St	Er to Type wedox	Erie Nésuk	Type SR	Type 18	2/3	4	5
95	H	HI-	DE STATE	TRC 1/2	92	No.	707	2776	34	0.0	94	A P.	Type	Type	Typ.	87-1/2	130 87-1/2	280
riret i-y Plate Pilter	Second I-7 Grid Leak	Second I-7 Ingut Filter Seraination	Second I-P Orld Filter	First I-P Plate Pilter.	Second I-P Grid Tuned Coupling	First I-P Fiste Tuned Compiling	Limiter Lapat Pilter	Limiter Japat Pilter	Limiter Orid Coupling	Limiter Send Filler	Second 1-F Plate Pixed Paring	Semperature Compensator for C(3)	Temperature Compensator for Ope	Limiter Orid Fixed Tuning	Second I-P Plate Pilter	Limiter Orid Leak	Limiter Orid Leak	Limiter Input Filter Formication
Capacitor, 0.005 af, 500 volts do Nart of FL2A	Resistor, 0.1 megadas z 106 Part of Figh	Restator, 47,000 obsa z log	Resistor, 10,000 shae a 108	Resistor, 1,000 obus s 108 Fast of Figh	Coll Part of FLSA	COAL OF FLOA	Pilter	Oapacitor, 50 mar a 54	Capacitor, 100 par # 5#, 500 valts de Part of FLJA	Oapseitor, 0.001 pf, 500 rolls de Part of Mila	Capacitor, 50 ppf 2 96, 500 wolts do hart of Pays	Capacitor, 10 z 1 ppf, 500 volte do Fast of FLSA	Capacitor, 10 m 1 pgf, 500 voits do Fart of PLAs	Capacitor, 50 ppf # 56, 500 volts do Part of PL3A	Capacitor, 0.006 pf, 300 veits do Part of PLAA	Resistor, 0.1 megshm : 108	Zesistor, 250,000 chas s 106 Fart of FLAA	Part of FLAA
3866-10	324550	26693	321529	324545	2014034/09	2044034/09	2C4460-583A/P3	309100-13	319100-194	3141-22	319050-13	329010-5	2500005	329050-13	35W6-10	055426	295426	326643
190	198	398	863	Bbs	197	1,68	17LM	140.	140	2773	543	460	54.0	940	14.0	144	*371	872

	AR. 4	15	1	RA	DI	0 5	ETS	sc	R-6	08-	A /	ND	sc	R - 6	28	A		TM	11-6
Ending of The Parish and The Parish	Drawing Number					Eso-680255-1	ESD-680855-1	EEL-680250-1											
and the state of Paris	Tre Surve	100 H	2H0 ME-1/2	2/7-M	270	Fer drawing	VE drawing	VE Per draving	0-D 2370 SV	Cape 1V	0-D 737e 1V	No. 14 No. No. O. W.	25 pe 58	C-D Type 58	C-D Sa	Brite N650K	130 HF-1/2	INC M-1/2	
Manual Distriction of Part Control of Part Con	Punction	Limiter Input Filter Persiantion	Limites Grid Pilter	Second I-y rists Filter	Second 1-9 Plate Filter	Limiter Orid Tuned Coupling	Second 1-P Plate Pared Ovepling	Discriminator Filter Network	Detector N-F By-pass	Detector Cathride Filter	Limiter Plate Filter	Temperature Compensation for Slope Circuit Secondary	Sair of Maps Circuit Secondary Puning	Half of Slope Circuit Secondary Cuning	Limiter Plate Fixed funding	Superature Compensator for Off	Detector Load	Detector Cathode Blas	
	(continued).	New Section, 30,000 chas a 106 Part of FL3A	Resistor, 10,000 okes a 109 Part of FL3A	Part of FLMA	Resistor, 1,000 obms : 106 Fast of FLSA	COLD PLAN	Part of MAN	Filter	Capacitor, 250 mpf a log, 500 valte do Part of FLA	Capacitor, G.006 p.f. 900 volta do Part of File	Ospenitor, 0.006 pf, 300 volta de Part of Mia	Obpositor, 5 2 0.5 ppf, 500 volts de Nart of Fild	Ospection, 50 pair # 36, 500 volts do Furt of MiA	Ompression, 50 mpf # 25, 500 volts do yest of FiA	Capacitor, 25 ppf 2 76, 500 rolts do	Capacitor, 10 t 1 ppf, 500 volts de Part of 214	Resistor, 70,000 chas # 106	Restator, O.25 megokm # 10% Part of FLA	*Modification during manufactures and Tensors his
	Rumber a. Sadio He	*872	нт.	BTA	PHAP	m	745	1924	180	095	690	480	630	930	84	880	193	182	*Modification

-						-			L C MI			-						PAR.
								•	-1							4		
			880-690654-3	E30-650294-4	127-694060-3			220-684085-5	ESL-68408:-1					230-681063-1	850-684083-1	XXC-694079-3	ESE-694190-1	
130 80-1/2	IBC 1/2	BC-1/2	KE Fer craving	Per Graving	Per drawing	Q-D Type 18	190 81-1/2	YE Per drewing	NE GRENING	Eric Media	Erle Most	77pe 1K	100 37-1/2	For Grewing	WE GRAVING	WE drawing	Yer drowing	0-D
Detector Load	Datestor Cathode Bine	Liniter Plate Filter	Defector Japut Fused Ocupling	Limiter Fiste Tuned Coupling	Antenna Ouspiling	BP Grid Filter	R-F Grid Filter	Antenna Coupling	Modulator Input Puning	E-7 Plate Tuning and Compensation	Modulator Orid Tuning and Compensation	S-7 Plate Filter	R-F Plate Filter	8-F Plate Funed Coupling	Modulator Brid Tuesd Occpling	N-F Oscillator Tuning Bail	E-F Oscillator Tuning Unit	Series Pedder
Resistor, 70,000 ohms # 10\$ Nart of FLA	Resistor, 0.2% megokm : 10% Part of FLA	Sesiator, 1,000 obns : 106	Cott Part of Fal	Cott Cot Past	Complies Deat	Ospection, 0.006 at, 500 walks de Part of LOTA	Resistor, 0.25 regolm : 134 Pars of LCUIA	OMI TANK OF LEGILA	Coupling unit	Ougheiter, 10 : 1 paf, 500 volts de Part of Létal	Ospacitor, 5 # 0.5 ppf., 530 valta de Parc of LOTEA	Capacitor, 0,006 pf, 300 volta do Fart of LCGZA	Neafetor, 1903 ohms : 106	Coil Part of Louis	0011	Tuned unit (unrealed)	Tured unit (sealed)	Capathor, 700 ugf 4 36, 500 voite de Part of LOUSA
326670-1	324562	324585	2014/034/010	80/YC01608	\$04460-683A/Y4	3046-10	324962	204460-683A/CI	204460-683A/95	2000000	709005-13	3DM6-10	324525	2C4460-683A/CE	2C4460-6534/c2	2C4460-653A/FG	204460-683A/NG	31597.00
863	*8#	8895	181	1,92	PLOUIA	602	137	132	11,012.6	963	cys	660	828	1.33	1.34	NOUN	*11,0000	09.1

AR.	15	_	R A	DIC) s	ETS	sc	R - 6	08-	A /	ND	50	R - 6	28.	A	-	TM
Traving Number									E80-684084-1	ESL-680247-1					,		
type Number	Er te Pype McGOX	fape 58	Eric Figur	Erte Robot.	Muter Type M200L	Syle 58	Type B660K	1310 BIT-3/2	ver drawing	Yer drawing	0-D 7776 SR	Type B683K	Type SR	D-0 54	IRC BF-1/2	INC DT-1/2	180 27-1/2
Pasetton	Pemperature Concession for Oil	Besting Ceciliator Syid		Sesting Oscillator Plate coupling		Coullator-Modulator Coupling	Beating Cantilator Plate Temperature Compensation	Mobilator Suppressor Orid Lesk	Beating Cacillator Pusing and President	I-F Cecilister Paring	I-F Coullistor Grid Coupling	1-9 Oscillator 7late Shant.	1-7 Occillator Pixed Public	I-P Coellister Plats Compiling	I-P Castllator Orid Leak	1-P Geefilistor Plate Load	1-9 Cacillator Plate Load
hase and Description of Part continued	Osymotton, 200 : 10 mg.f., 500 walts do Part of LOUSA	Capacitor, 100 pp.f # 55, 500 volts do Part of LOUSA	Ospanitor, 30 z 1.5 maf, 500 volts do Part of LOUSA	Capacitor, 30 a 1.5 pgf, 500 volts do part of LCOSA	Onparitor, 30 a 1.5 paf, 500 volta de Part of LOUSA	Capacitor, 100 par # 36, 500 volts do Part of LOUSA	Capacitor, 20 t 1 ppf, 500 valts do Part of LOUSA	Nesistor, C.1 magolm : 10%	Part of LIUSA	Puned units	Capaultor, 50 ppf t 56, 500 volta de Fast of LCDA	Ospanitor, 50 t 9 ppr. 500 volta de Fart of LCDA	Outsettor, 100 ppf # 56, 500 volts do Fart of LODs	Capacitor, 50 par 2 55, 500 volts de Part of LCDs	Resistor, O.1 megohm : 10%	Resistor, 40,000 chas a 106 Fart of LCUS	Nealston, 40,000 chms # 106 Fart of Loth
Nosher Stock Bisher	3D9800-6	3D9100-19A	1	309030=3	1	3D91.00-19A	309080-1	324550	204460-6834/03	2044034/21	309050-13	30370	V61-001636	309090-13	224550	224549	646424
Rosher Radio E	340	640	+04	140	*60*	646	980	341	143	Lots	160	635	663	460	191	892	N93

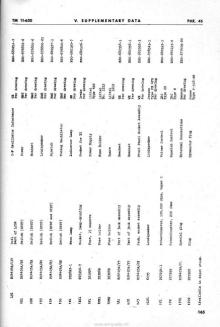

PAR. 4	5	_		RA	DIO	5	ETS	50	R-	608	- A	AI	N D	sci	8-6	28	. A		1	M	11-6
Contrador's Lenging Susper	E50-683958-1	ES-8714											331-678315-6 331-678315-10	E2-10059.		E00-684095-1	E20-684036-2	250-684058-5 250-684056-1			
Eype Sumber	VE Granding	25.	304 (540?)	(5507)	(55%)	MCM (15207)	MCA (10907)	(GAUT)	(90%)	30% (69%-32)	BOA (681,7-09)	BOX. (661.7-07)	Chitsd 7er Gravings	5	g						
Fortier	Proct Panel Commeticas	Autho Output	S-F Asplifter	Modulator	Oss1114;3F	I-F Asplifter	I-F Amplifier	Listter	Detector	Second Audio Applifior	A70 and Squalet.	First Audio and Oscillator	Dooler t	Positog	Fraing						
Name and Description of Part antimose).	Flug, part of jack assembly	Audio auspat transformer (50-1005)	Vacuum tube VI-112	Vacium tube vP-112	Vacuum tube VP-94	Waters tube WF-209	Vacuum tube VP-209	Vapuum tuhe VP-112	Vacuum tube 19-90	Vacuum tuke VF-L07-A	VActum tube VI-229	Varian Sale VI-229	South	Ca.2, Ci.3, Ci.4, Ci.5, Ci.5, Ci.7 and Ci.5)	Locking nesembly, part of push-button tuner weesship, consisting of:	Retainer yoks assetbiy	Char	Yoke lock servin	1/4-26 (852) nex. mult 3/8 im. norces	1/4-26 (EG3) hex. nut 3/5 in. across	THE WORLD THE CONCENTRAL DIMENT
Number Stanki Derga Number Stock Number Padto Reseiver BC-653-A (continued)	2044034/73	204403A/T2	21712	21112	2794	21209	21209	21112	0646	SCHOOL	52259	62228	2014034/52	20M034/25.1	808494/36/8						donthly in dance about
Number Number	504	1.0	1/4	43	73	54	8.4	9.4	2.4	vě	64	V10	VS1-								dentlable 4

TM	11-62	0	_	-	201	V.	SU	PPL	EM	EN	TAR'	Y DA	ATA	-	-	_		PAR.	45
E5-10099	330-678546-2	EBO-675764-16	K85-678764-20	330-690129-2	E80-660492-1	E80-690495-2	BSO-660382-3	M38-575445-10		380-677334-11	E80-660841-2	ESO-678672-1	880-695720-1						
24	wg Fer drawing	Ng Per drawing	Ver draving	VE Graving	Ver drawing	NE fraving	NE GREVING	NS drawing	Szug	WE drawing	NE drawing	WE Grawing	VR No draving				0-0 0-0	0-0 77pc 1873	
String.	Prost Pasel Protection	Antenna Connection	dround Connection	Securing Receiver	Antenna Jack Contractions	Antenna Post Commetitons	Volume Control Each	Cover	Securing Cover	Roughlag Nat.	Newoling Stating Posts A and 0	Proof Panel	Mounting Small Parts				Pirst A-P Streen By-yans	First 2-F Fiste Coupling	
ther assembly	Front panel guard	post A	pres o	Bracket, hold-down	Michided wire sesembly	Chielded wire assembly			Makeproof fastemer	nezes			strip	Sardware for Radio Receiver NG-685-A Mire for Radio Receiver BG-685-A		Madic Franklitter SC-594-A	Ongaetter, 0.303 pf., 800 vaits do	Capacitor, 0.0001 pf + 56. Sco voits de	
toper as	Font p	Sinting post A	Sinding pest 0	Spiroket,	Shielded	Chielded		Dust cover	Shakepro	Special sores	Insulator	Bandle	Mounting atrip	Hardware Wire for	4:	Radio Tre	Onpactor	Capacitor	
* ACREATOR COLOR	2044034/01	2044034/81	2044.03A/BE	204403A/B9	204403A/N1	SONASA/VR	201460-683A/XI	201160-6834/022	20649AA/92	2094038/21/1	204403A/33	2044074/III	2044034/81	28508/11	b. Radio Transmitter Ec-684-a.	A489-048008	3-6406	109100-51	tkrailable in depot stock.
			_	-					+						b. Radio		10101	10103	* Kraflable

PAR.	4:	5		R A	010	\$1	TS	sc	R-60	8 - A	AND	SCI	R - 6	28-	A	TM	11-620
Draving Number																	
Tyle Burber		C-D fype IMPS	Property Person	2	C-D Type 1VPS	C-D 1978	Type 1875	C-U CAST	NA.	¥	g	24	Type 1878	Pype 1875	p	B	
Pastion		Capillator Fiste Eg-pace	Opelilator Plate Tening	Rectifies Getd Tuning	Rectifier Orld Coupling	Rectifier Suresn Sy-pass	Tripler Plate By-pass	poubler drid By-pass	fripler Plate Tuning	Tripler rists Trianer	Doubler Orth Puning	Doubler Grid frimmer	Doubler Screen By-yoss	poubler Plate Sy-pass	Dombier Plate Tuning	Doubler Plate Primer	
Hans and Description of Part	(complumed).	Capacitor, 0.0005 pf, 800 relts de	Oupsettor, 15 upf # 10\$, 500 valte do	Variable air capacitor, 350 ppf. Fart of push-button tuner capacitor ansambly	Capacitur, 0.0005 pf, 800 volts do	Ompanoitor, 0.003 µZ, 800 volts de	Oapsoltor, 0.005 pt, 800 velts de	Capabitor, 0.003 pf, Sco wells do	Variable als ospector, 60 per, Yar of push-busten tuner capacitor assembly	Tariable air chaetter, 20 mpf. Yat of pust-butten tunst expector assembly	variable air capacitor, 60 par, Yar's of push-button tuner espection acasemity	Variable air capicitor, 20 ppf. Yart of public bulken tuner capacitor assembly	Capacitor, 0.003 pf. 853 voits do	CapAcitor, 0.003 pf. 803 volts do	Variable air capabiltor, do uni- Fart, of pumb-button tuner papeoffer Assembly	Wariable air capacitor, 20 ppf Mari of push-buiton tuber capacitor assessiy	HOTE: Capacitors clof, Clij, Clij, Clij, Clig, Clig, Clig, Clig, Clig, Clif, C
Stank Supper	b. Radio Pransmitter BO-684-A (continued).	303500-80	309015-2	See Note	309500-20	3043-6	328.3-6	3243-6	Bee Hote	See Note	See Note	See Note	3DA3-6	3043-6	See Note	See Note	20, 0153, 0157, 012 50, 0153, 0157, 012
Nuber	. Radio ?.	1010	0105	9010	9010	60101	11101	6118	\$110	*****	6110	9110	TEED	81104	6113	10320	BOTS: CR

A continued from the part of t	
The state of Tables From 1979, 13 There supplies that the state of the state which the state of	Caymestor, 0.003 pf, 800 voite de
There dustifies these from the part of the	Cajasttur, 0.01 af, 300 volts do
to whether the control of the contro	Onjactior, 0.000 pf, 1,250 volts de
The shall be the passes of the shall be the shall b	Warishis air capacitor, 60 pail Nart of push-button tuner sassably
The annual bank have to the state of the sta	Cartable air capacitor, 20 spf. Fart of push-button tuner assembly
the date of the press. It is not known to press	Variable air capacitor, 100 paf Part of push-button tuner sesembly
An investment checking \$50,000 for the control of t	Capacitor, 0.5 pf, 600 volts de
The state of the s	Capacitor, 600 volts de Pro sections, each 0.1 pf
connection states with a property of the control of	Okpatior, 0.5 pf, 600 volts do
The state part of the state of	Electrolytic ompacitor, 30 m.f
House dailed dead they see a page inter-cell from the first that years a page of the first see a page	Capacitor, 0.5 pt, 650 volta de
Decond andin Gereen Repass Trate Supply Filter Ostillaber Sereen Ny-pess Frest n-7 Flate Pedding First n-7 Flate Pedding	Capacitor, 600 valta de Two sections, each 0.1 pf
Flate Supply Filter Ossilator Screen No-pass Flate N-P Flate Padding Flate N-P Flate Padding	Capacitor, 0.5 µ2, 600 volts de
Ossillator Suress Ny-pass First N-P Plate Padding First N-P Plate Padding	Capacitor, 2 pf, 1,000 velts do
Piret B-P Plate Padding First B-P Plate Padding	Capacitor, 0.005 pf, 830 volts de
Pirst B.P Plate Pedding	Ospanitor, 175 pp.f a 36, 500 volts de
	Capacitor, 175 par # 26, 800 velts de

Drawing Suber	. 4:	5		RA	DI	O SE	rs s	CR-	608	- A	AND	sci	2-61	28-4			TM 1
															ED0-678687-5		
Mr.'s. Code and Tage Bunker		Sylve 14PS	fype t	Fape 1475	C-D Type 5878	g.	¥	C-D Type 18FS	0-D 77pe-19F5	22	9	Type 1875	0-0 220-10	C-D Type 94PS	C-D AVL	Cype 1878	2/1-1/2
Percetton		Yower Amplifier Orld Sy-pass	Power Ampliffer Fiate Coupling	Ossillator Fiste Coupling	Ossillator Grid	Sectifier Plate Turing	Rectifier Plate Trimmor	Restiffer Plate My-pass	Tripler Grid By-pass	Tripler Grid Fusing	triples Orid Trimes	Pripler Screen By-yess	Pripler Pilament Sp-pass	Transmission Line Series	Dynamitor Selay Filter	Tripler Plate By-pass	Oscillator Grid
Mane and Description of Part	A (continued),	Capacitor, 0.003 pf. Soc volta do	Ospanitor, C.001 pf, 1,200 volts de	Oapsoltor, C.001 gf, 800 volts do	Oapsaitor, 0.00005 pf ± 55, 800 volts do	Variable air capacitor, 60 ppf Aart of push-button tuner capacitor samemity	Warishie air ospecitor, 20 wef Part of push-button tumer ospecitor assembly	Capacitor, 0.003 pf. 850 volts do	Capacitor, 0.003 pf, 803 volts de	Wariable air ospecitor, 60 per Park of push-button tuner cancellor assembly	Variatic air capacitor, 20 mpf fart of gual-button turn respective assembly	Oapholtor, 0.003 pf. 800 velts do	Ompasitor, 0.01 pf, 300 velts de	Oxymettor, 0.0001 pf, 800 volts do	Electrolitic ospector, 4 p.f., 70 raits de	Capacitor, 0.003 pf, 1,000 volte do	Resistor, 100,000 obms # 106
Signed Corps Stock Number	b. Radio Transmitter BO-681-A (continued).	3043-6	3041-21	3041-72	(5-05060K	des Mote, yags 168	See Note, page 168	3-2425	3-CYCK	See Note, page 168	See Note, page 168	3.043-6	30410-48	399100-70	20(4944/02	3DA3-6	324550
Reference	b. Radio	10148	10119	10150	10191	0152	10153	102.54	10155	9500	10157	10158	65104	10161	10162	*10164	10184

10.00 10.0	1770 7	V-L Oype A	INC.1	130 BT-1/2	MO MI 1/2	200	130 87-1/2	A-8 08-1	380 88-1/2	220	280	1750	77,000	BW-1/2	V-1.	200 200-2	200 BT-1/2	280	130
	Migh Folloge Reducing	High Voltage Reducing	Pirel S-P Screen	Reutifier Grid .	Rectifier Street	First R.F Grid Metering	Doubler dead	Doubler Grid	Doubler Grid Metering	Doubler Screen	Rectiffer Orid Metering	Ampliffer Grid	Amplifler Orid	Ampliffer Orid Mctering	Filesent	Applifier Screen	First Audio Orld Loading	Amplifier Streen	First Audio Brid Filter
	or, 2 in., 1,000 obus # 10\$	or, 2 in., 667 ohms ± 10%	ver, 250,000 chms a 10%	or, 70,500 ches ± 10\$	ar, 50,000 chms = 10#	or, 100 chas * 106	or, 30,000 obas a 10\$	or, 30,000 obne # 10\$	or, 30 chose ± 56	de, 75,000 obms ± 109	or, 1,000 ches ± 10\$	or, 15,000 okms # 10\$	cr, 30,000 chars a log	or, 10 ohms : 10%	or, 1-3/4 In., 1.0 ohm # 5#	ne, 30,000 obms # 10\$	or, 100,000 obus : 106	ar, 30,000 abms t 10\$	or, 50,000 ohms # 10#
		Sansata Restati	Sa6T25-5 Resist	326670-1 Resist	yateyat Resiste	926010-18 Resfeto	929540 Nestato	326630-21 Pesisto	NZ5005-13 Resista	325675-10 Resista	32A525 Resisto	326615-14 Resisto	326590-6 Restate		324801-1 Featsto	326650-7 Resisto	324550 Resista	Széggo-7 Resisto	324531 Resisto

has and Depositation of Parts matter, 50,000 chm s 106 stater, 100,000 chm s 106 stater, 1,000 chm s 106 stater, 1,000 chm s 106	Practice Desilator Plate Desilator Plate Medilior Plate Medilior Plate	Mrr's. code and Syse Euglar 250 E	Contsecon's Praving Fuller
sistor, 200 ohms 2 106 sistor, 100 ohms 2 106 sistor, 200 ohms 2 106 sistor, 10,000 ohms 2 106	Carbon Misrophume Pilter Carbon Misrophume Pilter First Audio Soresa First Audio State Pilter	24.17 24.17 24.17 24.17 24.17	
stator, 10,000 obes 2 106 stator, 5,000 obes 2 106 stator, 75,000 obes 2 106	Second Audio Orid Filter Second Audio Orid Becond Audio Sureso	M-1/2 M-1/2 M-1/2 M-1/2 M-1/2	
statur, 2-3/4 lm., 3.0 obs. 1 96 statur, 2.0.000 obs. 1 106 statur, 2 lm., 5,000 obs. 1 106 statur, 2 lm., 100 obs. 1 106	Filement Eidertone Fired Miss Eise	7 045 115 115 115 115 115 115 115 115 115 1	
stator, 2 In., 12 chas a 54 stator, 2 In., 12 chas a 54 s acceptable by.	Filesent Supply Series	Take Y	

| March 1982 | Mar

18129

Spinstote Relay Series late Oursent Retering

Pilament Supply Series Filament Supply Series

Martin, 100 date 1155
Pestitor, 50,000 date 115
Pestitor, 20,000 date 115
Pestitor, 2 lo, 12 date 2 g
Pestitor, 2 lo, 12 date 2 g
Pestitor, 2 lo, 12 date 2 g
Pestitor, 100,000 date 115
Pestitor, 100,000 date 135
Pestitor, 100,000 date 135

Plret 3-P Grid

Decillator Screen Meter Series

Tripler Orid Metering

Sectifier Screen Shun Tripler Brid Lesk Tripler Screen High Voltage Reducing

Decillator Grid Anti-Sing leater for Orystal Oven First Audio Flate

resistor, 50 chas a 106 with Lilly Nesistor, 100,000 ohme m 105

Resistor, 50,000 obus t 10\$ Resistor, 2 in., 667 obus t 10\$

725,95647

R145 IRLAY 81149 maistor, 6.3 opps 1 10\$

173

seistor, 1-3/4 in., 80 chms 2 106 Basistor, 30,000 chms # 105 Besistor, 1-3/4 in., 30 chms # 105

Seatstor, 30,000 chas # 109

irel Audio Spreen Shan

intense and Dischling

8-01092 324530 324530 324512 124512

18139

3140 13141 3142

	some edit	Antenna Statio Leak INC 85-1/2	A-F Load Din	Tripler Plate Filter INC.	Tripler Plate Filter INC.	122 Fours Asplitter Grid 175 R50-680390-2 Astl-Sing Fee Cavaling Fee Cavaling	Doublar Soresa Sount 190	High Voltage Reducing N.L. Type A.	Amplifier Orid INC.1	Cesiliator Flate 1380	Oseillator Piate INC Br-2	Atderson Control. The CP HD-680249.6 Type CP FT Security.	2 First B.F Pinte Choke MR Per drawing E50-660045-9	Oscillator Flate 75 drewing E80-660243.4	Al First S4 Take Tuning NE Per drawing E50-690077-2	Modulation MR D-164820	
Was and Taxonfolion of San	(gontinued).	Resistor, 100,000 ohms t 10\$	Resistor, 30 obms # 10%	Reelstor, 500 chas 1 log	Resistor, ydd ohns i 106	Sestator, 50 ones a 105 with L122	Pesistor, 100,000 obms 2 109	Resistor, 2 in., 667 obes 1 108	Resistor, 90,000 obset 106	Resistor, 100,000 chas s 106	Heafstor, 100,000 ceme : 109	Potentiometer, 50,000 cham	Coil, 3 millibearies, duclateral	Coll, I milliberry, duclateral	Coil, 0.38 millibenry, duclateral	Setardation soil (80-1003)	A. 10 at 15
Signal Corps	b. Redio Transmittor BC-686-A (continued).	384550	1-500985	326030-5	326630-11	6-50092K	324608	325,96647	326630-8	386700-12	386700-12	22208-3	205494A/08	206494A/09	206530-6844/010	2064944/011	OTHER AND AND AND
Reference	b. Redio	1B155	1R156	+B15T	*##15T	18158	18159	18160	19361	18362	11163	1014	12101	12102	*L103A	*1230	417704

*Notification during manufacture; IAvailable in depot stock.

м	11-62	0				_	V.	5	UP	PLE	M	N	TAR	Y	DAT	A	-				PAR	. 45
	380-684453-1	320-694453-2	X80-584455-1	X30-654455-1	\$30-GB0330-2	E20-684453-5	\$50-684457-3			E80-680390-2	ES-8715	E5-8715	ESO-681226-1	E80-680389-1	ESO-677080-3			850-676800-10	mo-67600-10	880-676800-81	ESO-680330-3	
Per drawing	VS Fer drawing	WE drawing	Fer drawing	Fer drawing	Fer drawing	Yer drawing	Fer drawing	Chaite	Cleatte	Fer drawing	9	20	Allied Per drawing	Allied For drawing	Allied Per drewing			Nak Per drawing	Nam	Nak Per drewing	Mailory Type 32261	
Brenny pages andres	Doubler Orld Tuiting	Doubler Plate Tuning	Amplifter Output Funfag	Antenna Coupling	Oscillator Grid Anti-Sing	Tripler Orid Funing	Rectifier Flate Tuning	Power Amplifier Plate Choke	Fower Amplifier Grid Choke	Power Amplifier Grid Anti-Sing	Missrophone Input	Audio Output	Antenna Switching	Systemator Starting	Receiver Mashing	Quarts Plate Selector	Antenna Capacitor Selector	Panel Noter	Receiver Tune	Power Supply	Circuit Test	
executive somewheater arrow	Coll, close-wound solemoid	Coii, close-wound solemoid	Cail, apson-wound solomots	Cail, speas-wound salemoid	Got1, wound on \$249	doil, closs-wound solenoid	doil, close-wound splenoid	Coil, 21 choke	Coil, 21 choze	Coil, weumed on 8155	Audio imput treasferner (SI-1005)	Audic output transformer (30-1005)	Relay (coil resistance, 44 chart 2 SK)	Moing (coll resistance, JT chas, ain, 73 chas, max. 84 chas)	Selay (coil restatable, 90 chms)	Switch (SPST), part of push-button tuner assembly	Switch (BFST), part of push-button	Toggle switch (1957)	Togale owitch (IFDT)	Toggle switch (2007)	Switch, with slotted shaft 1/2 in. long	
CTO/WACD-OCCOPY	205530-684A/013	306530-684A/014	20653C-684A/015	206530-684A/015	2064944/016	2065 yo-684A/317	205530-6844/017	206530-684A/21	206530-6894/01	2054944/016	20649ta/TE	205494A/E3	205494a/RP	2004944/83	2064944/85	E	1	2064944/83	2064.944/83	2064 944/54	2064944/85	tAvailable in depot atcok.
977	1017	1108	1110	TITE	1117	1118	6111	1.120	1121	1122	1203	7102	19193	9104	18105	plot to plic incl.	plil to	19161	8755	pret	10125	Available 2

PAR. 4	15		RA	DI	o s	ETS	s c	R-60	8 - A	AN	D :	CR	62	1 - A		TM	11-
Contractor's Draving Busher				280-680353-3				E80-680843-7	ESS-680843-5	ESD-680941-1	330-680241-7	320-680302-7	E30-677409-19				
Wir's, Code and Type Murber	Type 440	Catalog No. 1712	littel Catalog No. 1212	Aughenol Per drawing	24.50	70000 r-400-43	Junes 7-4c6-43	Marca T 1-3/4 651 Base	Drako Par drawing	Model No. 907 Per drawing	Meston Per drawing	Spanes Fer drawing	Cannon Per drawing	RCA (1519)	3CA (16:9)	(36.9)	
Panatton	High Tollage	Fuse Solder	Spare Puse Solder	Dynamics Migrophone	Carbon Microphone	Dynamicor Flug	Dynamotor	Pilot Light	Societ for Pilot Lasp	Tuning and Antenna Current	Antenna Current	Ovem Control	External Connections	First R-7 Amplifier	B-F Sectifier	Poubler	
Name and Description of Part (continued).	Fuss, 1/2 axpere	Puse post	Puse jost	Jeck, 4-contact competer	Jack, with mickel-pisted sleave	Flug. 1/16, eight-contect plug	Plug, 1/16, eight-contact plug	Lamp bulb, 26 volte, 0.17 ampere	LAmp mounting	Motor	Thermocouple, 120 ms. radio frequency	Thermostat.	7Jug	Vacuum tube, VI-164	Would jube, 77-164	Vacuum bubo, VT-164	
Notice Signal Corps Name Same : Notice State State State State Same : D. Radio Cranamittee SC-684.4 (continued).	X2595.3	72,7262	25.72/28	2064944/81	825575	24/446902	2069494/72	9525956	225990-2	yebpi-r	174-01646	22,9185	2064944/PI	92164	22364	49128	
Neference Surber	19101	PRIOL	1 24102	10101	1,3102	110103	1 POLCH	19101	, KELOL	10134	101014	totd14	10104	1014	\$01A4	\$07A1	

Vesuse tube, VF-155	Power Amplifier	(1524)		-
Wenuts tube, VT-154	First Audio Amplifier	(1519)		11-6
Vasuum tube, vr-164	Second Audio Amplifier	SCA (1519)		
Various tube, VT-164	Ossillator	(3619)		
Vaccoun tube, 77-164	Tripler	NCA (3519)		
booket	bookst	United Fer drawing	ZBL-678315-3	
Scoket, Jeslantile, 5-press	Bocket	National Type CIR-5		V. \$
Telebrator times assembly 728,026, (Insidence to 101.0120 to 101.0120 to 102.0120, (Insidence to 101.0120) to 101.0120 to 101.	Tealor	5	X8-10096	UPPLEA
Looking assembly, part of push-button tuner assembly, consisting of:	Tuntag	5		
Retainer your assembly			ESD-684055-1	
Cum			ESS-684096-2	
Yoke look sures			ESO-684054-5	-
Onn yoke			ESO-684055-1	AT
1/4-28(NC) hex. nt. 3/8 in. screan				
1/4-28 (MC3) hear, rut 3/8 in. across				
Push button, part of push-button tuner assembly	Tuning .	5	X3+10098	
Front panel guard	Front Pasel Protection	201	850-679593-2	
Binding pass A	Antenna Comechion	Fer drawing	350-678764-16	
				PAR.
arate from on contract.				-

to in depo *Cock. ubos furnibles ks deparate item

19ber

17156 77156 17156 77156 17156 77156 17150 77156 17151

PAR	. 45	5	_	RA	DIC	0 5	ETS	sc	R - 6	08-	A /	ND	50	R - 6	28-	A		TM	11-620
Contractor's Desving Rusher		HSC-670754-19	120-67659-1	200-674652-5	250-680-36-2	200-580741-16	X80-576528-7	E35-696936-3	N=272069=66E	320-686913-1	320-690910-6	MAC-580873-1	330-680333-1	230-580002-1	E30-579429-2	Z50-680274-1	200-580y21-2		
Mr. a. Bode and Type Busher		VET Graving	VS Fer draving	VS For drawing	Va Per drawing	VIII	VE Ter drawing	Per drawing	VE Per drawing	VE Graving	VE Per Graving	VE CHANTAG	VX bur drawing	VR. Per draving	VE Per deserted	VE drawing	VE Per drawing	Deus	Dies
Pure Llon		Ground Commention	Securing Seals Transmitter	Securing Resto Transmitteer.	Coaxtal Cable From FG101	Consist Cable from 5101 to Dinding Fost A	Burdle	Sesister and Capacitor Noushing	Mounting Blik and Plif	Mountfug 8112	Mounting Silt and Silts	(0111-5120 Incl.)	Organal Compartment Cover	Notice Cover	Top Cover	Back Cover	Scotteria	Grystal Druser	Top, Botton-aud Back Cover
Sage and Description of Past	continue).	Strating post 6	And-dom sares [Loal, hold-down cup and apring]	Bold-down apaner	Sable assembly	Table assembly	andla	Mounting plate	Monating plate	Mounting plate	Mounting plate	Cate	Cover	COASE	Cover	Cover	Crystal accket strip	Patterer	Pultane
Stgrit Aurya Stocypusber	b. Midle Treasuitty Sc-684-A (continued).	30519482	80549M89	200194413	2063944,02	3061944.63	2004 pan.	206530-(8A/P3 x	205530-64A/P1	206530-644/15	206494A/5	1 1/4/6150g	3054944/224	PC64944,/125	826536-684A/CI	2064944/027	2064944/310	2004944/91	
Reference	D. Medio Tr	_		1															1 806/944/P2

0-1000000000000000000000000000000000000	0508-3	7														
	1890-19	200-680970-2	. E80-680506-5	820-605325-3	REG-606525-9	E00-675721-6	E00-650851-2		100-680506-3	550-681,967-1	B30-680065-1			ES-8640		350-640100
Per drawing	VE Por drawing	W. Par drawing	Per desving	Per drewing	Fer drawing	NE drawing	NE drawing	Dismond Bo. 6	VS For drawing	Yer drawing	VZ Per drawing	A8:501				5
Spane	Cube Charp	Orystal Storage.	Mounting Foldi	Crystal Seriet Stat (abort institutor)	Crystal Socket Stat (long insulator)	Antonna Stoding Post.	Ground Binding Post	Securing Cabled Viring	Tube Cleap Assembly	Plate or vice	Organia Inawar					Frequency Control
Tube look spaces assessing	Tube clamp	Orystal drawer assembly	Xcanting annex	Ersulator	Insulator	Essister	Tranlator	Cable otsup	Ciden descentig	Fiate comments	Spirit	deans glug betten	Mirdware for Sedio Cransaitter E0-654-A	Mire for Badlo Vennestiter Sc-654-A		E.15Get9 oryesal units W.G. Sinna, Corps Soldors Fr-841-A. Fur absance FFG-309 in the Ff.C. to 90.9-res tange
516/A4/905	2064,944/030	206530-68ta/029	2014914/P1/L	8564944/48	2064944/23	2064911/44	2064944/25	SDE494A/CX2	2000,4944,0530	2054944/032	2064944/3:2	anskyla/hy	28508/81	23508/1	Pailto.	
															c. Seyetal Saite.	

PAR. 45

PAR. 4	15		R	A D	0	SET	s s	CR-	608	- A	AN	D S	CR-	628	- A	,	TM 1	
Contractor's Desking Number			320-677409-8	350-677409-8	x30-677409-7	ESO-678769-17	ES0-675764-15		ES0-650179-1		ESS-680163-1	ESS-680163-1	ESO-650165-3	E80-678721-6				
Type Surber		0-2 Type 59	Chance Fer drawing	Cannon Fer drawing	Cannon Per drawing	vg Per drowing	Per drawing	United No. 46157	UNN Grawing	888	No. Per Grewing	vg Per drewing	NE Grewing	Var drewing				
Punction		Sadio Receiver Transmission- Line Compensator	Madio Meceiver A Connection	Radio Receiver B Connection	Transmiller Competion	Transmitter Antonna	Sadio Sepelver Antenna	Cover for Unused Oable	Shork Absorber	Battery Puse	Rounting Flate	Nomiting 71ste	Flexible Geombling Strap	Antenna Minding	Seconing Nounting to Ventale	Securing Hounting to Vehicle	Securing Bounting to Vehicle	
Name and Description of Part.	Mounting FF-237-(*)	Capacitor, D.CCOl pf., 500 volts do	Receptacle	Receptable	Receptable	Porminal	Terminal	Buston	Wibru-fasulator shotk zonating	Puse, 75 asperte	Yess mounting (part of plate assembly)	Terminal strip (part of plate assembly)	Ground Strap	Insulator	Mounting seres, 5/15-24x9/16 hea.	Nounting screw, 5/16-20x1-3/8 ber. head-iron out mounting screw	Mounting mat, 5/16-24 elastic stop gosating mat	
Signal Corps Stock Busher Pf-237-(*).	226721-2370	309100-20	226721-237A/B1	226721-2374/81	226721-237A/R2	226721-2378,722	226721-2378/91	223480	925500	3221668	14/4/12-12/925	226721-2378/P1	\$20014	N2/YN6Y928	61Agcs-9.242	614905-22.242	62,3505-24	
Rothern Stand Co Forber Stock Num d. Mounting PI-237-(*).		10401	1.7403	1 2402	1 3403	10404	1 3405		-	1 2401	* PMPO.	rako:						

-	_	_									_							
			#30-680504-1	EN0-654051-1	830-680341-5	E30-68c341-6	250-675721-5	250-676721-4	ESO-680941-X			\$50-680164.4	ESO-680364-8	350-680365-2	350-580159-1	B30-680159-34		
		Eterick No. 79		Fer drawing	Yer drawing	ve draving	Per drawing	We drawing	VE Per desuing	7.0	37	VE Fer drawing	VE Per drawing	WR Fer drawing	VE Per draving	VE Per drawing	Dive	
Securing Nounting to Vehicle	Securing Memning to Venicle	Cable Clasp	Battery Commetitues	Covers for Brused Receptables	Long Coaxial Cable	Short Coaxial Cable	Corner for Competion Assembly	7-Shaped Connectur	L-Staped Connector			Total Cable Clamp	Interphone Cable	Cabbed Waring Charp	Kear Cover	End Cover	Date	
5/16-24x3/4 hax. head-lron cap mounting screw	5/16x9/64x5/64 steel nontengling spring look washer	Cable slamp	Signal Corps Cord 50-278	COVER	Coaxial cable	Gearfal cable	Coner	Connector seadebly	Commester Assembly	Rear guide and featener .	Front fastener	Clamp	Olasp	Claup	Covez	Onese	Paelagar	
524905-12.242	\$001Z79	222600	yaza78	226721-2378/01	226721-2374/05	226721-2378/06	256721-2378/C2	226721-2578/011	226781-2378AD12	ezérel-eyja/Ry	226 T21-23 TA/P2	226721-2378/07	80/47(\$-1478E	826721-8374/09	226721-2378/03	226721-257A/04	226721-237A/F1	

or the Table of Replaceable Parts for this unit, see Technical Manual TH 11-306

Remote Control Unit HM-29-D.

PAR.	45			RAD	10	SET	rs :	SCR	- 60	8-	A	A	N D	s c	R - 6	28-5
Contractor's Draving Subber		KB-5981, List 1								Par'se of	1405 1,	7 TOE 3		ES-SHRIIST I		
Mr. s. Code and Type Rusber		Per drawing	0-D Type 147	O-D Sype 189	777e 34P	Type 1V7	Jones 5-5-88	Junes 15-6-An		57		¥	Per drawing	Fer drawing	7.7. # 3.J.	
Percutes		Migh. Woltege Supply. with Jank to Make 12-Yolt Circuit Changes	R-7 By-pare	R-F Sy-pass	R-F By-pass	8-9 By-pass	Prassector Connection and	12-Volt Circuit Charges	Dynamotor Input	Systemotor Onlyws						
Name and Descripition of Pays	tier; id-Volt].	Dynamotor	Ospication, 0.003 p.f. 808 volts do	Capacitor, 0.002 af, 500 volts do	Capacitor, 0.003 pf, 800 velta de	Capacitor, 6,002 ps, 800 volta do	Receptable	Moneytenle	Low-voltage dynamotor brushos	High-voltage dynamics brushes	Dynamotor areature and bearings	Dynamotor bearings	Knd bell	9020W	Lagolowst, 1/2-15. esc.	Rubber groundte
Signal Corps Stock Sunber	f. Oyramotor DM-35-(*) (Transmitter; 12-Volt).	9816350	5-006605	7-5.405	3c9300-2	3xx3-7	3816358/81	3816 954/81	3816 354/bit	381.6354/85	3416354/41	287.42% 5082	3836 354 /827	1879/2/9181	69670	628919
Reference	f. Dyramotor	185501	0201	10501	0900	*10502	1,0501	80%F 4				-	-	-		

Lifetian during manufeture; see Paregraph 45.
Limble in depot atom.

Depot a foreign forming of spores. Tements spare parts list.
To complete disconsist and see a sees lastened of these parts.

TM 11-620

- 5
-
ä
8
d
-9
#
10
2
3
4
22
**
3
.5
74
17
ž
6
11
22
9
×
3
10
2
3
3
31
əl
8
#
5
2
ä
3)
31
60
7
•
J
2
él i
9
BI
비
2
B.
19 (

		Francisco documento	Might-Voltage Supply, with Jack to Make 24-Volt Circuit Charges	Per drawing .	Mar 2011,
1090	309300-8	dapasitor, 0.503 mf, 800 value de	S.P Sp.pass	D-D 235e 187	
1090	3DA3-7	Capacitur, 0.000 p.5 800 valts do	R-F By-pass	TAL AND	
8090	309300-2	Capacitor, 0.005 p.5 800 velts de	N-F hy-pass	Control 197	
3090	5043-7	Capacitor, 0.000 a.f. 800 velts ds	N-F 37-5038	Type 1VP	
2602	M16 99A/B1	Receptagle	Provided Counseller and al-Yelt Circuit Changes	Jones 50-5-48	
2602	3836 358./81	Receptacle	Drawmotor Commotion and 21-Volt Circuit Changes	20000 33-8-68	
	3H16 57A/94	low-voltage dynamotor brushes	Presentar Ingut	7.8	
	3B16.25A/35	High-voltage dynamics brushes	Dynamotor Oglass	9	
	5816 578/A1	Dynamics agains and bearings		99	Parts of
	387.878.788	Dynamotor bearings		9	Lint 2,
	3816378/827	End bell		Sign dead to	
	3616354/81	Sares		Die description	Ka-9950, Lint Q.
	04969	Lubricent, 1/2-ib. oan		N.Y. & R.J.	
	626,629	Subbor groundto		of an artis	
Creery	h. Creenitor DM-34.(*), (Rocoiver; 12-Velt).	18-Velt.).			
102501	and bine	Dynamics Assembly	Migg-Wolfage Supply, with Jesk to Make 12-Yolk Circuit Chames	Per draving	MD-5582.
0701	SDA5-13	Capaditor, 0.005 pf. 800 value do	N-F 27-pass	0.0	

organista distributation on apares. The present apare parts.

PAR.	45			R A	DIO	SE	TS	sci	2-60	8-1		N D	s	R - 6	28	A	. 1
Contractor's Drawing Number														380-690352-2	ESO-680352-5	E80-680352-3	
Type Sunber	9	Type MP	0-D 1770 347	C-D AVE	0-D 77pe 54P	Lype yv	Type yer	0-D	7770 per	Type NP	Cape yer	Cape yer	ž.	ver drawing	WE drawing	WE DENTING	Jones 3-315-43
Punption	h.P fr-cass		R-F Sy-pass	N.P Sy-pass	B-7 3y-yess	E-P 3y-pass	N.P by-pass	8-F by-pats	N-P 39-pass	R.P By-pass	3-F By-pass	R-F By-pass	Migh-Voltage Filter	Low-Voltage Filter	Eigh-Voltage Filter	Low-Woltsge Pilter	Dynamotor Connection And 12-Yelt Circuit Changes
Sage and Description of Part	h. Dynkotos DM:34-(*); Receiver; 12-Volt)(continued).	capacitation of the state of	Oxphettor, 0.005 pf, 800 valts de	Capacitor, 0.003 ht, 1,000 volta de	Capacitor, 0.005 pf, 800 volts do	Capacitor, 0.003 pf, 500 volts do	Capacitor, 0.665 pf, 508 volte de	Capacitor, 0.603 ag 500 volts de	Capacitor, 0.005 pt 800 volts do	Capsoltor, 0.003 af, 1.000 walte do	Capacitor, 0.005 pf, 800 volta de	Capacitor. 0.009 Mf. 1,000 volts do	Choke coll (80-1004)	1700	0633	0011	Receptable
Signal Corps	. IN-34-(*); (Receive	MA 5-24	5245-13	XA3.24	3EM5-13	XXA 3-23	XX8-13	3043-23	30A9-13	30A.5-24	35A5-13	30A3-24	SCHUOJA/CB	2826 344/02	3836 344/02	WI674A/C2	3816944/81
Reference	h. Dynagotos	** 0701	0,100	*****	6040	*10703	**************************************	*1 0TO4	9010	\$070	9020	90201	12,703	12702	11703	1L704	1,7701

TM	11-620
	Listly Pig. 2
	5580
	202

Dynamolor Indul

V.	SUPP	LEMI	NTARY	DATA

ī	A 1	1-62	0	_	_	10.00	_	V. SI	JPPI	E M	ENT	ARY	DA	TA	_	-	1		
	Parts of	ES-5559, Listl.			ES-5952, Listly, Detail 3			KB-5982, List 2											
		~	9	NE drawing	Ver drawing	E.Y. & H.J.		NE drawing	0-0 2770 MP	175 MT	777 WF	Type MP	Type yer	W +421	7770 NF	0-D Type 3v	0-D 7770 947	C-D Type 347	
District to the trainer	Dynamotor Dutput						for information only).	High-Voltage Supply, with Jack to Make 24-Volt Olecuit Changes	R-P by-pass	8-F 2y-pass	2-F Sy-pass	2-F by-pass	A-P By-pass	R-P Sy-pass	R.F Sy-pass	R.F By-pass	N.F Sy-pass	R-F hy-pass	
TON-AGTINGS CAINWOODS SATSONS	High-rollage dynamotor brushes	Dynamics armius and bearings	Dynamotor bearings	End bell	Neses	Lubricant, 1-1/2 lb. can	1. Dynamotor DM-Mc-[*); (Necesymer, 24-Velt) (not furnished on this order; listed for information only).	Dynamitor assembly	"Capacitor, 0.005 p.5 800 wolts de	Capacitor, 0.003 pf 1,000 volte de	Capacitor, 0.005 pf. 800 volts de	Capacitor, 6.007 MG 1,000 volts de	Capacitor, 0.005 pg 800 volts do	Capacitor, 0.003 pf. 500 valts de	Capaction, 0.405 pf, 800 volta do	Capacitor. 0.003 pf, 900 valts de	Capanitor, 0.005 p.c. 800 value de	Ospacitor, 0.005 pf, 1,000 volta de	
SHIELDAW/BY	3416 344/B5	3816,344/81	SILE 344/DE	3016344/827	3816344/51	60670	100-36-(*), (Necel	306300	35A5-13	35M3-84	30A5-13	3DA3-24	XP65-13	3063-23	30A5-13	3043-23	3045-13	3043-24	
						-	1. Dynamotor	мойол	1080	*O803	ogos	*0502	0503	*0803	cBoh	*080*	0803	*0803	


ure; see Paragraph 45.


PAR.	45			R	ADI	0	SETS	5 6	CR.	- 6 (8 -	A	AI	N D	SCR	-628-
Contractor's Icaving Number					msq-680358+8	350-680342-5	R90+680352+5				Parts of	Item 2, Fig. 2		ES-5659, List 2, Detail 3		
Mfr's, Code and Type Number		2-D 247	C.D SAP	2	Fer Graving	We drawing	er drawing	Jones 5-310.An	N N	2	N.		Per drawing	Per drawing	N.Y. & N.F.	
Punction		R-P Sy-pass	3-9 By-pass	Eigh-Foltage Filter	Low-Valtage Filter	Migh-Folloge Pilter	Low-Voltage Pilter	Dynamicor Connection and 24-Volt Circuit Changes	Dynamotor Input	Dynamotor Cutput						
Nean and Description of Part	Dynamotor DM-76-(*); (Receiver; 24-Volt) (continued).	Capacitor, 0.005 pf, 800 volta do	Capacitor, 0.005 az 1,000 volta čo	Choke coll (80-1004)	1700	Cott	dest	Receptions	Low-voltage dynamicor brushes	High-voltage dynamotor brushes	Dynamotor arregule and bearings	Dynamotor bearings	End Dell	Berev	Lubricant, 1/2-1b. com	
Signal Corps	IM-76-(*); (Receiv	SMS-13	3543-29	2044034/38	3826344/51	2816344/02	SH16344/52	MISSAARI	3816 36A/B4	381634A/85	3816364/81	3816 56A/82	7526,868,052K	X216.34A/51	60570	
Reference	. Dynamotor	0800	*c806	1,801	LBoz	£0gr	1,804	1801								


186

TM 11-620


Kfr's. Cods	Name .		Address	
7	Allen-Srediev Co.	136	136 West Greenfield Avenue, Milyaukee, Mis.	á
	attitud Gandani Co.	222	227 Pulton Street, New York, N.Y.	
A1114d	ALLES CONTRACT OF	100	OLD Then Suran Street, Ohlospo, Ill.	
Amphenol	Azerless Phesolic corporation	-	Office ordered by the second or the	
Cannon	Cannon Electric Development Co.	929	AND West Avenue 35, Los Argeles, Calli.	
d-S	Coynell-Dibiller Electric Corp.	200	South Flainfield, M.T.	
Dismond	Diamond Expansion Bolt Co.	ONC	Mewood, B.J.	
Danke	Deale Manufacturing Co.	171	713 West Hubbard Street, Chicago, 111.	
1000	Date Restoner Co., 380.	Bot	ehylon, N.Y.	
Defe.	Nets Bestator Corporation	S-22	P-26, Fa.	
200	Canada Riestpie Co.	Set	Schmeetedy, N.Y.	
	Armon Dart & Radgest, Stadtwin Co.	Bar	Sartford, Open.	
Date:	Votesment found Bandahance Co.	101	Of Horth Brosd Street, Philadelphia, Fa.	
200	Taclandilla. Tonomenanial	233	33 Sposieny, Sev Zork, N.Y.	
ANTOURTER	Townson Study Manufacturing Co.	099	Sol Seuth Larente Svenue, Chicago, 111.	
1000en	CONTRACT CONTRACTOR OF THE CONTRACTOR		Carpo Galaccala duestes (Money, 211).	
Copes	HOWERT B. Jones	230	O MEDITOR PARENCE, CHANGES ALL	
14850	littelfuse, Inc.	475	757 Sevenswood Avenue, Chicago, 111.	
Mallory	P. R. Ballory & Co., Ibc.	Zec	Indianapolis, Ind.	
100	Mother Company	125	255 South Michigan Avenue, Chicago, 111.	
Bartonal	Settonal Company	Xe3	balden, Mess.	
1 1 4 5 1	You York and Hew Jersey Lubricant Co.	300	000 Delancey Street, Hewark, N.J.	
200	Tak Manufleding Do.	356	Sée dippoura Averue, Chicago, Ill.	
Specifical Co.	then the Manufacturing Co.	183	4837 Flowmany Street, Chicago, Ill.	
200	BCA Manufacturing Co., Inc.	SAZ	Sarthon, N.J.	
Stanoor	Spencer Thermostat Co.	455	tilebors, Mass.	
Wated	United-Carr Pastener Corp.	Caso	Achtidge, Mess.	
liste	faited States Subter Co.	19.	9. Ruderm Street, Bew York, S.Y.	
3	Nastaen Blastein Co Inc.	120	120 Broadway, New York, M.Y.	
	Navi-Leonard Steatete Onto.	35	52 South Street, Mount Vernon, H.Y.	
Mango	Newton Riestrical Retrement Corp.	619	618 Preylingbuysen Avenue, Newark, N.J.	
Tantok	Storick Manufacturing Co.	386	555 Derard Avenue, New York, N.T.	

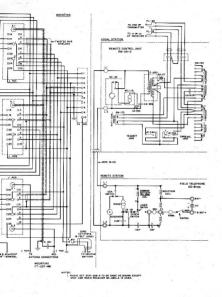


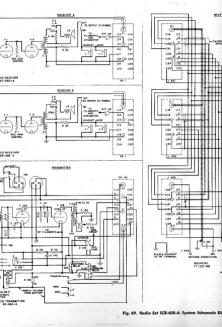

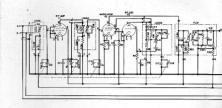



COMO.	DESCRIPTION	2100.	CAPACITORS DESCRIPTION	prueo.	DESCRIPTION	SWIN	OCCUPATION
929253		0 87	CODE OF MO V CO LE SOO V COOL OF SOO V SOUR ME SOO V COOL OF SOO V	6 804 6 806 6 808	000 0001 F 1007	333	PROFIT PANEL PLUE
UB.	SELECT MENT	0 66	10 UIF WHAT BOOK	_	00115	2.0	
20000	0.000 UF 100 V 0.000 UF 100 V 0.000 UF 100 V	0 M	50 UAF SEE NOTES 0006 UF 500 V 100 50 UF 500 V 500 UF 500 V 50 UF 600 V	22.2	LAFTEN CHRISCH CHOICE ATTENNA COLFLAG AT PLATE NCC CHE	11	800A 80000A
000000000000000000000000000000000000000	000 UF 500 V 000 UF 500 V 000 F 500 V 000 F 500 V 000 F 500 V 000 UF 500 V 000 UF 500 V 00 UF 500 V	0 m 0 m 0 m 0 m 0 m 0 m 0 m 0 m 0 m 0 m	DUF SET NOTE DOWN TO DESCRIPT SET NOTE DOWN TO DE SET NOTE DE SET	TENSOR STATE	ONE PRINT COM I I I I I I I I I I I I I I I I I I I	# 1 # 8 # 8 # 8 # 8 # 8 # 8 # 8 # 8 # 8 # 8	E 5 5 7 0 4 5 25000 A 19W 15000 A 17W 15000 A 12W
6 83.5 6 83.5 0 8 0 92 0 92 0 94 0 95	01 IF 800 Y 01 IF 800 Y 000 IF 800 Y 0005 IF 800 Y 1 IF 800 Y 2 IF 800 Y 2 IF 800 Y	0 M 0 M 0 M 0 M 0 M	to the sco v	L 708 L 708 L 708 L 704	2 7 700	***	2000 V 1 A MARIN 2000 V 1 A M
30	60 0008 UF 300Y		100	000	DAMPOLD DR-20-DEGES		30,000 A 12 W
0.00	5 (UF 500 V 500N UF 500 V 500 UF 500 V 500 UF 500 V 50 UF 500 V	0 708 0 708 6 708 6 708	0005-0001F 600V 0005-0001F 600V 0005-0001F 600V 0005-0001F 600V	L 900 L 900 L 900	W W FLIR	1000	\$,000 A 15 W \$0 A 15 W \$500 A 15 W
0 45	20 UF 500 V	6 706	-0:005 UF 800 V			F 80	
C 53	100 MF 100 V 100 MF 100 V 100 MF 100 V			1111	PRINCES PRINCES FRONT ISSNEL, JACK	1 30	50000 A 1 W 50000 A 15 W 50000 A 15 W
0.54	IT HET SEE NOTES	GRADES	PROSERVED DOS-34-000 24 5	J 801	DAMACTOR JACK	1.30	
0 55	SOURT SEE MOTE	0 most	0000 0000 UF 800V			11	100,000 A 12 W 100,000 A 12 W 13,000 A 12 W

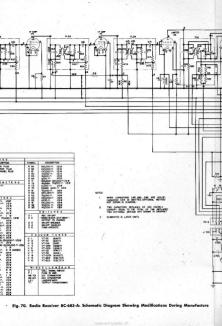

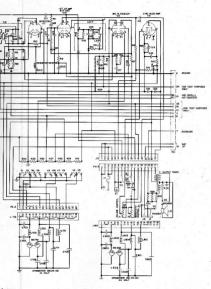

facture

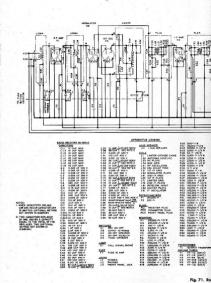

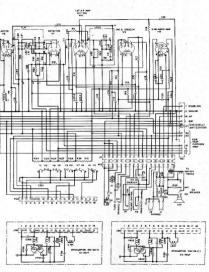

hematic Diagram

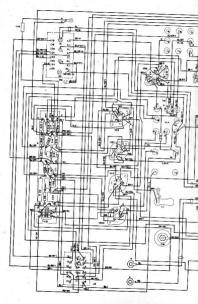
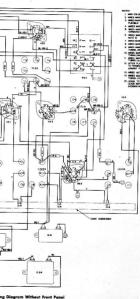
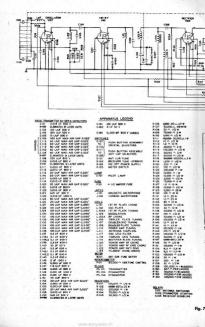
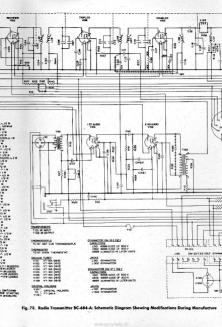
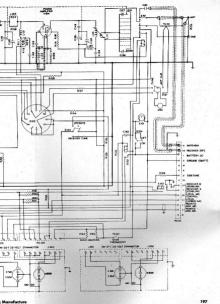


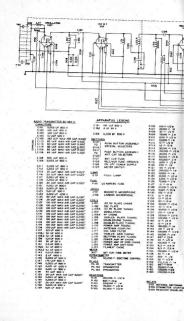
Fig. 72. Radio Receiver B

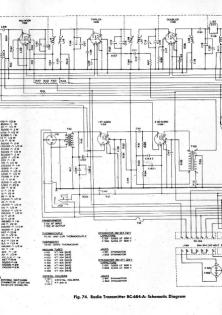


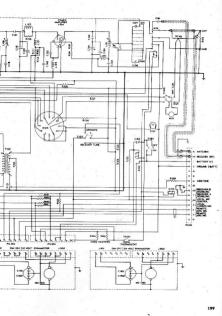


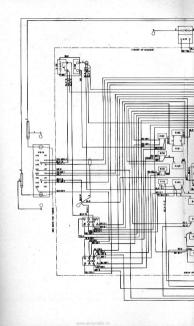


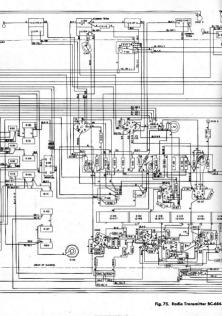


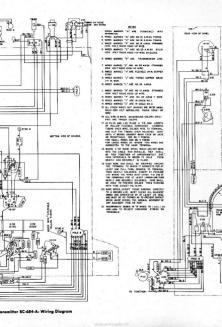


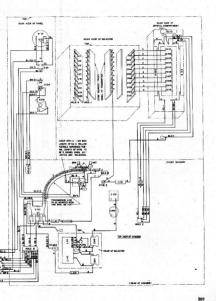













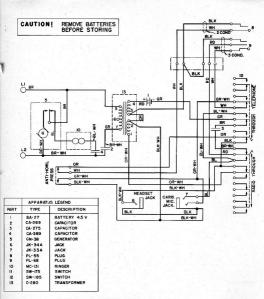


Fig. 76. Remote Control Unit RM-29-D: Schematic and Wiring Diagram

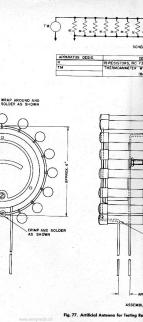

SCHEMATIC CIRCUIT DIAGRAM

DESCRIPTION
ISTORS, IRC F3, EACH 600 OHMS/APPROX. 40 OHMS TOTAL!
ROAMMETER WESTON MODEL 425 O-1 AMP.
(BANELITE CASE, FLUSH MOUNTING)

